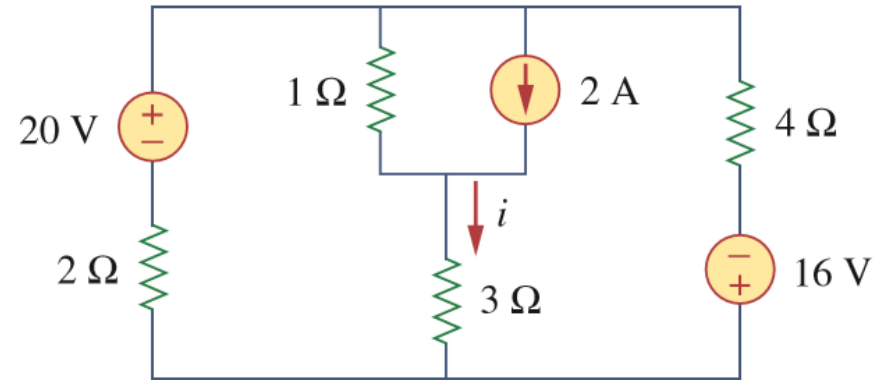


Weeks 1-4 Revision

Basis methods for circuit analysis

- Ohm's Law
- Voltage/Current Division Laws
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Nodal Analysis
- Mesh Analysis
- Superposition
- Source Transformation
- Thévenin's Theorem
- Norton's Theorem
- Maximum Power Transfer




Indicative Course Structure

Wk. No	Summary of Lecture Program
1	Introduction, Circuit Basics Overview + Lab Safety.
2	Kirchhoff's laws - Resistive circuits, Series & Parallel circuits, Power & Energy
3	Node Equations & Circuit analysis
4	Circuit theorems – Thévenin, Norton, Superposition Theorems, MPT
5	Energy storage elements - inductors and capacitors, energy storage
6	First order circuits – RL & RC circuits, transient responses
7	Introduction to AC/sinusoidal analysis, phasors & phasor diagrams
8	Sinusoidal steady-state analysis, AC circuit analysis, AC power analysis
9	Transformers and voltage shaping circuits
10	Operational amplifiers
11	Digital systems, number representation
12	Combination logic, digital circuit analysis

Weeks 5-12 Contents

Other electrical/electronic elements

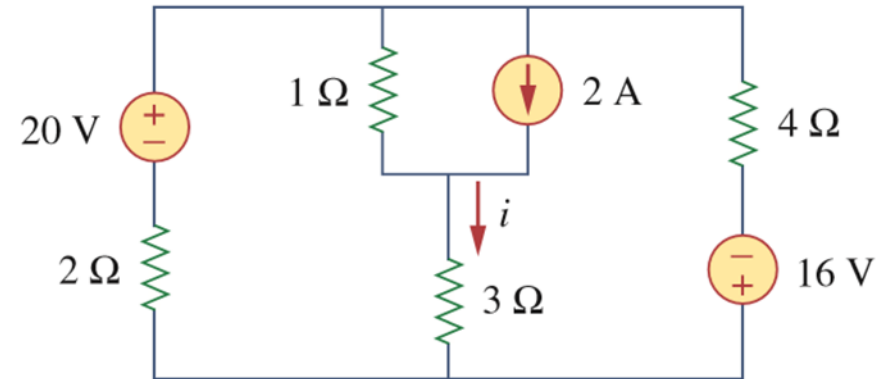- Capacitor
- Inductor
- OpAmp
- Transformers



AC signals (sinusoid signal)

- Phasor
- AC Power

Combination logic, digital circuit analysis

The basic laws & analysis methods in weeks 1-4 can be applied in all electrical circuits and will be used in the rest of semester



Lecture 7: Capacitors and RC Transients

ELEC1111 Electrical and Telecommunications Engineering


Never Stand Still

Faculty of Engineering

School of Electrical Engineering and Telecommunications

Capacitors

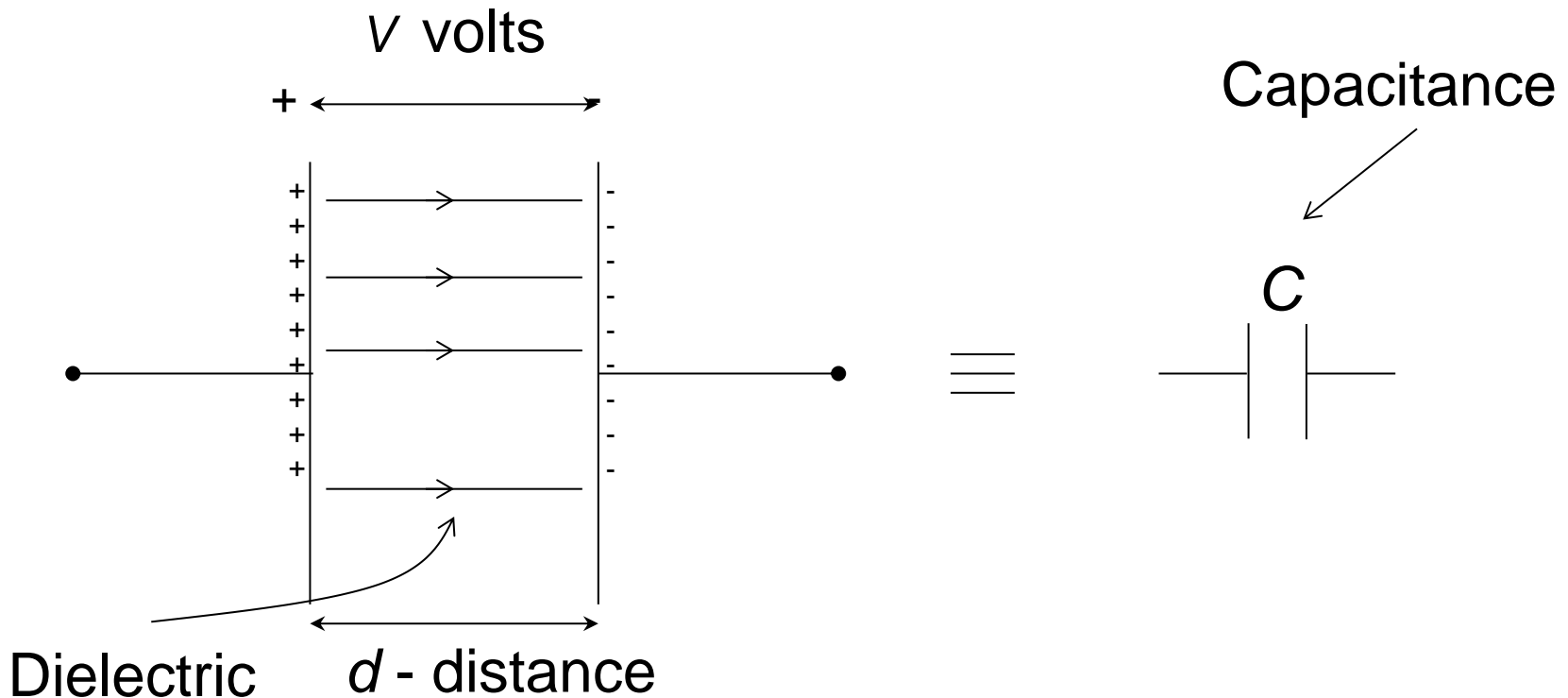- ✓ **Capacitor:** Constructed using two parallel conducting plates separated by an insulating material (e.g. air)



- ✓ **Capacitance** is a measure of capacitor's ability to store charge on its plates. (i.e. its storage capacity)

- ✓ A capacitor has a **capacitance** of 1 farad if 1 coulomb of charge is deposited on the plates by a potential difference of 1 volt across the plates.
- ✓ Expressed as an equation, the capacitance is determined by

$$C = \frac{Q}{V}$$

C = farads (F)

Q = coulombs (C)

V = volts (V)


Note: $C = 4 \text{ F}$

$C = 6 \mu\text{F}$ (microfarad) = $6 \times 10^{-6} \text{ F}$

$C = 2 \text{ nF}$ (nano farad) = $2 \times 10^{-9} \text{ F}$

$C = 3 \text{ pF}$ (pico farad) = $3 \times 10^{-12} \text{ F}$

$$\uparrow C = \frac{\uparrow Q}{V}$$

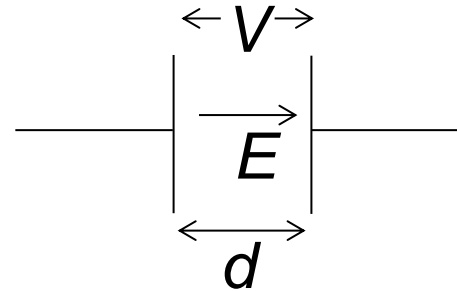

$$E = \frac{V}{d}$$

↗ Electric field strength ← Potential difference
 ← distance between the plates
 (volts/metres)

$$C = \underset{\substack{\uparrow \\ \text{dielectric constant} \\ \text{or} \\ \text{relative permittivity}}}{\varepsilon} \frac{A}{\underset{\substack{\leftarrow \\ \text{distance between} \\ \text{the plates)}}}{d}}$$


area of the plates

$$\varepsilon = \underset{\substack{\uparrow \\ \text{permittivity for vacuum} \\ [8.85 \times 10^{-12} \text{ F/m}]}{\varepsilon_0}} \varepsilon_r$$


$$\begin{aligned} \varepsilon_r &= 1 \text{ for vacuum} \\ &= 7 \text{ for glass} \\ &= 2 \text{ for nylon} \end{aligned}$$

- ✓ **Breakdown Voltage:** The maximum voltage that can be applied across a capacitor is known as the breakdown voltage.

Note:

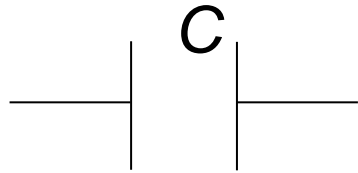

Fixed capacitor

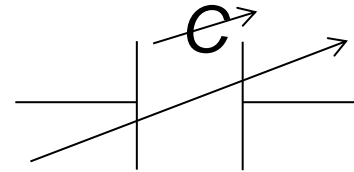


Variable capacitor


Standard values of capacitor:

$10\text{pF}, \dots, 0.01\mu\text{F}, 0.1\mu\text{F}, 0.22\mu\text{F}, 0.33\mu\text{F}, \dots > 1\mu\text{F}, 2.2\mu\text{F}, 3.3\mu\text{F}, 4.7\mu\text{F}, \dots$

No polarity

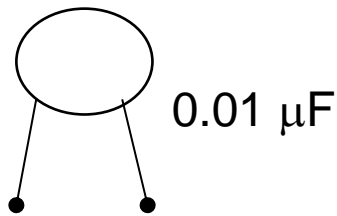


polarity is important

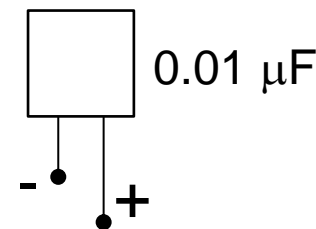

Capacitors in Series and Parallel

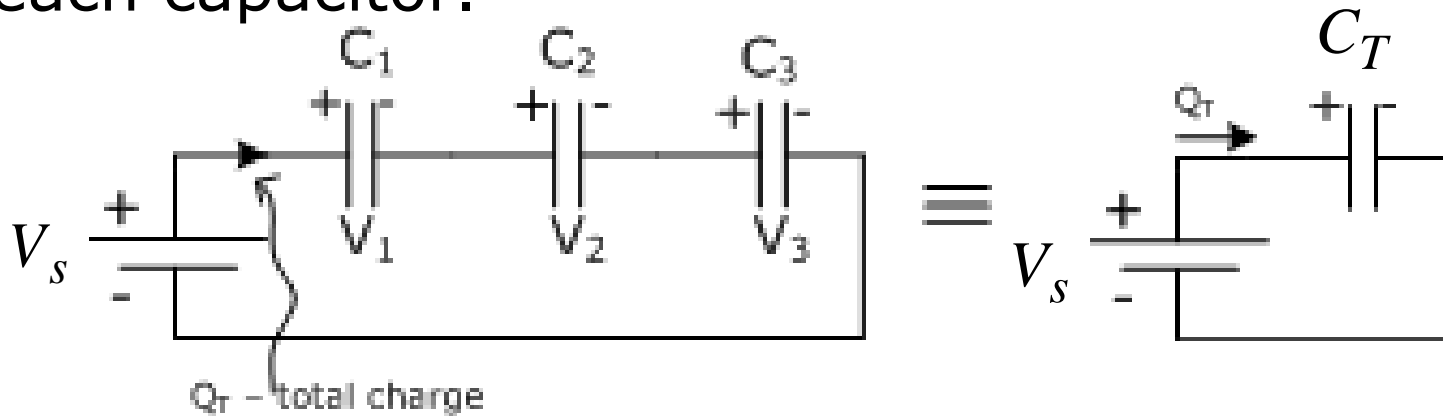- ✓ Capacitors, like resistors, can be placed in series and in parallel.
- ✓ **Capacitors in Series:** the charge is the same on each capacitor.



$$V_s = V_1 + V_2 + V_3$$

$$\frac{Q_T}{C_T} = \frac{Q_T}{C_1} + \frac{Q_T}{C_2} + \frac{Q_T}{C_3}$$

$$\therefore \frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$


- ✓ The total capacitance of two capacitors in series is

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\therefore C_T = \frac{C_1 C_2}{C_1 + C_2}$$

Capacitors in Parallel

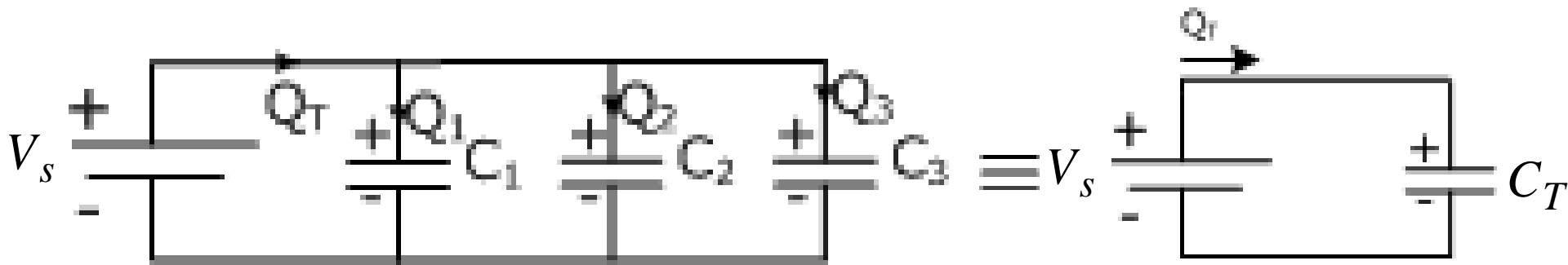- ✓ For capacitors in parallel, the voltage is the same across each capacitor, and the total charge is the sum of that on each capacitor.



Q_T – total charge

$$Q_T = Q_1 + Q_2 + Q_3$$


$$C_T V_s = C_1 V_s + C_2 V_s + C_3 V_s$$

$$\therefore C_T = C_1 + C_2 + C_3$$


For the circuit shown below,

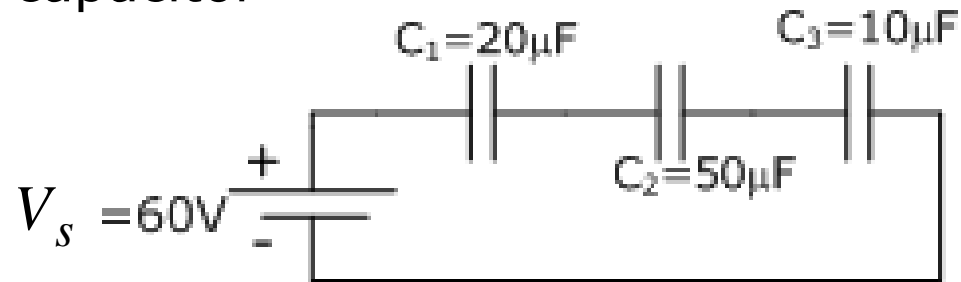- (a) Find the total capacitance
- (b) Determine the charge on each plate
- (c) Find the voltage across each capacitor

$$\begin{aligned} \text{(a)} \quad \frac{1}{C_T} &= \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \\ &= \frac{1}{20 \times 10^{-6}} + \frac{1}{50 \times 10^{-6}} + \frac{1}{10 \times 10^{-6}} \\ &= 0.05 \times 10^6 + 0.02 \times 10^6 + 0.1 \times 10^6 \\ \frac{1}{C_T} &= 0.17 \times 10^6 \\ \therefore C_T &= \frac{1}{0.17 \times 10^6} \\ &= 5.88 \mu\text{F} \end{aligned}$$


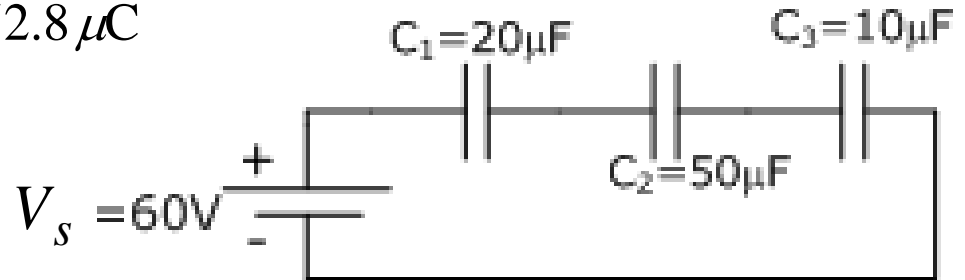
$$(b) \quad Q_T = C_T V_s = 5.88 \mu F \times 60 = 352.8 \mu C$$



$$(c) \quad V_1 = \frac{Q_T}{C_1} = \frac{352.8 \times 10^{-6} C}{20 \times 10^{-6} F} = 17.64 V$$

$$V_2 = \frac{Q_T}{C_2} = \frac{352.8 \times 10^{-6} C}{50 \times 10^{-6} F} = 7.056 V$$

$$V_3 = \frac{Q_T}{C_3} = \frac{352.8 \times 10^{-6} C}{10 \times 10^{-6} F} = 35.28 V$$


$$\text{and} \quad V_s = V_1 + V_2 + V_3 \\ = 60V$$

For the network shown below,


(a) Find the total capacitance

(b) Determine the charge on each plate

(c) Find the total charge

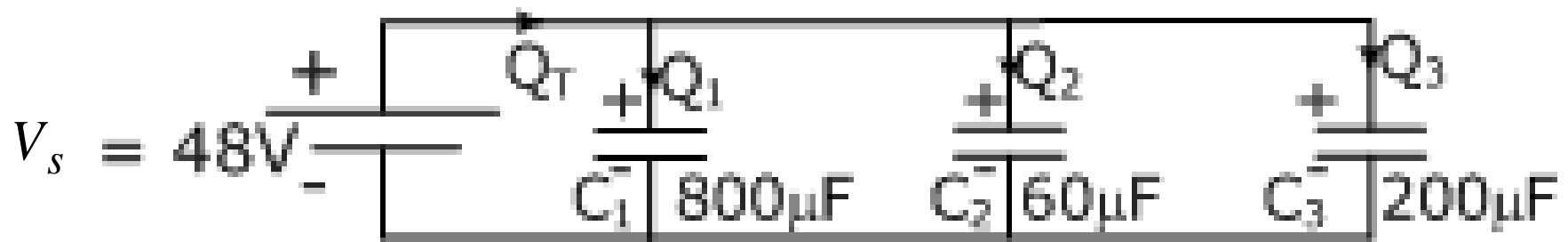
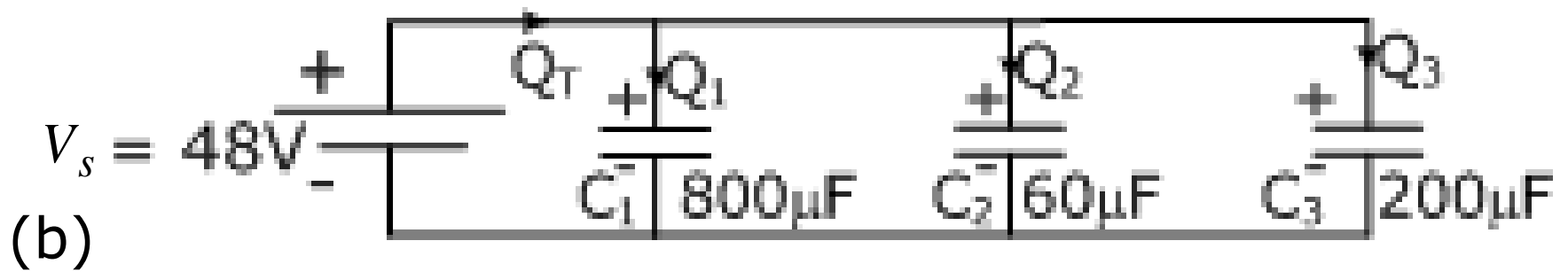
$$\begin{aligned} \text{(a)} \quad C_T &= C_1 + C_2 + C_3 \\ &= 800\mu F + 60\mu F + 200\mu F \\ &= 1060\mu F \end{aligned}$$



$$Q_1 = C_1 V_s = (800 \times 10^{-6} F)(48V) = 38.4\text{mC}$$

$$Q_2 = C_2 V_s = (60 \times 10^{-6} F)(48V) = 2.88\text{mC}$$

$$Q_3 = C_3 V_s = (200 \times 10^{-6} F)(48V) = 9.6\text{mC}$$

(c)

$$\begin{aligned} Q_T &= Q_1 + Q_2 + Q_3 \\ &= 38.4\text{mC} + 2.88\text{mC} + 9.6\text{mC} \\ &= 50.88\text{mC} \end{aligned}$$

Example


Find the voltage across and charge on each capacitor.



$$C_T' = C_2 + C_3 = 4\mu\text{F} + 2\mu\text{F} = 6\mu\text{F}$$

$$C_T = \frac{C_1 C_T'}{C_1 + C_T'} = \frac{(3\mu\text{F})(6\mu\text{F})}{3\mu\text{F} + 6\mu\text{F}} = 2\mu\text{F}$$
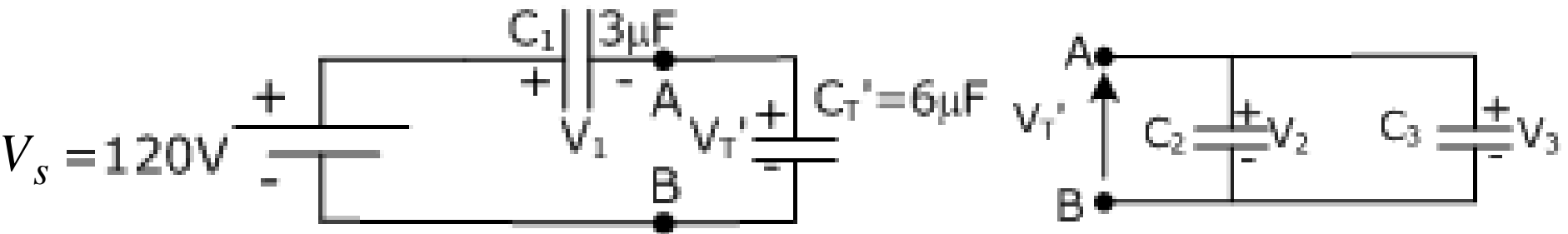
$$\begin{aligned} Q_T &= C_T V_s \\ &= (2\mu\text{F})(120\text{V}) \\ &= 240\mu\text{C} \end{aligned}$$



$$V_1 = \frac{Q_T}{C_1} = \frac{240 \times 10^{-6} \text{C}}{3 \times 10^{-6} \text{F}} = 80 \text{V}$$

$$V_T' = \frac{Q_T}{C_T'} = \frac{240 \times 10^{-6} \text{C}}{6 \times 10^{-6} \text{F}} = 40 \text{V}$$

$$\therefore Q_2 = C_2 V_2 = C_2 V_T' = (4 \times 10^{-6} \text{F})(40 \text{V}) = 160 \mu\text{C}$$

$$Q_3 = C_3 V_3 = C_3 V_T' = (2 \times 10^{-6} \text{F})(40 \text{V}) = 80 \mu\text{C}$$


Energy stored by a capacitor

- ✓ An ideal capacitor stores the energy in the form of an electric field between the capacitor plates.
- ✓ Energy stored

$$W_c = \frac{1}{2} CV^2 \quad \text{Joules}$$
$$= \frac{Q^2}{2C} \quad (\text{J})$$

- ✓ V is the **steady-state** voltage across the capacitor.

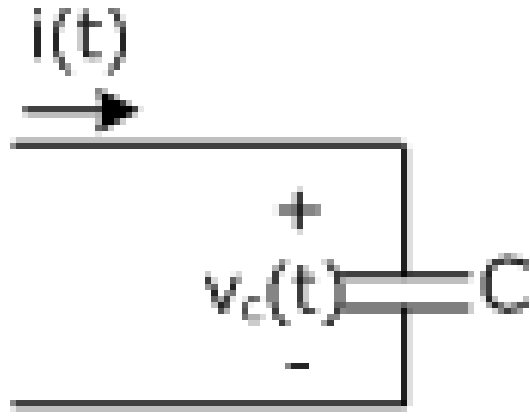Instantaneous current, voltage, charge on a capacitor



$i(t)$ – instantaneous current

$v_c(t)$ – instantaneous voltage across the capacitor

$$q(t) = C v_c(t)$$

$$\frac{dq(t)}{dt} = C \frac{dv_c(t)}{dt}$$

$q(t)$ – instantaneous charge on the capacitor

$$\parallel$$
$$i(t) = C \frac{dv_c(t)}{dt}$$


$$\Rightarrow v_c(t) = \frac{1}{C} \int_0^t i(t) dt$$

- ✓ **Instantaneous** power delivered to the capacitor

$$p(t) = v_c(t)i(t)$$

$$= v_c(t)C \frac{dv_c(t)}{dt}$$

$$= Cv_c(t) \frac{dv_c(t)}{dt}$$

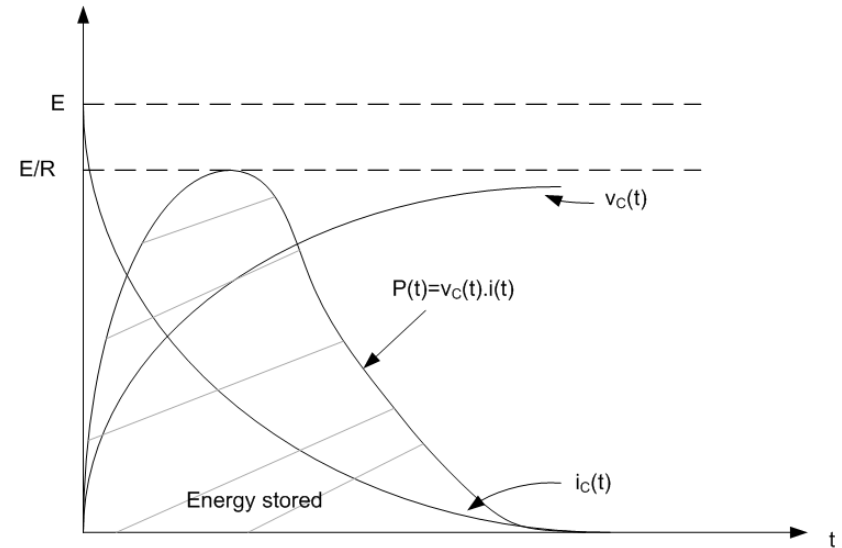

- ✓ The energy stored in the capacitor

$$w_c(t) = \int_0^t p(t)dt$$

$$= \int_0^t v_c(t)C \frac{dv_c(t)}{dt} dt$$

$$w_c(t) = C \int_0^t v_c(t)dv_c(t)$$

$$w_c(t) = \frac{1}{2} C v^2(t)$$


Transients in Capacitive Networks

Reference(s): Introductory Circuit Analysis – Boylestad,
Prentice Hall, 2000



Transients in Capacitive Networks

RC circuit: Charging Phase

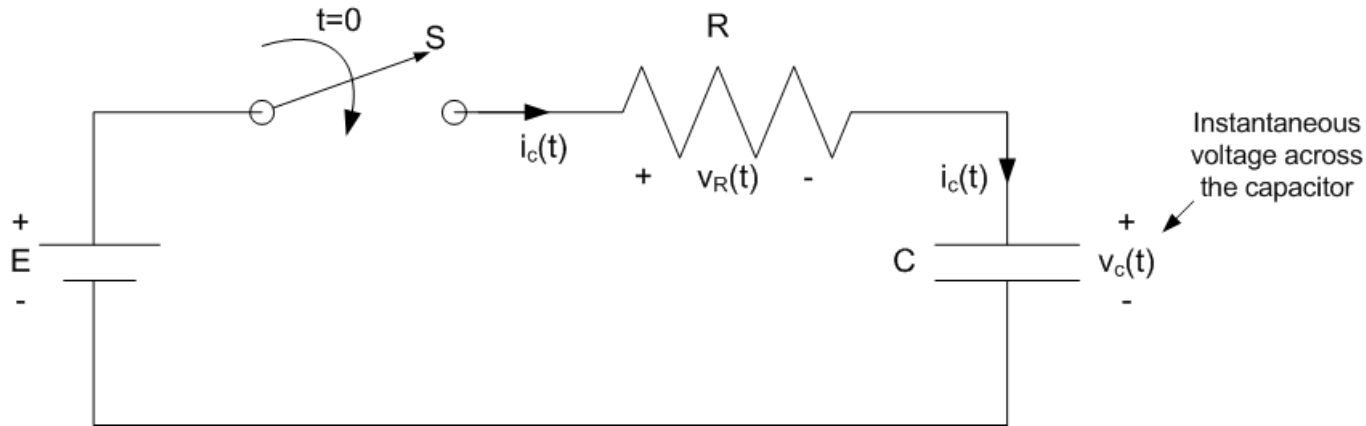

- ✓ when the switch **s** is closed at $t = 0$, $i_c(t)$ is the changing current, t is time



$$i_c(t) = C \frac{dv_c(t)}{dt} \quad \begin{aligned} E &= R i_c(t) + v_c(t) \\ &= RC \frac{dv_c(t)}{dt} + v_c(t) \end{aligned} \quad \therefore \boxed{\frac{dv_c(t)}{dt} + \frac{1}{RC} v_c(t) = \frac{E}{RC}}$$

Transients in Capacitive Networks

RC circuit: Charging Phase

$$\begin{aligned}\frac{dv_c(t)}{dt} &= \frac{1}{RC} [E - v_c(t)] \\ \therefore \int_0^t \frac{dv_c(t)}{E - v_c(t)} &= \frac{1}{RC} \int_0^t dt \\ \therefore \frac{t}{RC} &= -[\ln(E - v_c(t))]_0^t \\ -\frac{t}{RC} &= \ln \left[\frac{E - v_c(t)}{E} \right] \\ \frac{E - v_c(t)}{E} &= e^{-\frac{t}{RC}}\end{aligned}$$
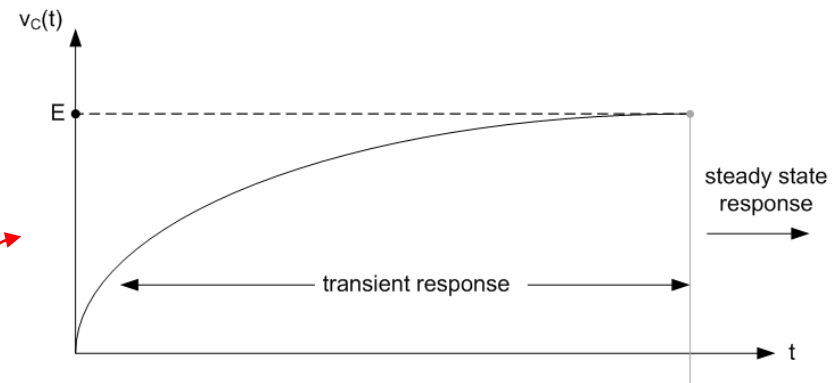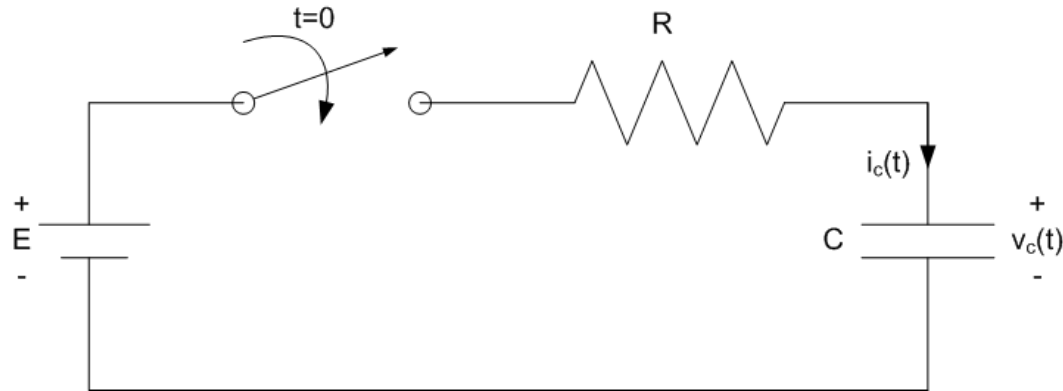
$$\therefore v_c(t) = E \left(1 - e^{-\frac{t}{RC}} \right) \quad (1)$$



Transients in Capacitive Networks

RC circuit: Charging Phase

$$v_C(t) = E(1 - e^{-\frac{t}{RC}})$$

$$\begin{aligned} i_C(t) &= C \frac{dv_C(t)}{dt} \\ &= C \cdot E \left[0 - \left(-\frac{1}{RC} \right) \cdot e^{-\frac{t}{RC}} \right] \end{aligned}$$

$$i_C(t) = \frac{E}{R} e^{-\frac{t}{RC}} \quad (2)$$


$$\begin{aligned} v_R(t) &= i_C(t)R \\ &= E e^{-\frac{t}{RC}} \end{aligned} \quad (3)$$

Transients in Capacitive Networks

RC circuit: Charging Phase

Current $i_c(t)$

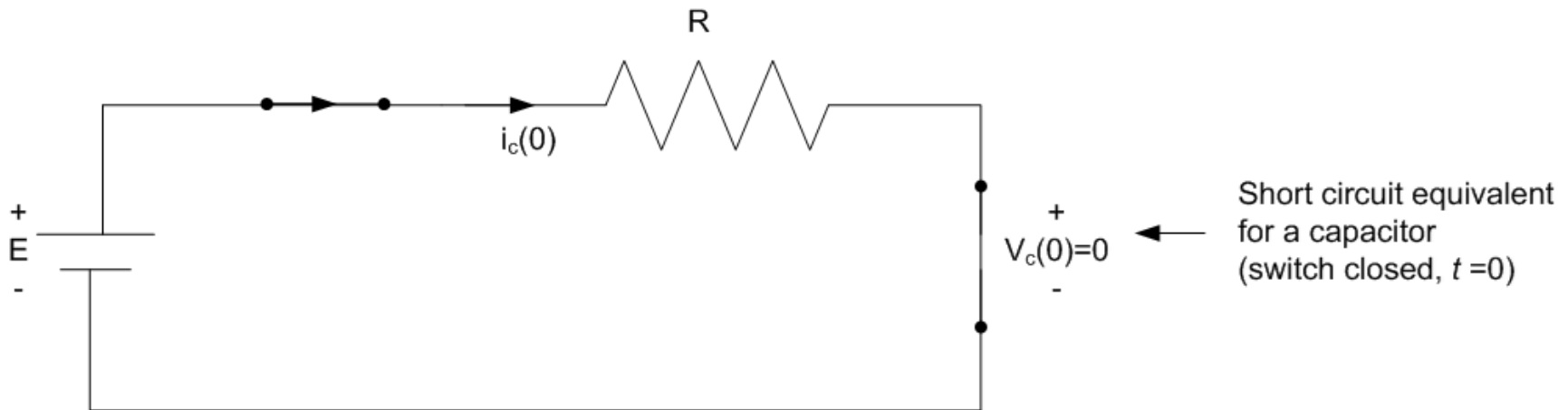- ✓ When the switch is closed at $t = 0$ sec, the current jumps to a value limited by the resistance of the RC circuit and then decays to zero as the capacitor is charged.
- ✓ At the instant the switch is closed, the capacitor behaves as a short circuit




Transients in Capacitive Networks

RC circuit: Charging Phase

Voltage $v_c(t)$

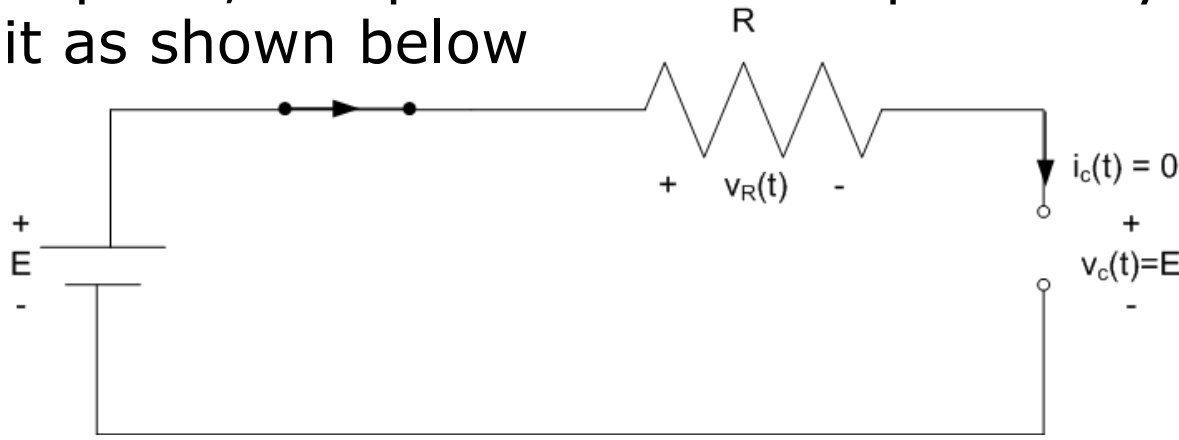- ✓ When the switch is closed at $t = 0$, the voltage across the capacitor is zero [assuming no initial charge on the plates of the capacitor]. As the current $i_c(t)$ decreases, the voltage $v_c(t)$ increases. Eventually the current $i_c(t)$ will be zero and the voltage $v_c(t)$ will be E .
- ✓ At this point, a capacitor can be replaced by an open circuit as shown below



Time Constant

- ✓ The factor RC in the following capacitor charging phase equations


$$\left[\begin{array}{l} V_C(t) = E \left[1 - e^{-\frac{t}{RC}} \right] \\ i_c(t) = \frac{E}{R} e^{-\frac{t}{RC}} \end{array} \right]$$

is called the **time constant**. Its symbol is τ (*tau*) and its unit of measure is seconds.

$$\tau = RC \text{ seconds}$$

$$\therefore \left[\begin{array}{l} V_C(t) = E \left[1 - e^{-\frac{t}{\tau}} \right] \\ i_c(t) = \frac{E}{R} e^{-\frac{t}{\tau}} \end{array} \right]$$


Time Constant

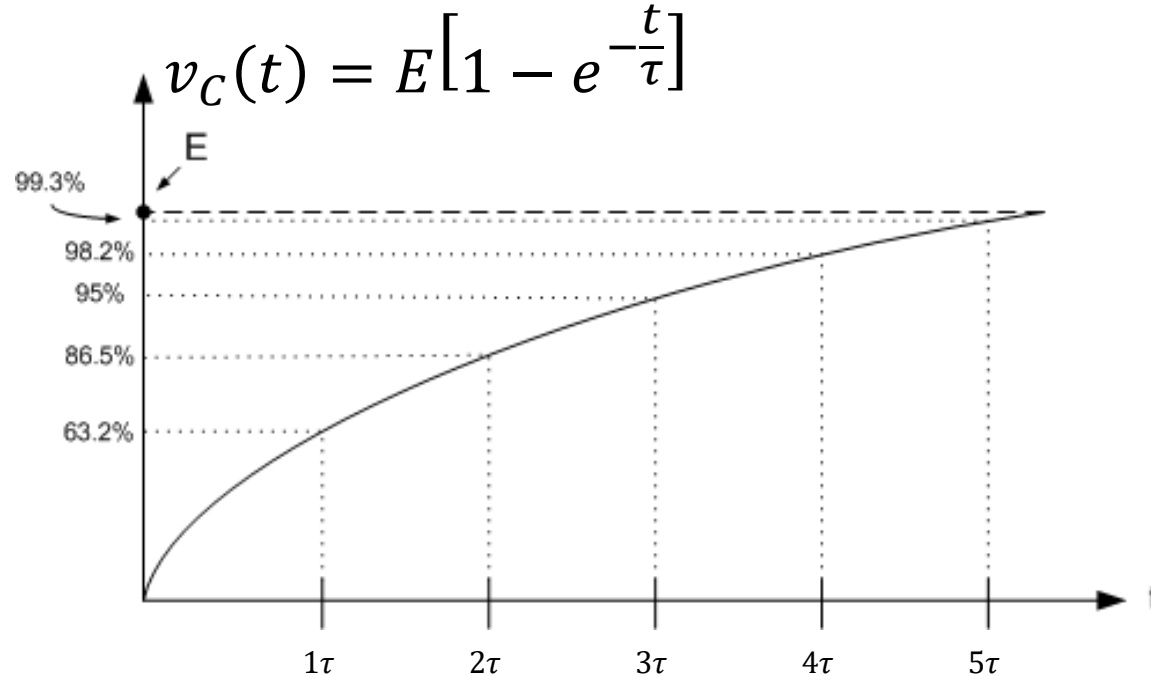

$$\tau = RC$$

The voltage across a capacitor cannot change instantaneously. The voltage across the capacitor is approximately equal to the supply voltage after five time constants, 5τ , of the charging phase have passed.


Time Constant

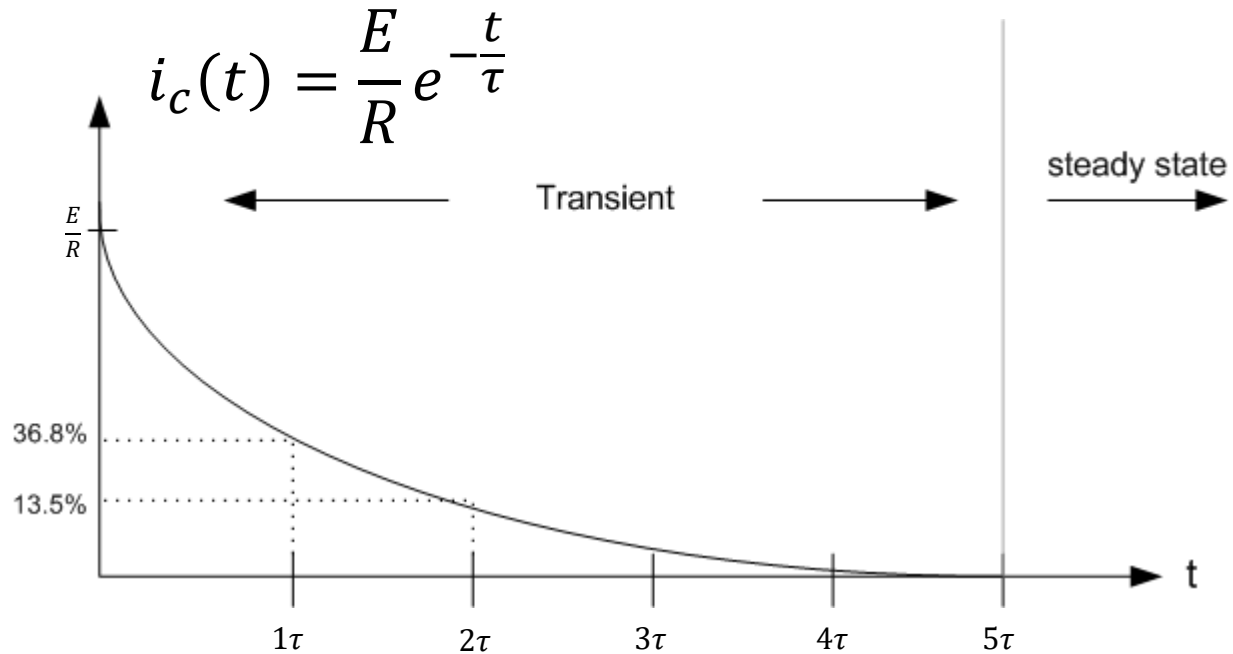

The current $i_c(t)$ of a capacitive network is approximately zero after five time constants of the charging phase have passed in a DC circuit.

Time Constant

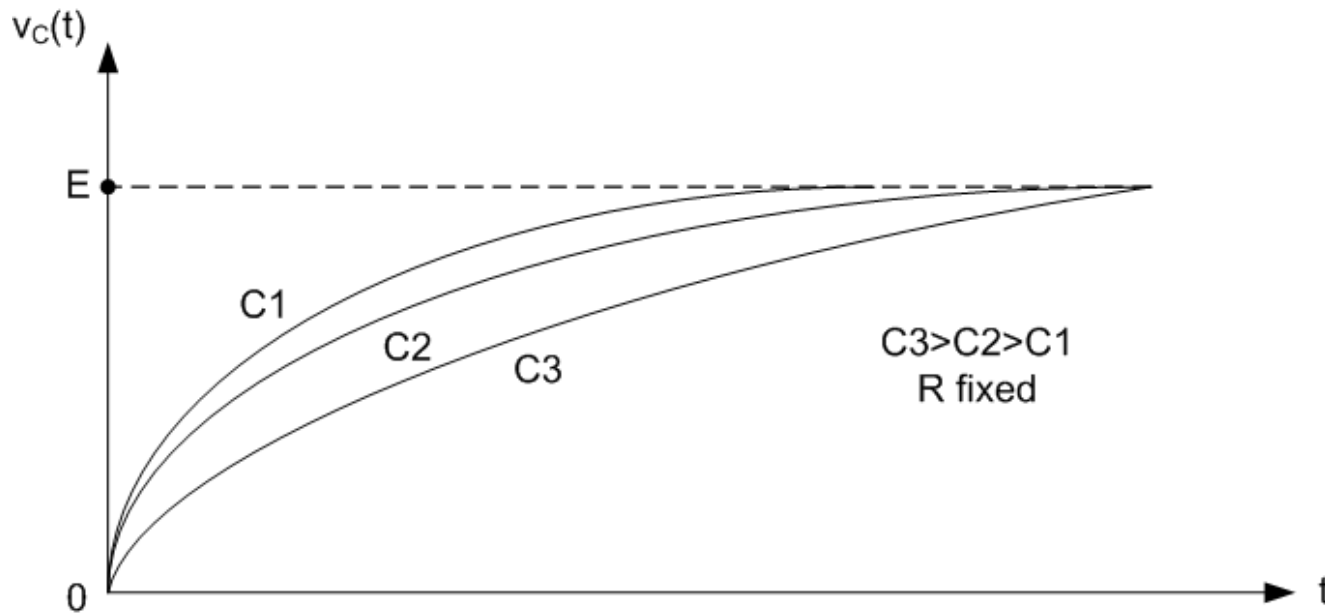- ✓ The capacitance of a DC (assuming R is fixed) circuit is also a measure of how quickly the capacitor could be charged.
- ✓ The larger the capacitance, the larger the time constant, and longer it takes to charge up to its fixed value




Time Constant

- ✓ A smaller capacitance would permit the voltage to build up more quickly since the time constant is smaller
- ✓ Once the voltage across the capacitor has reached the input voltage E , the capacitor is fully charged

RC circuit: Discharge Phase

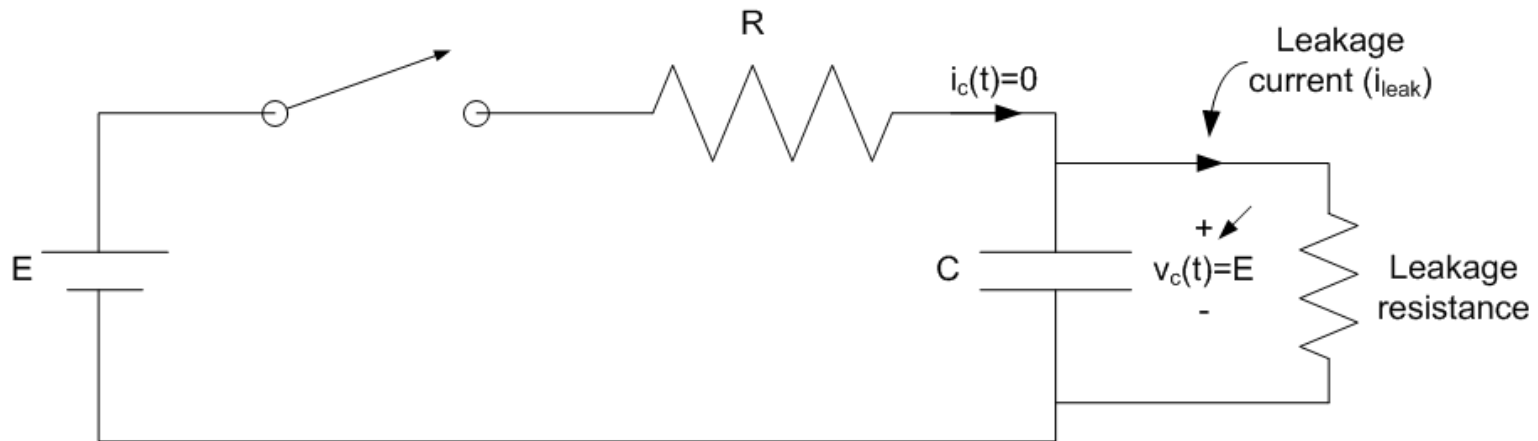- ✓ If the switch is opened (after fully charging the capacitor) see figure below




- ✓ The capacitance will retain its charge for a period of time determined by its leakage current.
- ✓ For capacitors such as the mica and ceramic, the leakage current is very small, enabling the capacitor to retain its charge for a long time.

RC circuit: Discharge Phase

- ✓ For electrolytic capacitors, which have a very high leakage currents, the capacitor will discharge more rapidly
- ✓ Note: a charged capacitor should be completely discharged by a lead (connecting both terminals) before they are handled

RC circuit: Discharge Phase

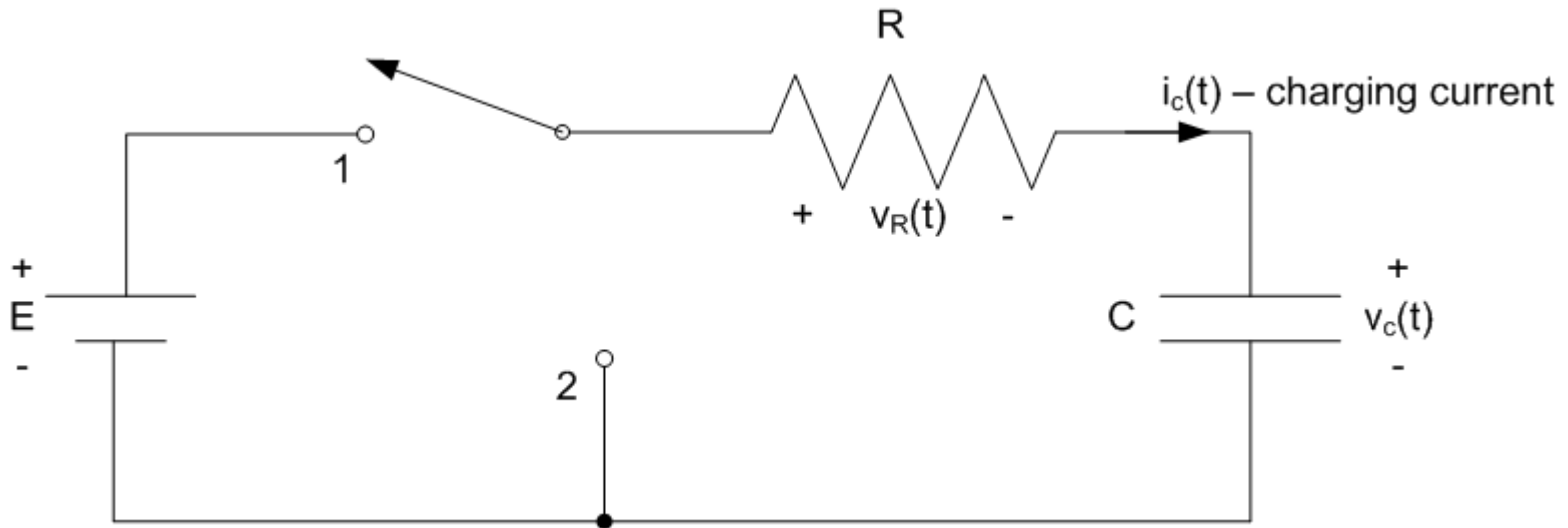
- ✓ The circuit below is designed to both charge and discharge the capacitor



When the switch is placed in position 1, the capacitor will charge toward the supply voltage.

RC circuit: Discharge Phase

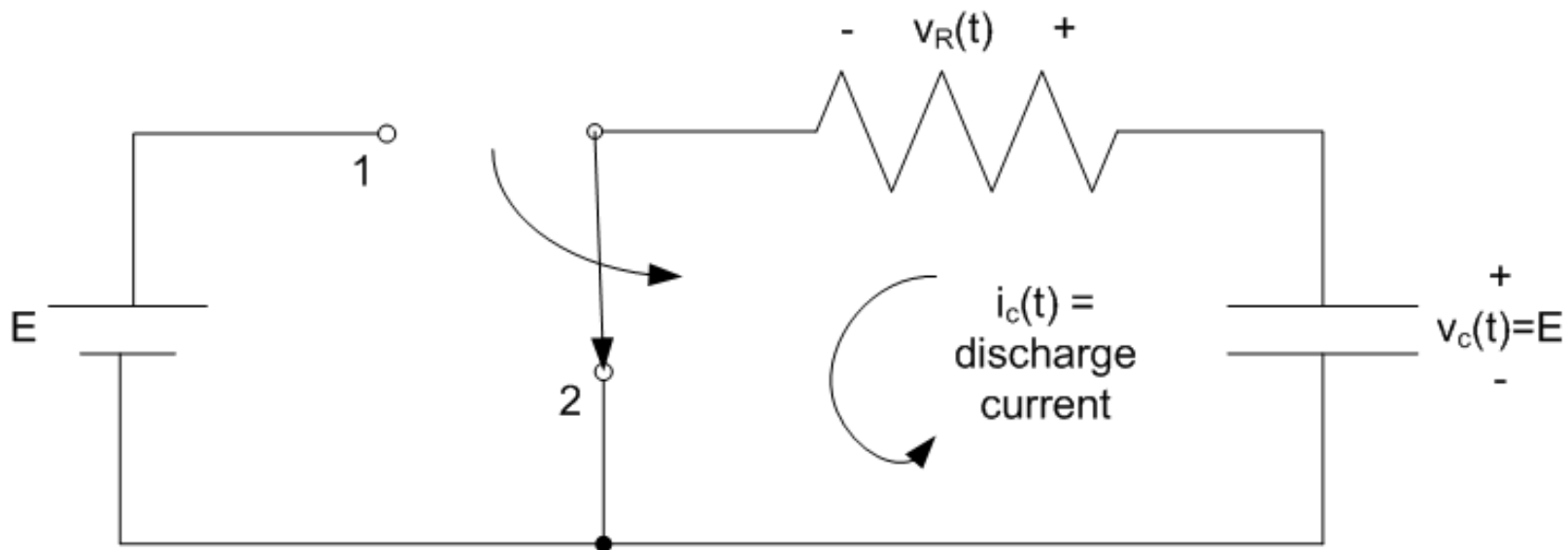If the capacitor is charged to the full battery voltage and then the switch is moved to position 2, the capacitor will begin to discharge at a rate sensitive to the same time constant, $\tau = RC$.



Discharging behaviour of a capacitor circuit

RC circuit: Discharge Phase

The voltage

$$v_c(t) = v_R(t)$$

$$v_c(t) = i_R(t) \cdot R$$

$$v_c(t) = R \left\{ -C \frac{dv_c(t)}{dt} \right\}$$

$$\therefore \frac{-1}{RC} \int_0^t dt = \int_0^t \frac{dv_c(t)}{v_c(t)}$$

$$\frac{-t}{RC} = [\ln v_c(t)]_0^t \leftarrow v_c(t) = E \text{ when } t = 0$$

$$\frac{-t}{RC} = \ln \frac{v_c(t)}{E}$$

$$\therefore v_c(t) = E e^{\frac{-t}{RC}}$$

$$i_c(t) = -C \frac{dv_c(t)}{dt} \\ = -C \cdot \left(\frac{-E}{RC} \right) e^{\frac{-t}{RC}}$$

$$i_c(t) = \frac{E}{R} e^{\frac{-t}{RC}}$$


$$v_R(t) = v_c(t) = E e^{\frac{-t}{RC}}$$

Charging current

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

$$i_c(t) = -C \frac{dv_c(t)}{dt}$$



discharging current

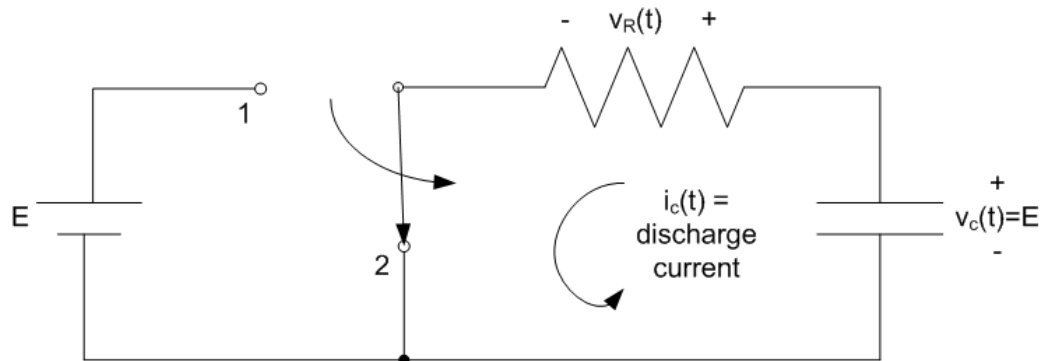

The complete discharge will occur for all practical purposes, in about five time constants.

RC circuit: Discharge Phase

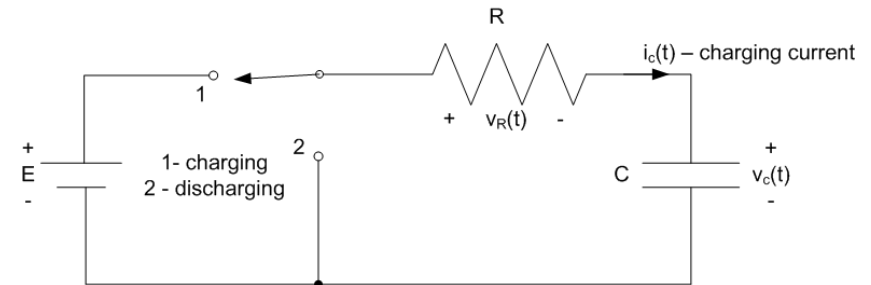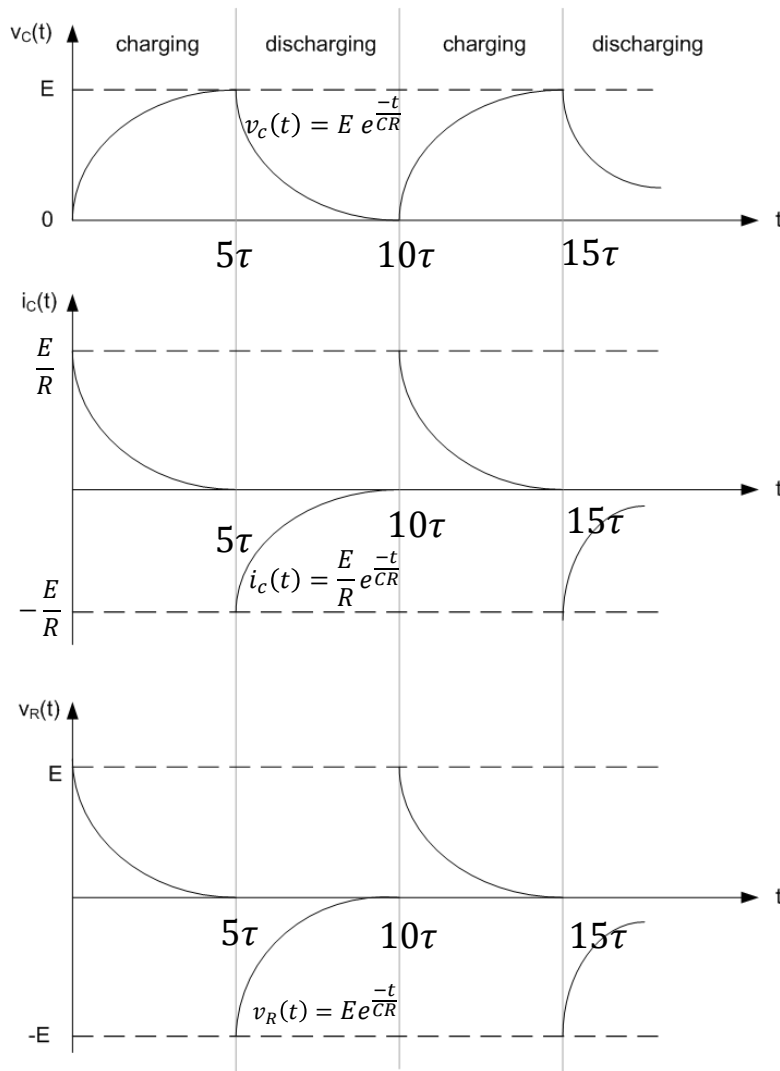
If the switch is moved to between terminals 1 and 2 every five time constants, sketch $v_c(t)$, $i_c(t)$, $v_R(t)$



- ✓ Since the polarity of $v_c(t)$ is the same for both the charging and discharging phases $v_c(t)$ is always above the t -axis.
- ✓ The current $i_c(t)$ reverse direction during the charging and discharging phase, producing a negative pulse for both the current and the voltage $v_R(t)$

Example

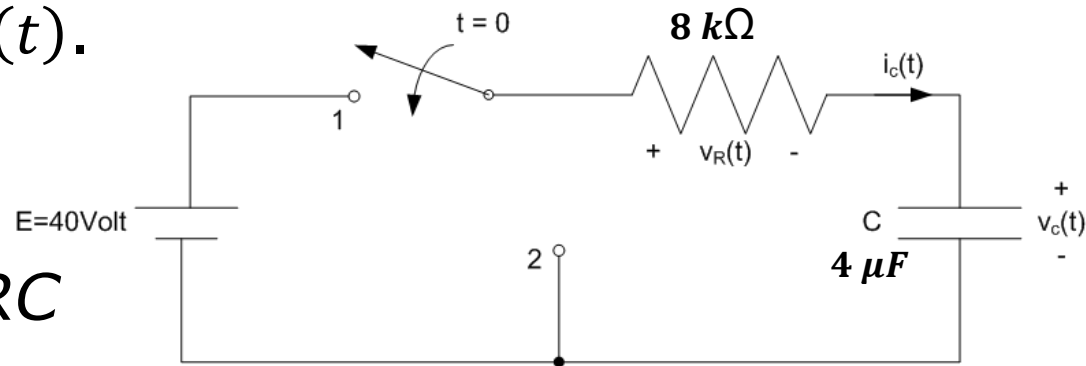(a) Find the mathematical expressions for the transient behaviour of $v_c(t)$, $i_c(t)$, $v_R(t)$ for the circuit below when the switch is moved to position 1. Plot the curves $v_c(t)$, $i_c(t)$, $v_R(t)$.



(a) Time constant (τ) = RC

$$\tau = 8 \times 10^3 \times 4 \times 10^{-6} = 32\text{ms}$$

$$v_c(t) = E \left[1 - e^{-\frac{t}{\tau}} \right] = 40 \left[1 - e^{-\frac{t}{(32 \times 10^{-3})}} \right]$$

$$i_c(t) = \frac{E}{R} e^{-\frac{t}{\tau}} = \frac{40}{8 \times 10^{-3}} e^{-\frac{t}{(32 \times 10^{-3})}}$$




$$v_R(t) = E e^{-\frac{t}{\tau}} = 40 e^{-\frac{t}{(32 \times 10^{-3})}}$$

Example

$$\begin{aligned}v_c(t) &= E[1 - e^{\frac{-t}{\tau}}] \\&= 40[1 - e^{\frac{-t}{(32 \times 10^{-3})}}]\end{aligned}$$


$$\begin{aligned}i_c(t) &= \frac{E}{R} e^{\frac{-t}{\tau}} \\&= \frac{40}{8 \times 10^{-3}} e^{-\frac{t}{(32 \times 10^{-3})}}\end{aligned}$$
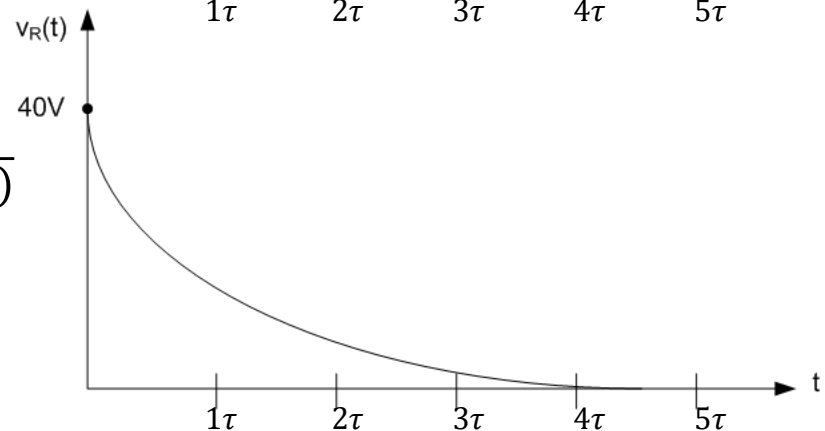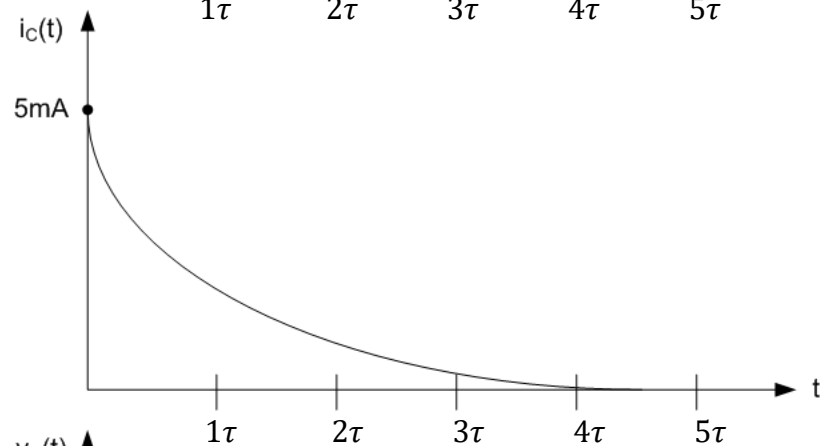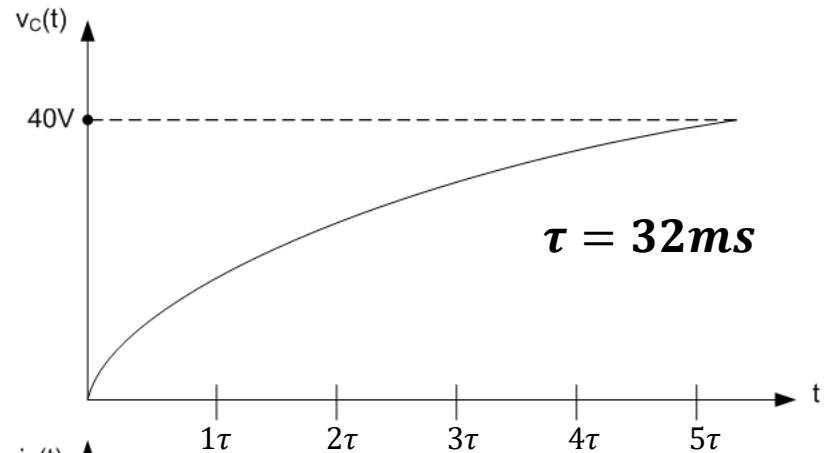
$$v_R(t) = E e^{-\frac{t}{\tau}} = 40 e^{-\frac{t}{(32 \times 10^{-3})}}$$



Example

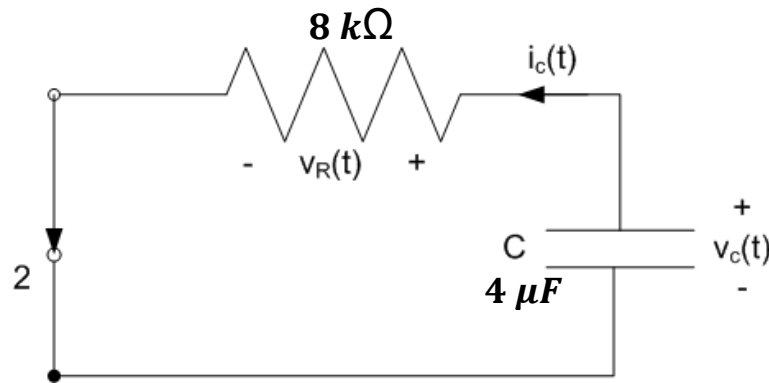(b) After $v_c(t)$ has reached its final value of 40V, the switch is thrown into position 2 (see diagram below) assume that when $t = 0$, the switch is moved to position 2. Plot the curves $v_c(t)$, $i_c(t)$, $v_R(t)$.



$$\tau = 32\text{ms}$$

$$v_c(t) = E e^{\frac{-t}{\tau}} = 40 e^{\frac{-t}{(32 \times 10^{-3})}} \quad v_R(t) = -E e^{\frac{-t}{\tau}} = -40 e^{\frac{-t}{(32 \times 10^{-3})}}$$


$$i_c(t) = -\frac{E}{R} e^{\frac{-t}{\tau}} = -(5 \times 10^{-3}) e^{\frac{-t}{(32 \times 10^{-3})}}$$

Example

$$v_c(t) = E e^{\frac{-t}{\tau}} = 40e^{\frac{-t}{(32 \times 10^{-3})}}$$

$$\begin{aligned} i_c(t) &= -\frac{E}{R} e^{\frac{-t}{\tau}} \\ &= -(5 \times 10^{-3}) e^{\frac{-t}{(32 \times 10^{-3})}} \end{aligned}$$


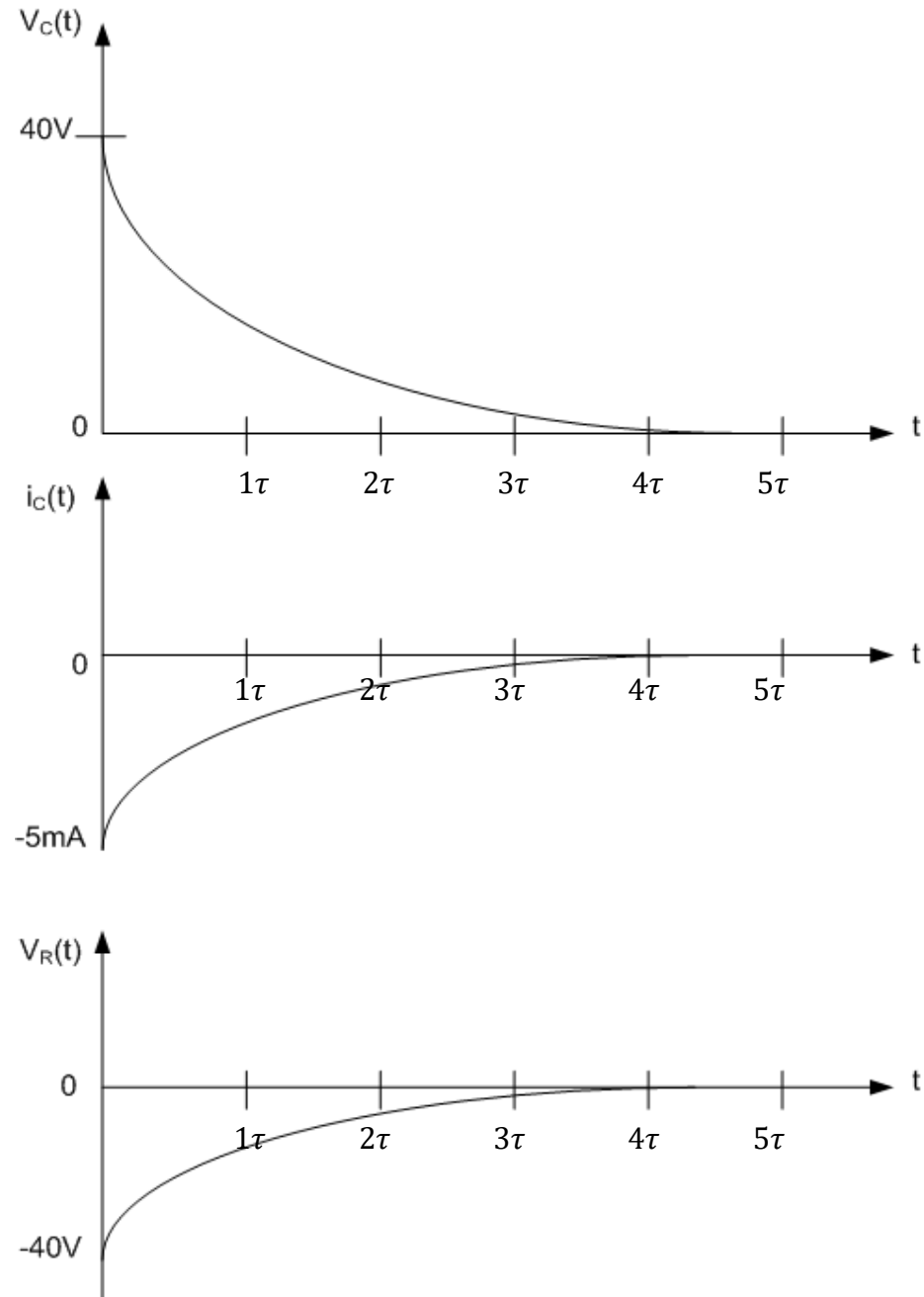
$$v_R(t) = -E e^{\frac{-t}{\tau}} = -40e^{\frac{-t}{(32 \times 10^{-3})}}$$



Initial Value

In the previous sections, it was assumed that the capacitor was uncharged before the switch was thrown (i.e. the initial charge in the capacitor = 0).

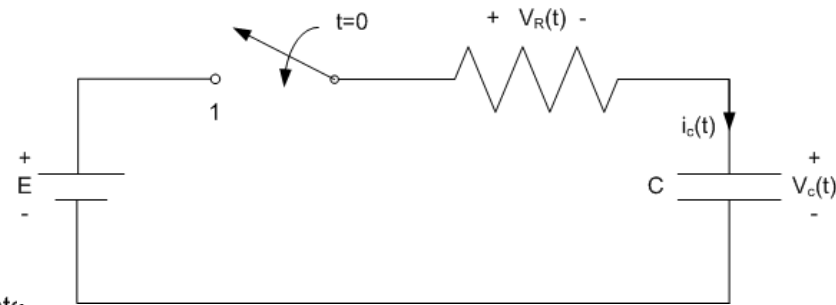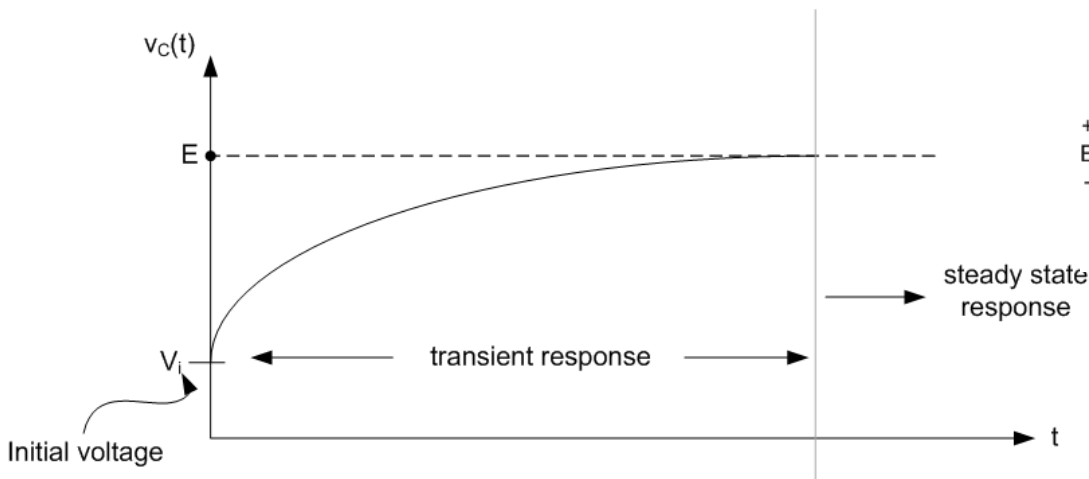We will now examine the effect of a charge (i.e. a voltage $V = \frac{Q}{C}$) on the plates at the instant the switch action takes place.



$$v_c(t) = V_i + (E - V_i)\left(1 - e^{-\frac{t}{\tau}}\right)$$


$$\therefore v_c(t) = E + (V_i - E) e^{-\frac{t}{\tau}}$$

If the capacitor is uncharged initially $V_i = 0$ then we get

$$v_c(t) = E\left(1 - e^{-\frac{t}{\tau}}\right)$$

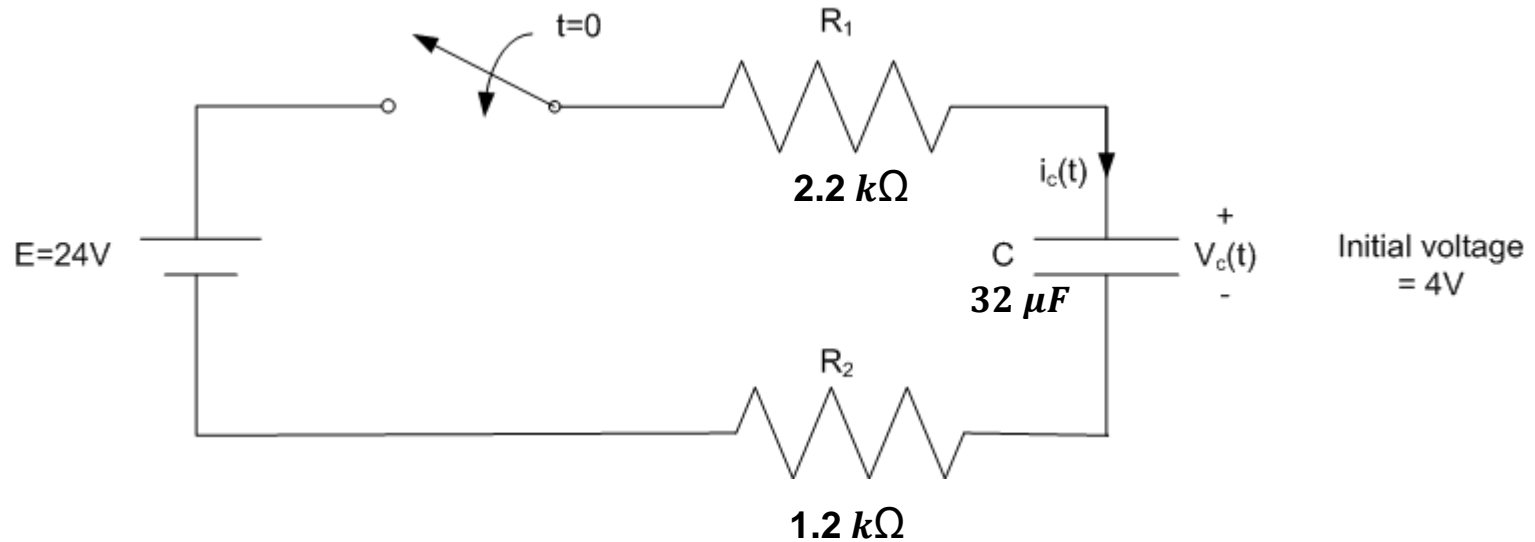Example

Suppose a capacitor has an initial voltage of 4V



- (a) Find the voltage $v_c(t)$ across the capacitor once the switch is closed
- (b) Find the current $i_c(t)$ during the transient period
- (c) Sketch $v_c(t)$ and $i_c(t)$

Example

(a) The time constant

$$\tau = (R_1 + R_2)C$$

$$= (2.2 + 1.2)\text{k}\Omega \times 3.3\mu\text{F}$$

$$= 11.22\text{ms and } 5\tau = 56.1\text{ms}$$

$$v_c(t) = E + (V_i - E) e^{-\frac{t}{\tau}}$$

$$= 24 + (4 - 24)e^{-\frac{t}{11.22\text{ms}}}$$

$$= 24 - 20e^{-\frac{t}{11.22 \times 10^{-3}}}$$

Example

(b) At the instant the switch is closed, the voltage across the resistive elements is $(24V - 4V) = 20V$.

∴ The peak current is $I_{max} = \frac{20}{R_1 + R_2} = 5.88mA$


$$\therefore i_c(t) = 5.88 \times 10^{-3} e^{-\frac{t}{11.22ms}}$$

Or use


$$i_c(t) = C \frac{dv_C}{dt}$$

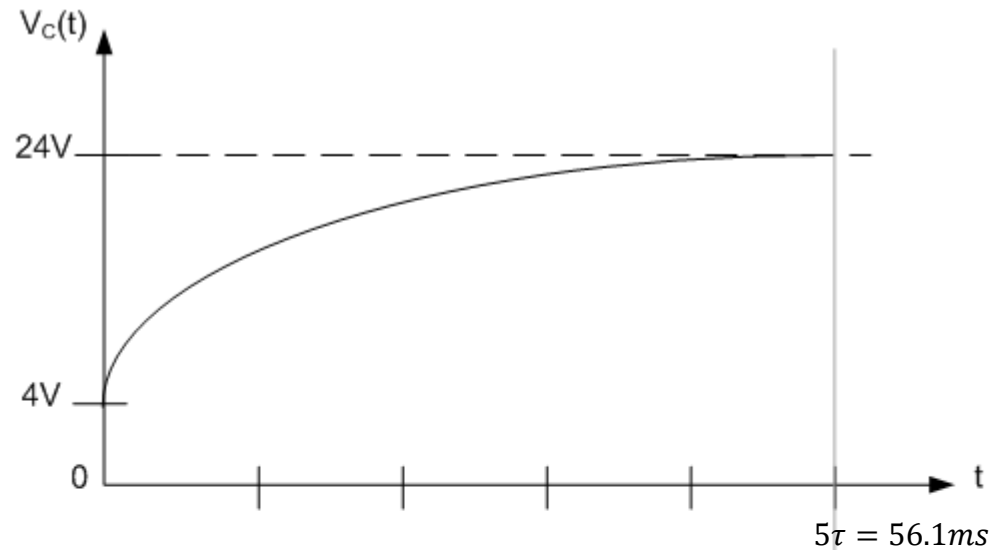Example

$$v_c(t) = 24 - 20e^{-\frac{t}{11.22 \times 10^{-3}}}$$



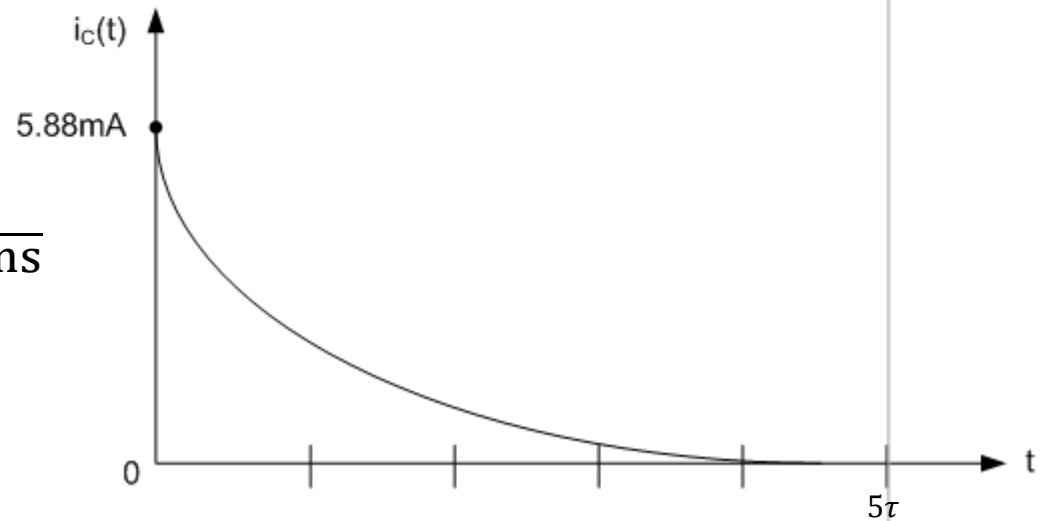
$$i_c(t) = 5.88 \times 10^{-3} e^{-\frac{t}{11.22\text{ms}}}$$



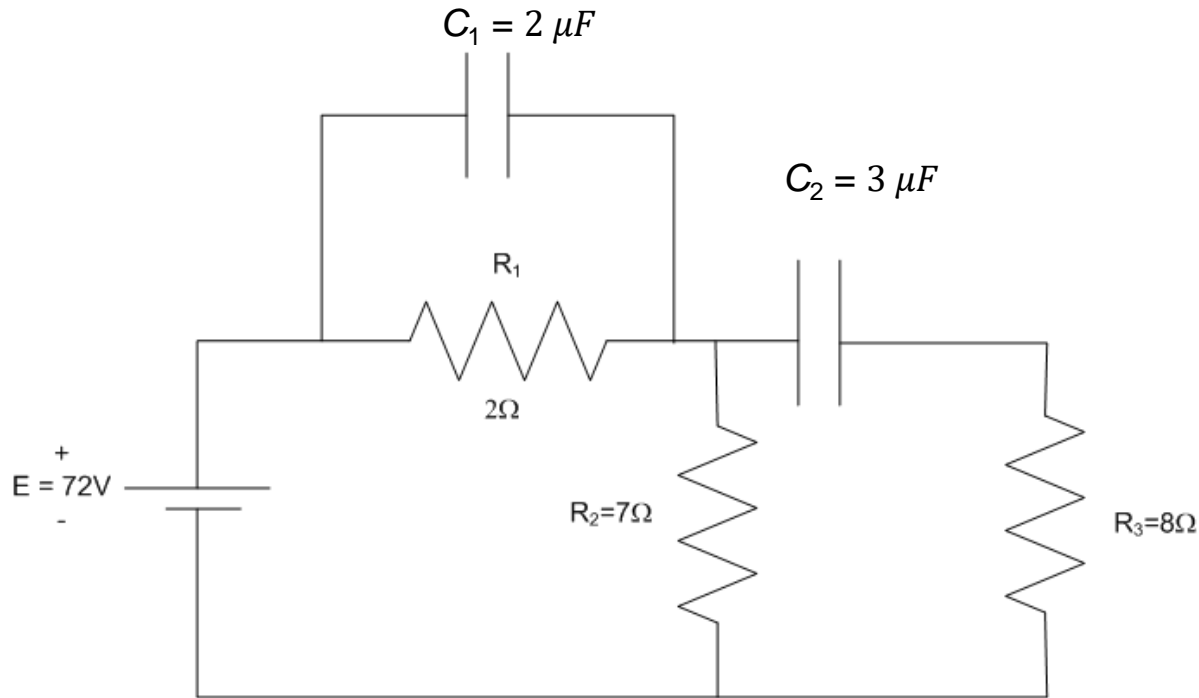
Example (Steady State)

Find the voltage across and charge on each capacitor of the circuit given below after each has charged up to its steady state value



Note: a capacitor can be replaced by an open-circuit equivalent once it has been charged up to its full value

Example (Steady State)

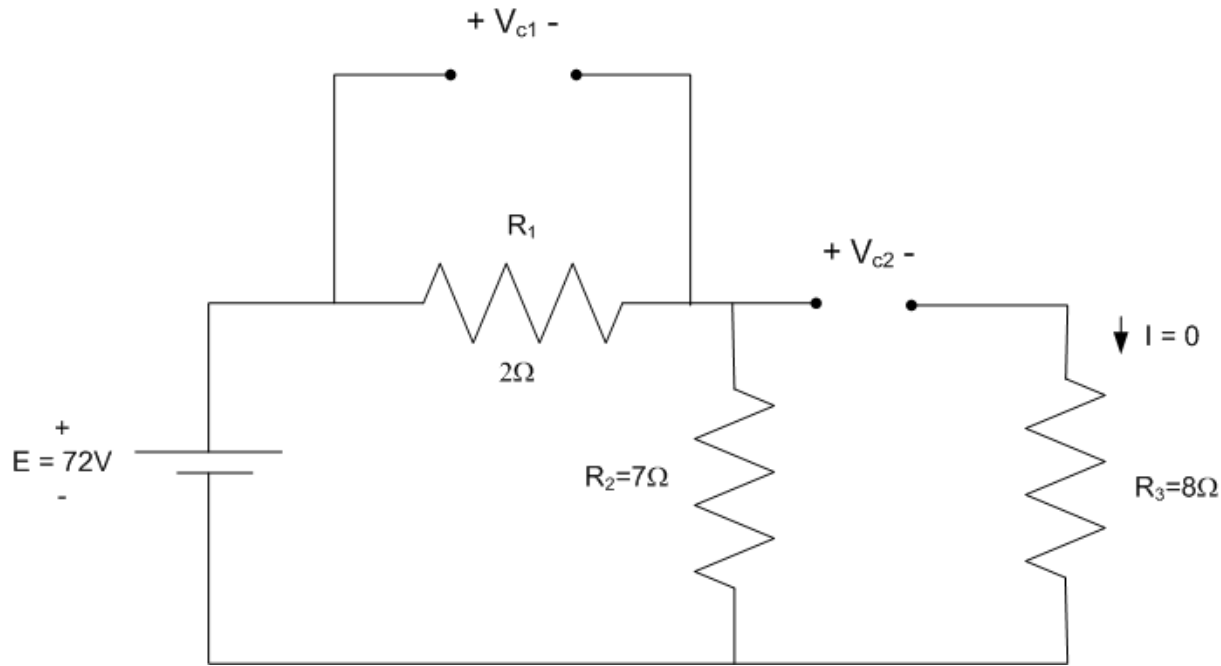

$$V_{c2} = \frac{7}{7 + 2} \times 72 = 56V$$


$$V_{c1} = \frac{2}{7 + 2} \times 72 = 16V$$

$$Q_1 = C_1 V_{c1} = (2 \times 10^{-6}F)(16V) = 32\mu C$$

$$Q_2 = C_2 V_{c2} = (3 \times 10^{-6}F)(56V) = 168\mu C$$

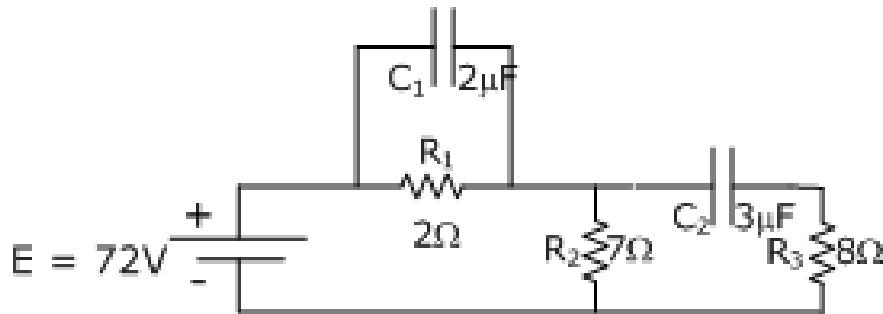Example

Also determine the energy stored by each capacitor.



$$V_{C_2} = 7 \times \frac{72}{7+2} = 56\text{V}$$


$$V_{C_1} = 2 \times \frac{72}{7+2} = 16\text{V}$$

For C_1 ,

$$w_C = \frac{1}{2} C_1 V_{C_1}^2 = \frac{1}{2} (2 \times 10^{-6} (16\text{V})^2) = 256\mu\text{J}$$

For C_2 ,
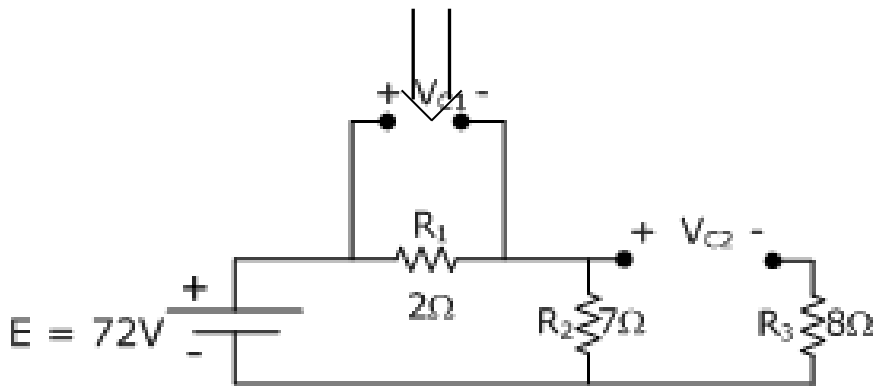
$$w_C = \frac{1}{2} C_2 V_{C_2}^2 = \frac{1}{2} (3 \times 10^{-6} (56\text{V})^2) = 4704\mu\text{J}$$



Reference: Introductory Circuit Analysis –
Boylestad, Prentice Hall, 2000

