




WEEK 9-2017

Verilog HDL-Shift Register

Register


- **An n - bit register consists of n flip-flops and is capable of storing n -bits of binary information.**
- **May also have combinational circuit that implements state transitions of the flip-flops.**
- **The flip-flops hold data and the combinational circuit determine the new or transformed data that will transfer to the flip-flops.**
- **A counter is special type of register that goes through a predetermined sequence of states.**
- **Useful for storing and manipulating information in digital computers.**

4- bit Register

  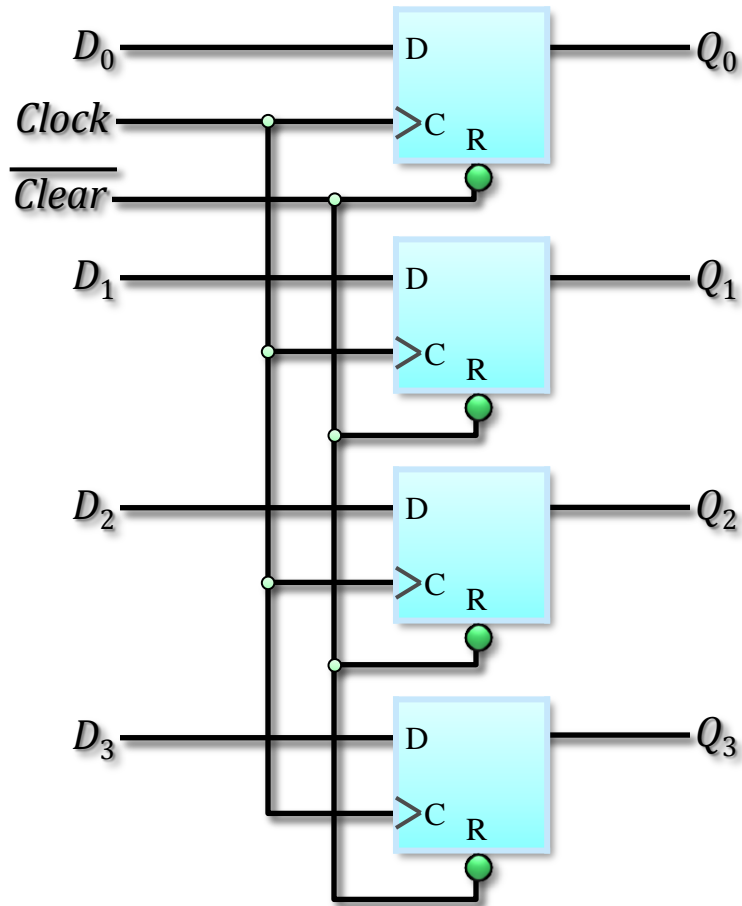

Shift-register

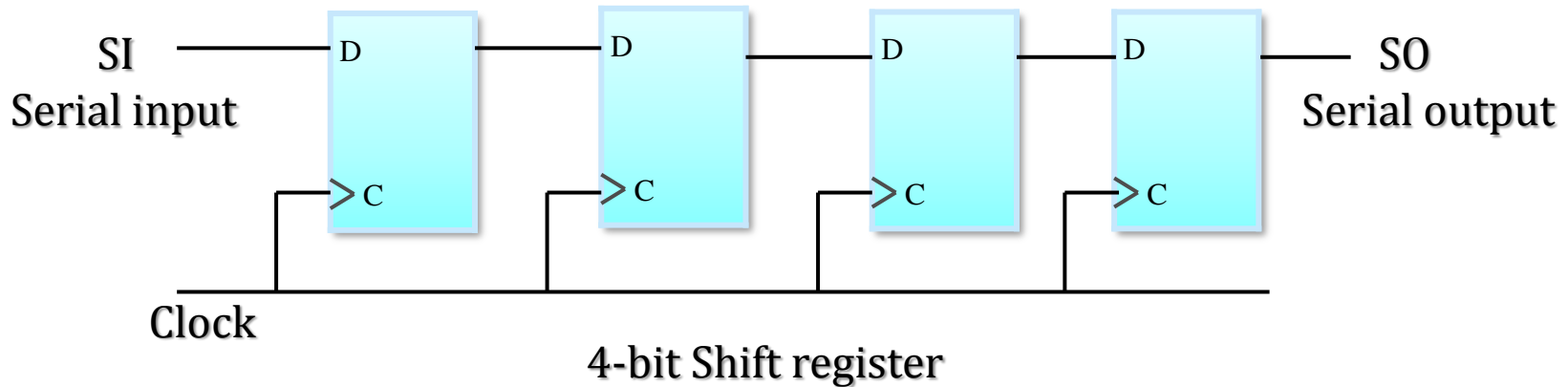
- **A register capable of shifting its stored bits laterally in one or both directions.**




- **Bidirectional shift register with parallel loading provides versatile operation.**

Bidirectional Shift Register

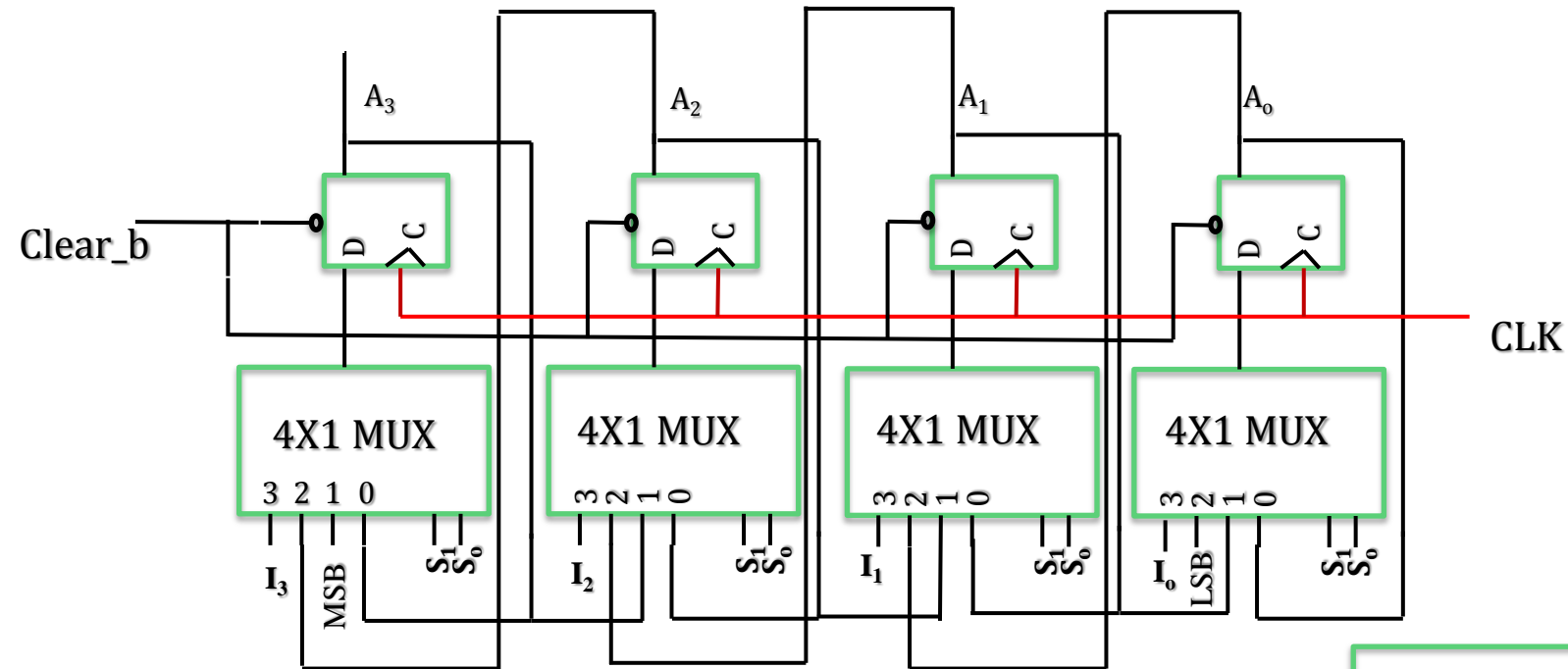- Capable of: left, right serial shift, parallel loading, and holding data.



Mode Control		Register Operation
S_1	S_0	
0	0	No change (Hold)
1	1	Parallel load
1	0	Shift left ($A_0 \leftarrow \text{LSB}$)
0	1	Shift right ($A_3 \leftarrow \text{MSB}$)

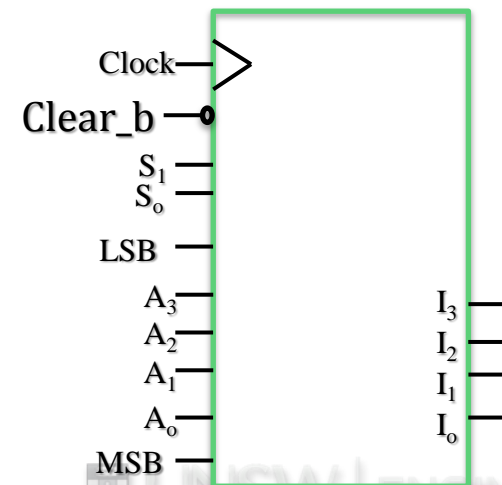


HDL for Shift Register

// Behavioral description of a 4-bit universal shift register

```
module Shift_Register_4_beh(  
  output reg   [3:0] A;          // Register output  
  input        [3:0] I;          //Parallel output  
  input        [1:0] S;          //Select inputs  
  input        MSB, LSB,        //Serial inputs  
                      CLK, Clear_b ); //Clock and Clear  
always @ (posedge CLK, negedge Clear_b)  
  if (Clear_b == 0) A <= 4'b0000;  
  else  
    case (S)  
      2'b00: A <= A;              // no change  
      2'b01: A <= {MSB, A[3:1]}; // Shift right  
      2'b10: A <= {A[2:0], LSB};  // Shift left  
      2'b11: A <= I;              //Parallel load of input  
    endcase  
  
endmodule
```

Bidirectional Shift Register

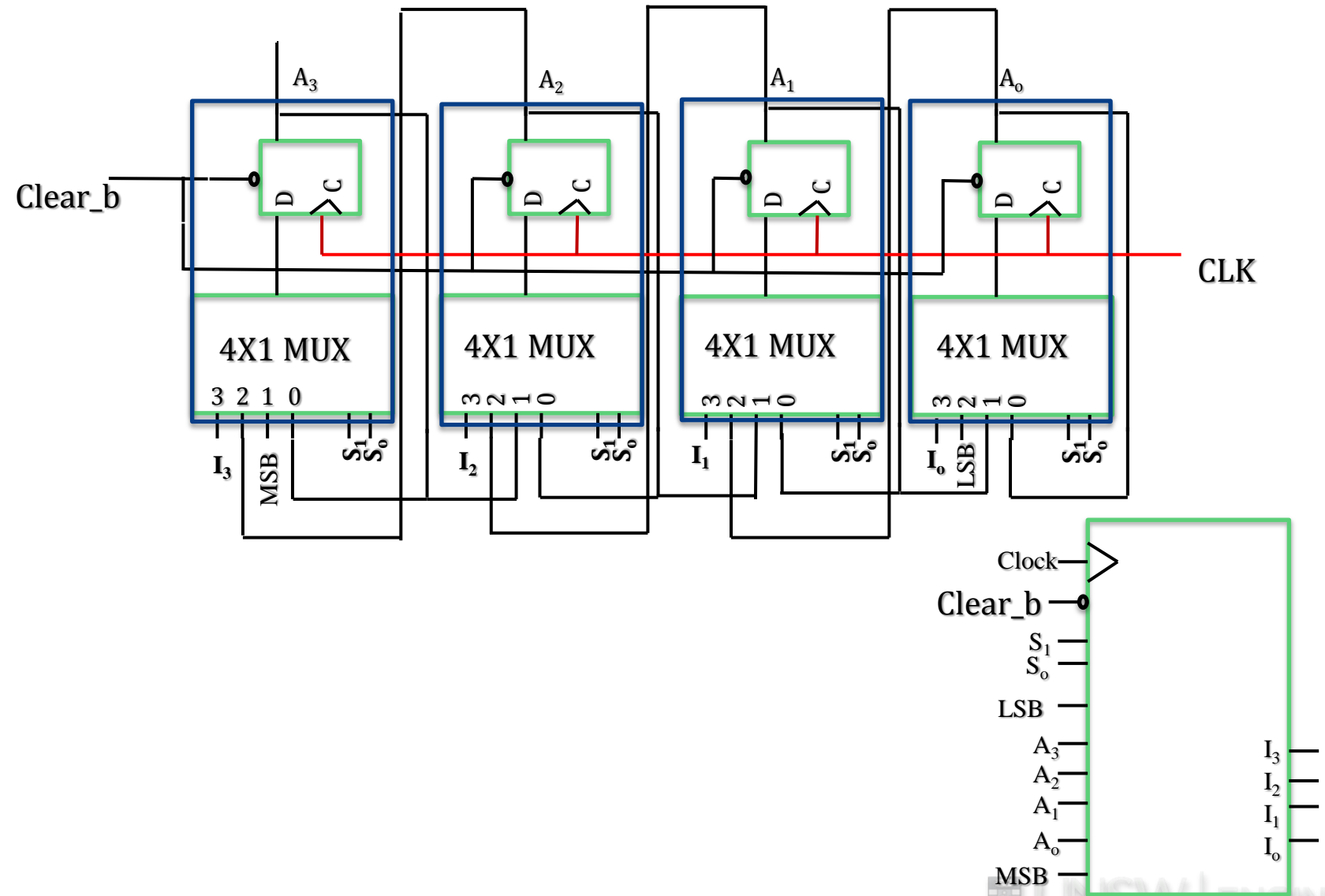

HDL for the Top Level Module

// Structural description of a 4-bit universal shift register

```
module Shift_Register_4_str(  
  output   [3:0] A;           // Register output  
  input    [3:0] I;           //Parallel output  
  input    [1:0] S;           //Select inputs  
  input    MSB, LSB,         //Serial inputs  
           CLK, Clear_b );    //Clock and Clear  
  
  // instantiate the four stages  
  
  stage ST0 (A[0], A[1], LSB, I[0], A[0], S, CLK, Clear_b);  
  stage ST1 (A[1], A[2], A[0], I[1], S, CLK, Clear_b);  
  stage ST2 (A[2], A[3], A[1], I[2], A[2], S, CLK, Clear_b);  
  stage ST3 (A[3], MSB, A[2], I[3], A[3], S, CLK, Clear_b);  
  
endmodule
```


HDL for the Next Top Level Module

// Declaring one stage of shift register

module stage(i0,i1,i2,i3,Q,select, CLK, Clr_b);

input i0, i1, i2, i3; // Register output

output Q; //Parallel output

input [1:0] select; //Select inputs

input CLK,Clr_b; //Serial inputs

wire mux_out; //Clock and Clear

// instantiate mux and flip-flop

mux_4_x_1 M0 (mux_out, i0, i1, i2, i3, select);

DFF M1 (Q,mux_out,CLK, Clr_b);

endmodule

Declaring the Low Level Modules

// Declaring 4x1 multiplexer

module Mux_4_x_1(mux_out,i0,i1,i2,i3,select);

input i0, i1, i2, i3;

output reg mux_out;

input [1:0] select;

Always @ (select, i0,i1,i2,i3)

case (select)

2'b00: mux_out = i0;

2'b01: mux_out = i1;

2'b10: mux_out = i2;

2'b11: mux_out = i3;

endcase

endmodule

// Declaring DFF

module DFF(Q,D,CLK, Clr_b);

output reg Q;

input D, CLK, Clr_b;

always @ (posedge CLK, negedge Clr_b)

if (Clr_b == 0) Q<= 1'b0;

else

Q <= D;

endmodule