



# Lecture 4: Kirchhoff's Laws

ELEC1111 Electrical and Telecommunications Engineering

Never Stand Still

Faculty of Engineering

School of Electrical Engineering and Telecommunications

# CONTENTS

- 1. Introduction**
- 2. Nodes, Branches, and Loops**
- 3. Kirchhoff's Current Law**
- 4. Kirchhoff's Voltage Law**
- 5. KVL & KCL Examples**

# 1. Introduction

## Why?


- ✓ To determine voltages and currents at any point in the circuit.

## How?

- ✓ To simplify the circuit as much as possible, e.g. series and parallel resistors, voltage division, sources in series & parallel, etc.
- ✓ Element laws, such as Ohm's law, relate terminal voltages and currents of individual elements.
- ✓ Circuit laws (Kirchhoff's laws) relate the voltages and currents shared at the interconnections of elements
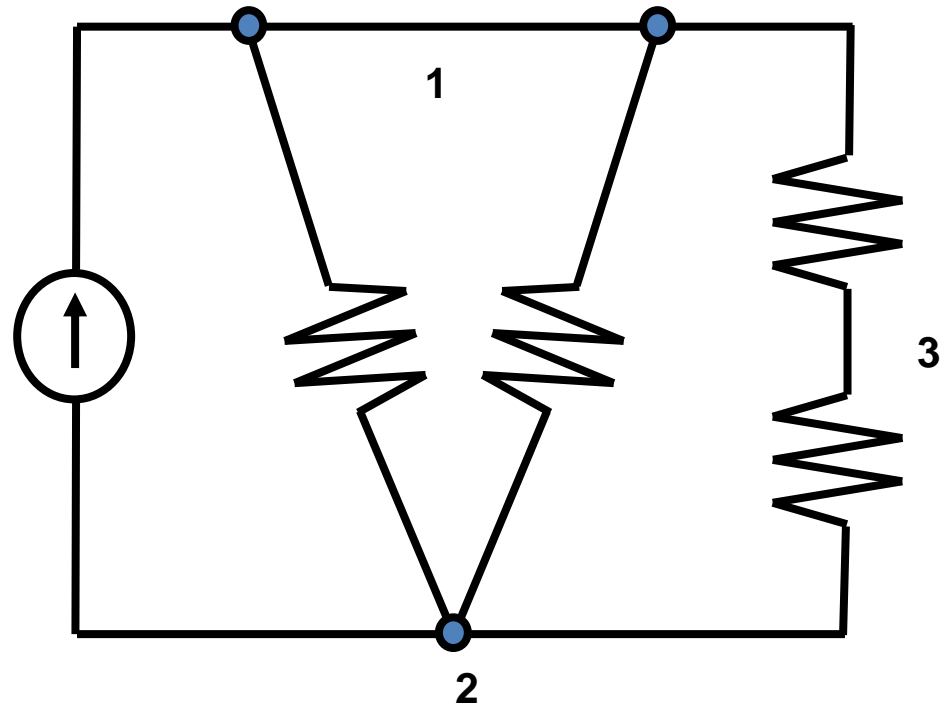
## 2. Nodes, Branches, Loops, Meshes


- ✓ A **branch** represents a single element such as a voltage source or a resistor. Wire connectors are assumed to have zero resistance.
- ✓ A **node** is the point of connection between two or more branches.
- ✓ All leads attached to a node are considered as part of that node.
- ✓ In moving from one node to another, if no node was encountered more than once, then the set of node and elements that we passed through is defined as a **path**.
- ✓ A **loop** is any closed path in a circuit.
- ✓ A **mesh** is a loop that contains no other loop.



A circuit containing 3 nodes and 5 branches


## 2. Nodes, Branches, Loops, Meshes

### Example

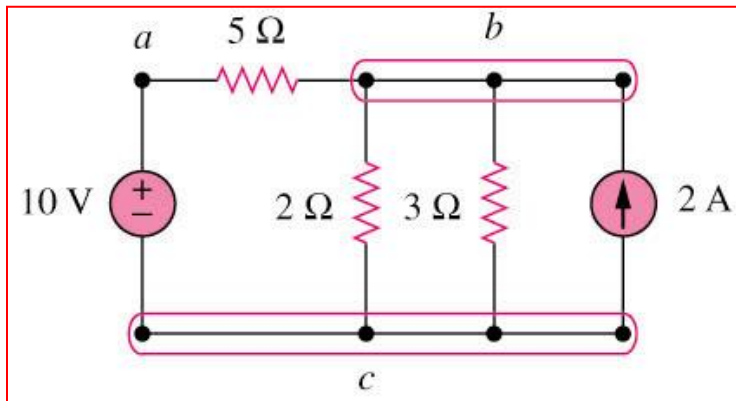

Original circuit


Nodes =  
Branches =  
Meshes =

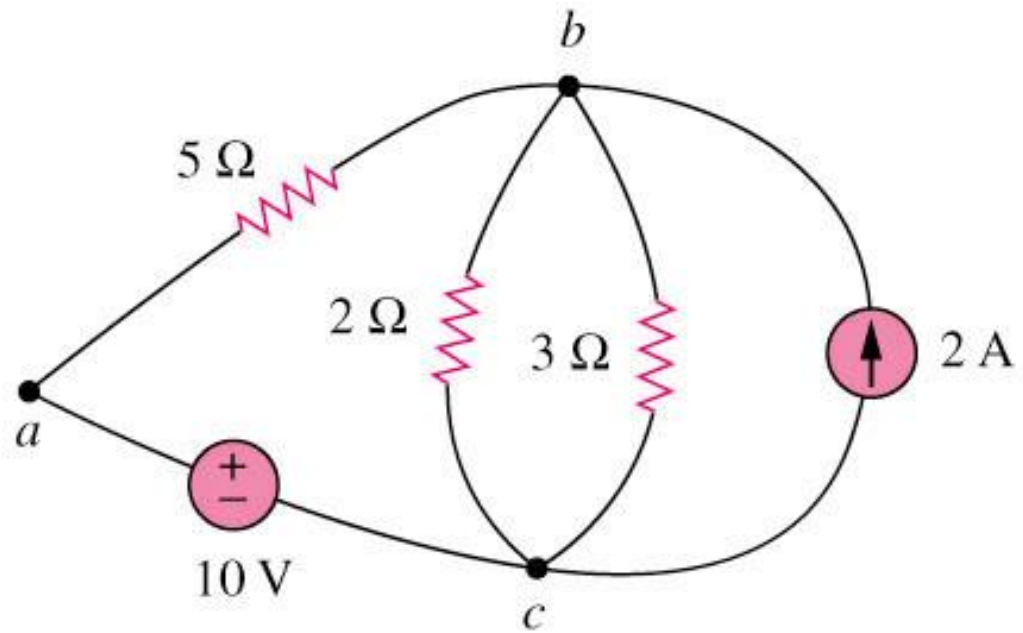

Equivalent circuit

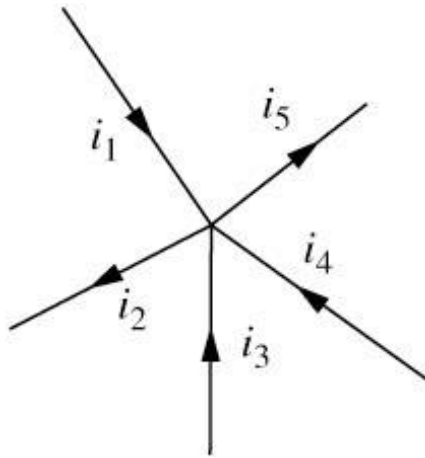
### 3. Kirchhoff's Current Law (KCL)

- ✓ **KCL:** *The algebraic sum of currents into a node (or closed boundary) at any instant is zero. (That is, charge cannot accumulate at a node)*



$$i_1 - i_2 + i_3 + i_4 - i_5 = 0$$


$$i_1 + i_3 + i_4 = i_2 + i_5$$

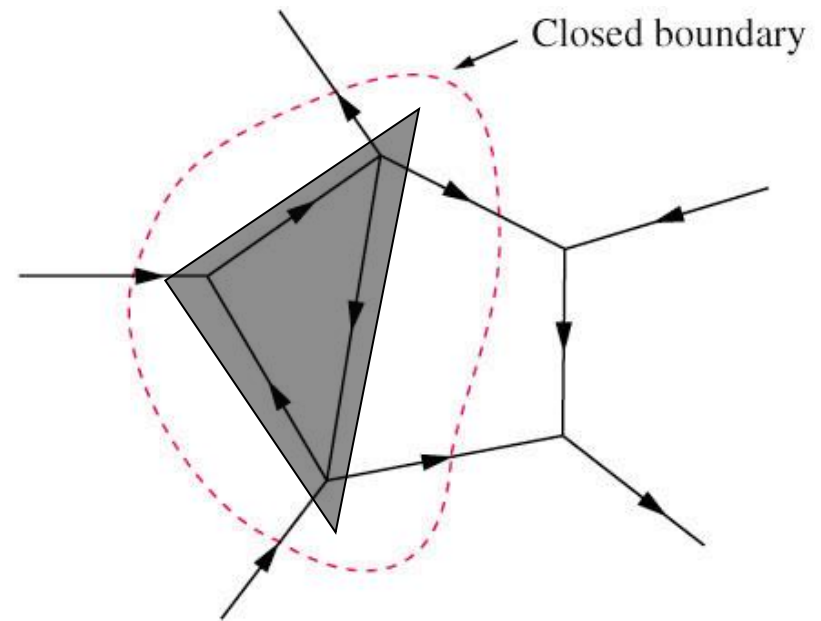

- ✓ **KCL** (restatement): *At any node (junction) in an [electrical circuit](#), the sum of [currents](#) flowing into that node is equal to the sum of currents flowing out of that node or equivalently*

### 3. Kirchhoff's Current Law (KCL)


#### Example

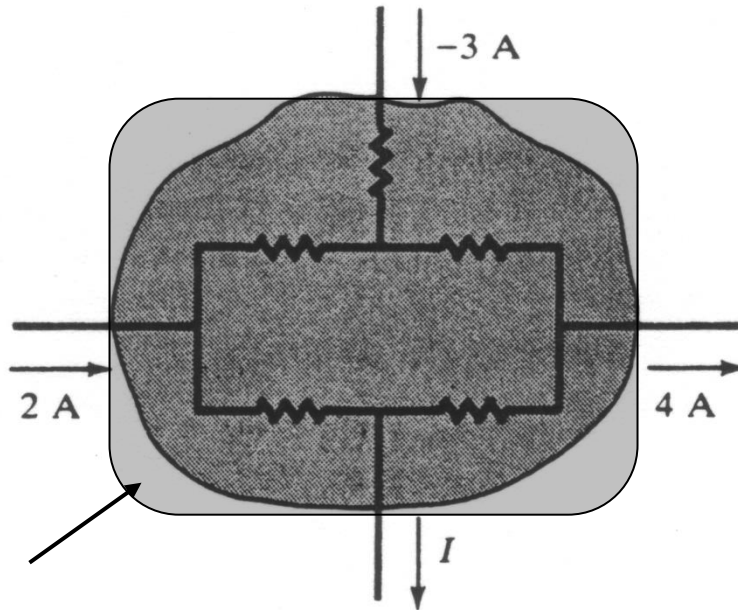

We can consider the whole enclosed area as one “node”.
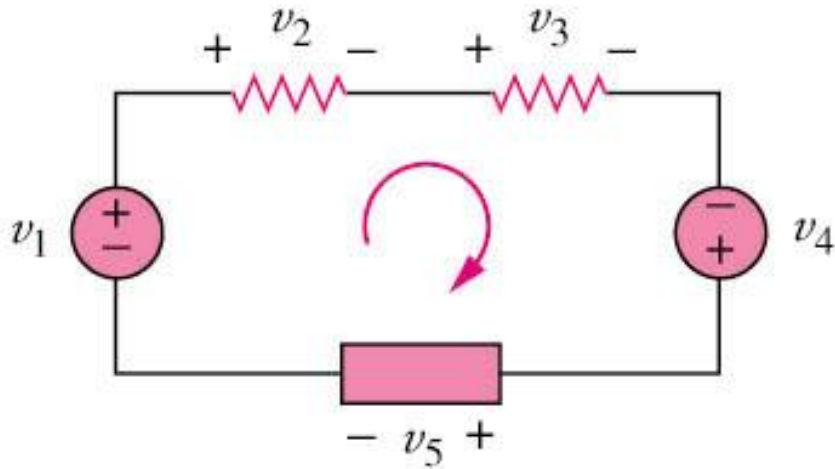
## 4. Kirchhoff's Voltage Law (KVL)

- ✓ **KVL:** *The algebraic sum of voltages around any closed path is zero.*
- ✓ **One method:** Move around the closed path in a clockwise direction and write down the voltage of each element using the sign on the first (or second) terminal encountered.



$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

$$v_1 + v_4 = v_2 + v_3 + v_5$$

- ✓ Total amount of energy gained per unit charge are equal to the amount of energy lost per unit charge (energy and charge are both conserved)
- ✓ Key – first label all the voltages and currents on the diagram




# 4. Kirchhoff's Voltage Law (KVL)

## The Single Loop Circuit

- ✓ **Circuit:** – circuits elements connected in series to form a single loop
- ✓ **What:-** determine the current, voltage (and power) associated with each element.
- ✓ **Steps:-**
  1. Assign current direction (e.g. clockwise)
  2. Label all voltages (prefer passive convention)
  3. Apply KVL
  4. Apply Ohm's law to resistors
  5. Solve for current
  6. Solve for  $v$ ,  $p$  for any element


# 4. Kirchhoff's Voltage Law (KVL)

## Example

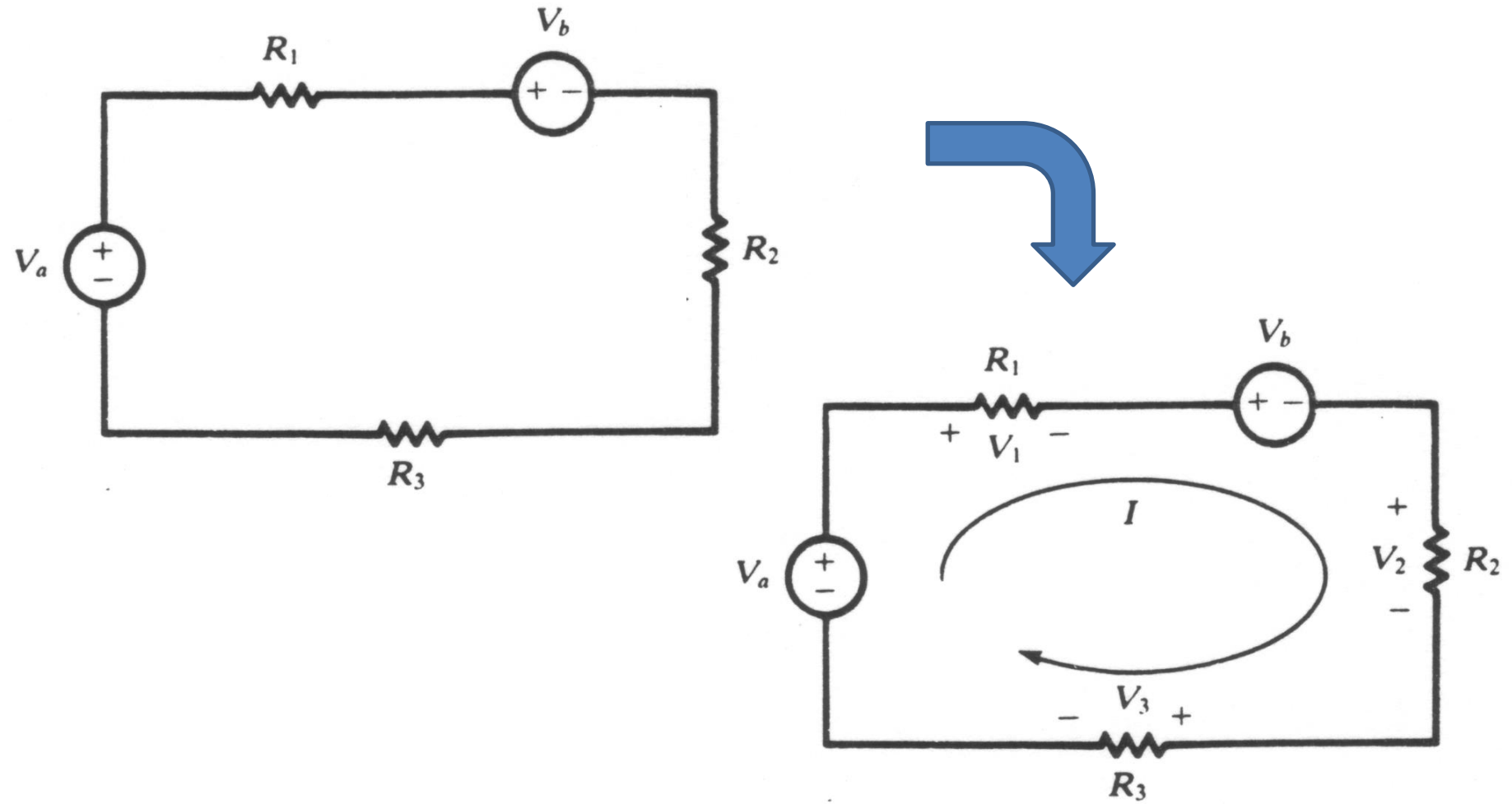

## 4. Kirchhoff's Voltage Law (KVL)

### Example

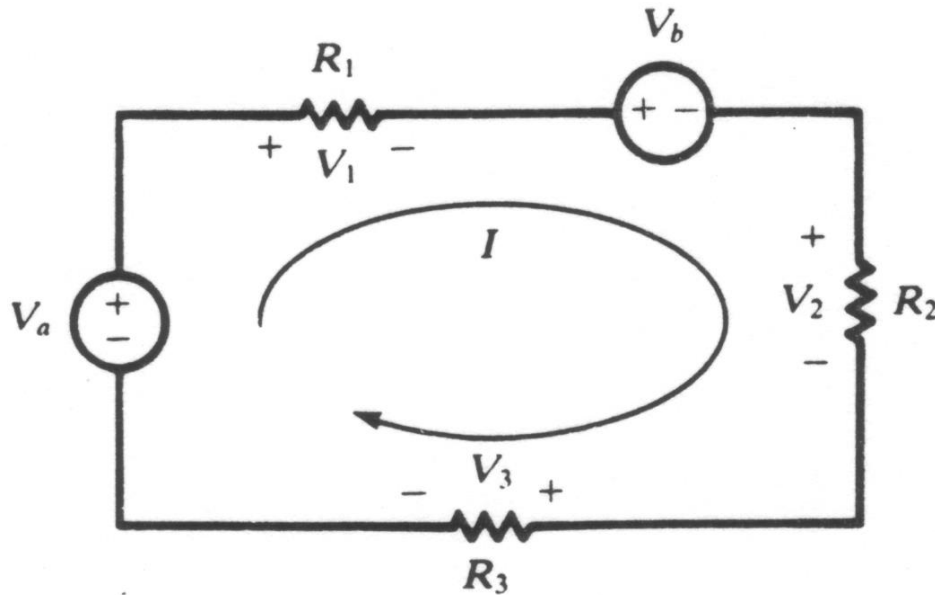

$$-V_a + V_1 + V_b + V_2 + V_3 = 0$$

$$V_1 = IR_1; V_2 = IR_2; V_3 = IR_3$$


$$V_a - V_b = I(R_1 + R_2 + R_3)$$

$$I = \frac{V_a - V_b}{R_1 + R_2 + R_3}$$

Voltage & Power?


# 5. KVL & KCL Examples

## Example 1

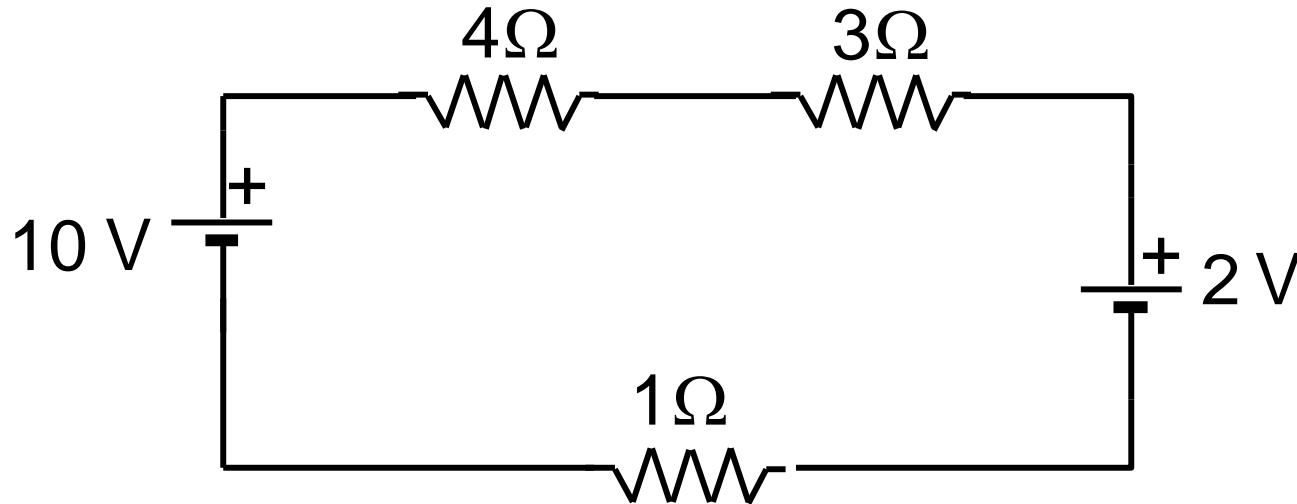


## 5. KVL & KCL Examples

### Example 2

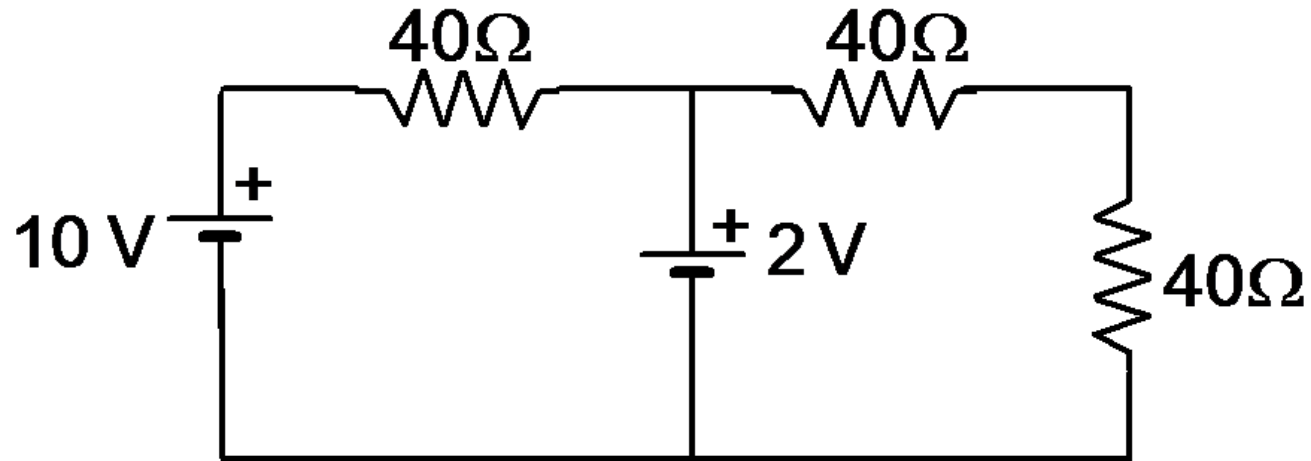


# 5. KVL & KCL Examples

## Example 3

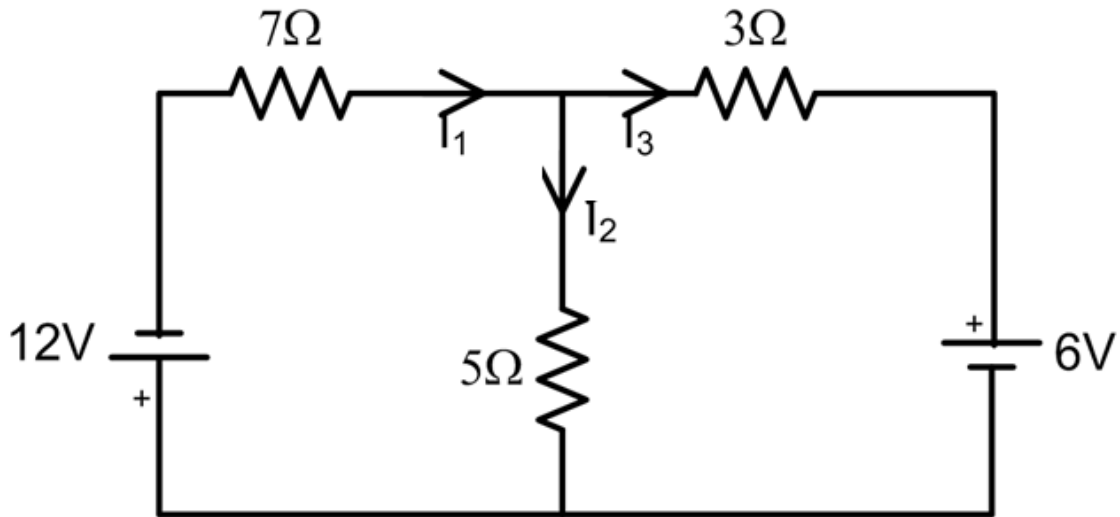


# 5. KVL & KCL Examples

## Example 3

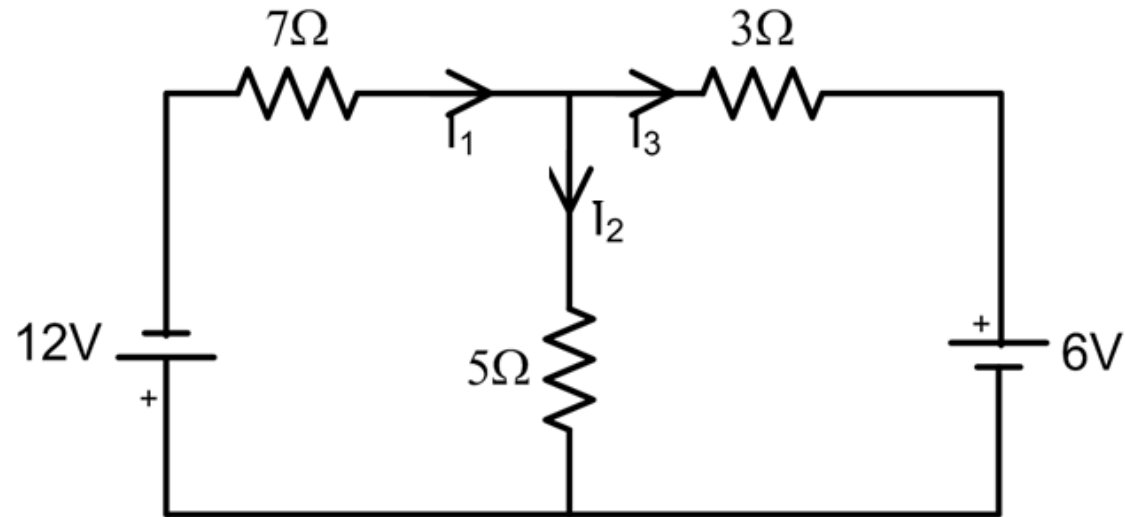

## 5. KVL & KCL Examples

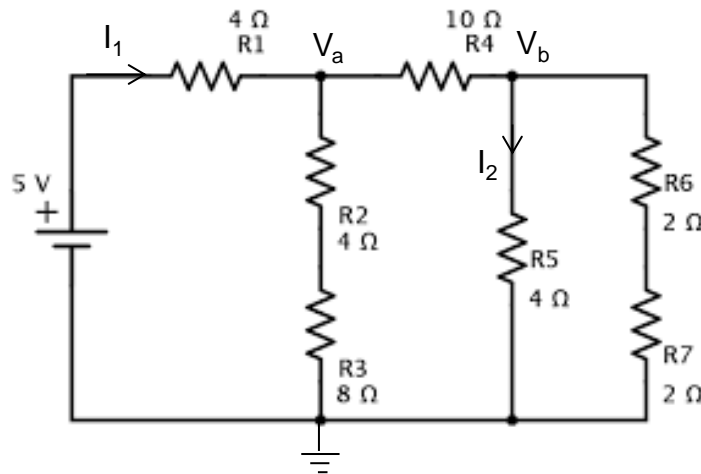Example 4: In the following circuit, find the value of  $I_1$ ,  $I_2$ ,  $V_a$ ,  $V_b$  and validate the power conservation condition of the circuit.





## 5. KVL & KCL Examples

Example 4: In the following circuits, find the resistance  $R_{AB}$  between A and B.

Figure 1

All resistors  $500\ \Omega$

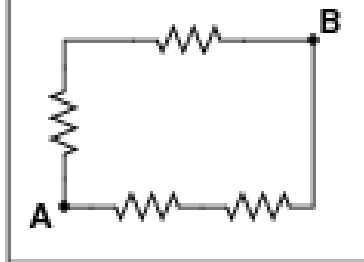


Figure 2

All resistors  $1\ \text{k}\Omega$


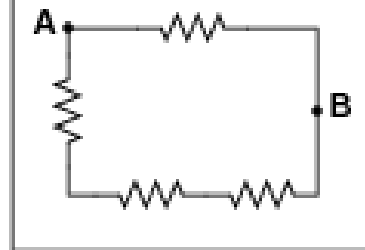


Figure 3

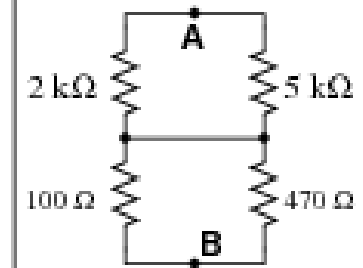

## 5. KVL & KCL Examples

Example 4 (cont.): In the following circuits, find the resistance  $R_{AB}$  between A and B.

Figure 4

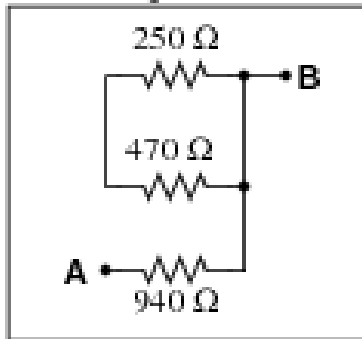


Figure 5



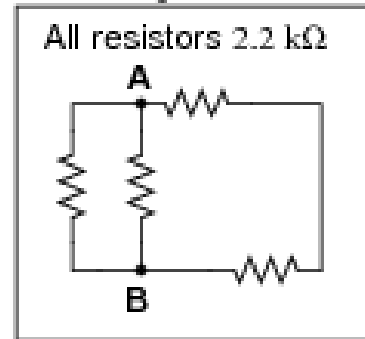


Figure 6

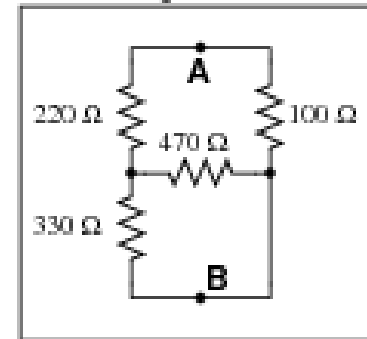


## 5. KVL & KCL Examples

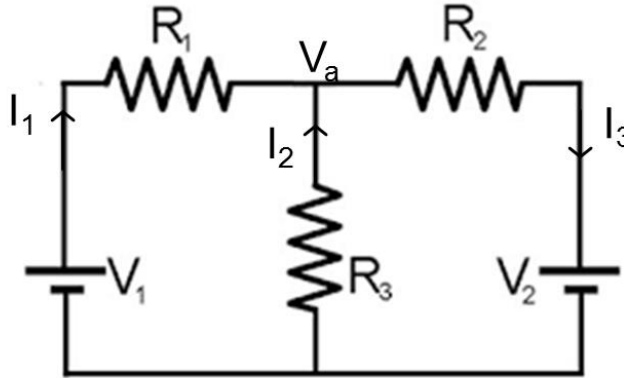Example 5: In the following circuit,  $V_1=10\text{V}$ ,  $V_2=5\text{V}$ ,  $R_1=2\Omega$ ,  $R_2=R_3=5\Omega$ , find currents  $I_1$ ,  $I_2$ ,  $I_3$  and voltage  $V_a$ . Validate the power conservation condition.



## 5. KVL & KCL Examples

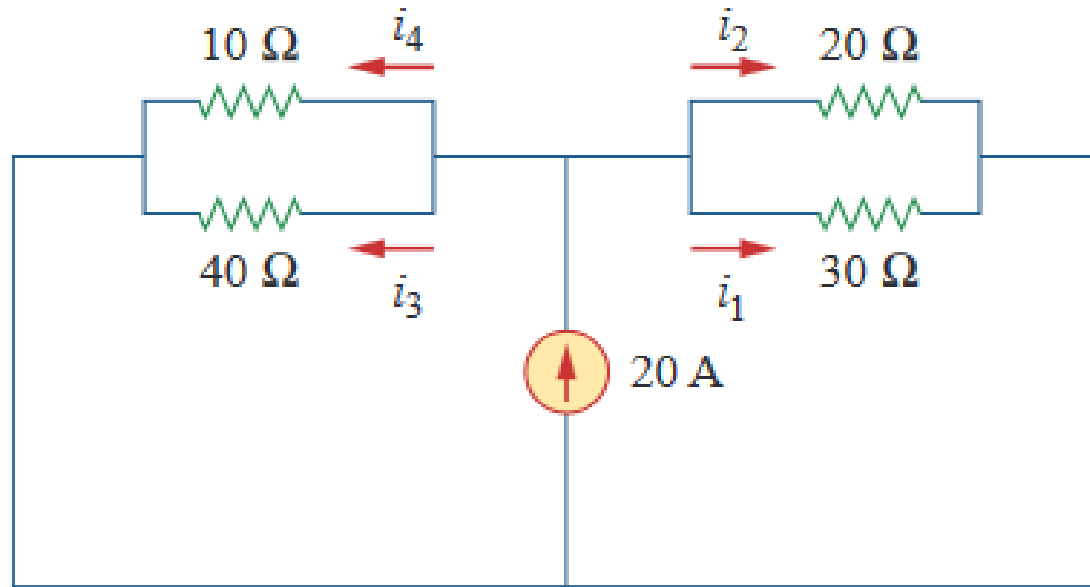
Example 6: Find the current  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$  in the following circuit



From “*Fundamentals of Electric Circuits*”, Alexander and Sadiku, McGraw-Hill

## 5. KVL & KCL Examples

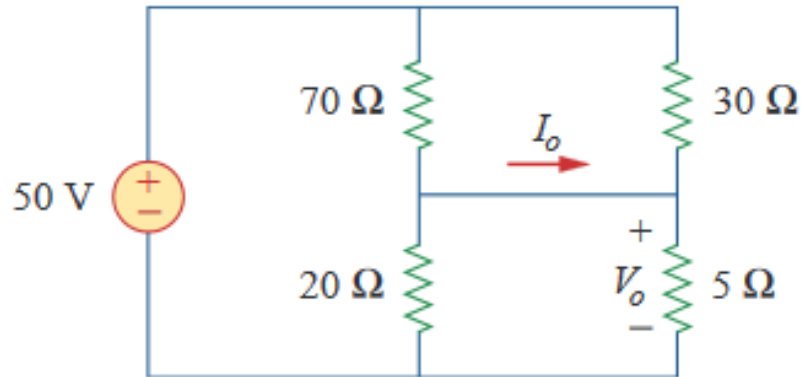
Example 7: Calculate  $V_o$  and  $I_o$  in the below circuit



From “*Fundamentals of Electric Circuits*”, Alexander and Sadiku, McGraw-Hill

## 5. KVL & KCL Examples

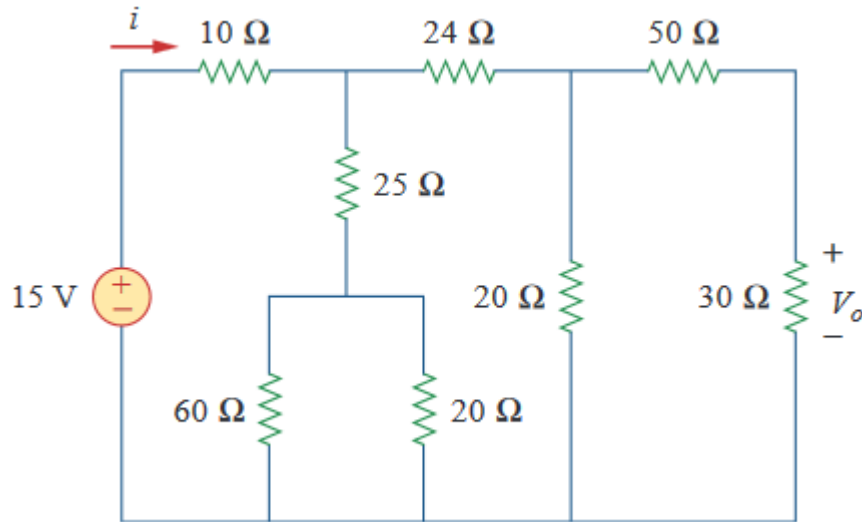
Example 8: Calculate  $i$  and  $V_o$  in the below circuit



From “*Fundamentals of Electric Circuits*”, Alexander and Sadiku, McGraw-Hill

## 5. KVL & KCL Examples

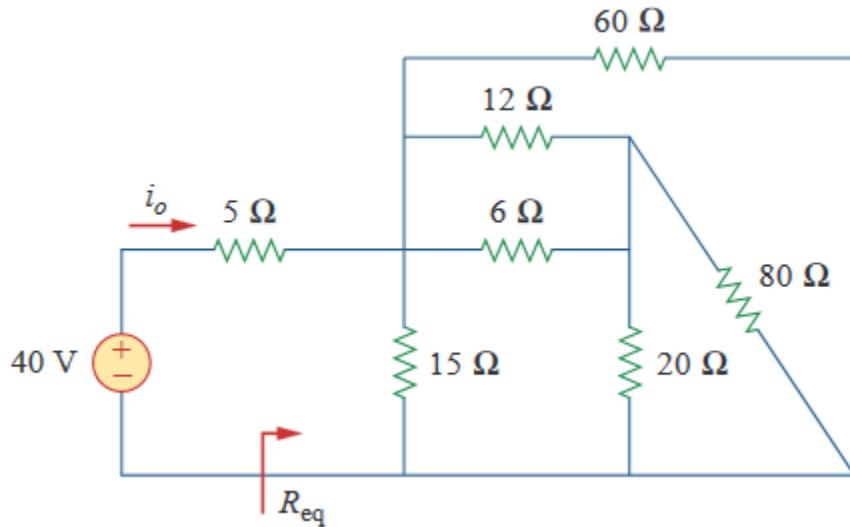Example 8: Find  $R_{eq}$  and  $i_o$  in the following circuit



From “*Fundamentals of Electric Circuits*”, Alexander and Sadiku, McGraw-Hill