

**WEEK 6-2017**

# Synchronous Sequential Circuit II



# Characteristic Tables

- A characteristic table defines the logical properties of a flip-flop by describing its operation in tabular form.
- It defines the next state as a function of the inputs and the presents state.
- The next state is the state of the flip-flop after the clock transition and denoted by  $Q(t+1)$ .
- The present state is the state of the flip-flop immediately before the clock edge and denoted by  $Q(t)$ .

# Characteristic Tables

J	K	Q (t+1)
0	0	
0	1	
1	0	
1	1	


D	Q (t+1)
0	
1	

T	Q (t+1)
0	
1	

# Characteristic Equations

Q	J	K	Q (t+1)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


$Q(t+1)$ :

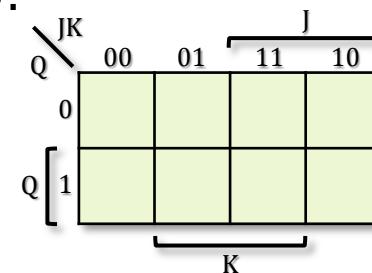

# Characteristic Equations


Q	D	Q (t+1)
0	0	
0	1	
1	0	
1	1	

$Q(t+1):$

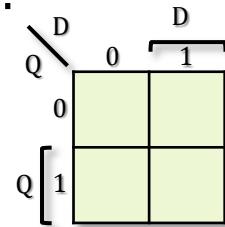


Q	T	Q (t+1)
0	0	
0	1	
1	0	
1	1	

$Q(t+1):$

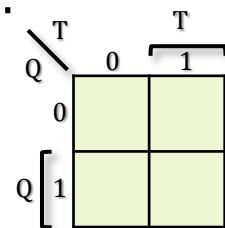
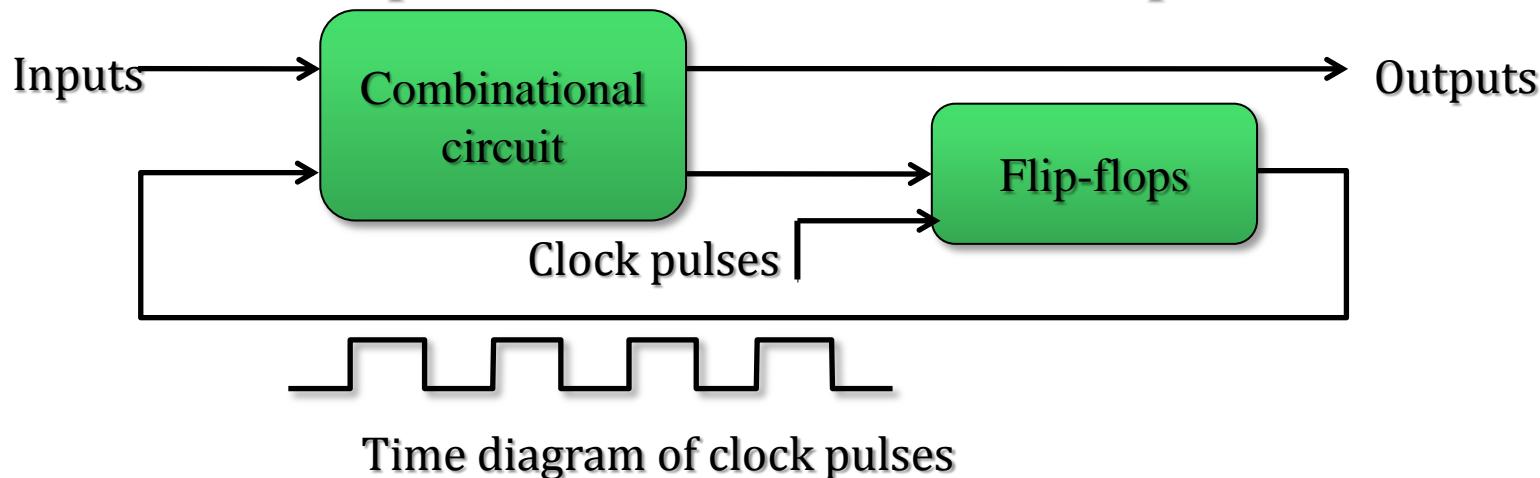
# Analysis of clocked Sequential Circuit

- The behavior of a clocked sequential circuit is determined from the inputs, internal states and outputs.




- The outputs and the next state are both the function of the inputs and the present state.
- Analysis of sequential circuit consists of obtaining a table or a diagram for the time sequence of inputs, internal states and outputs.
- Boolean expressions can be used to describe the behavior of the sequential circuit. In this case, it should include the necessary time sequence

# Analysis of clocked Sequential Circuit

- State equation, state table and state diagram will be used to describe the behavior of any clocked sequential circuit.

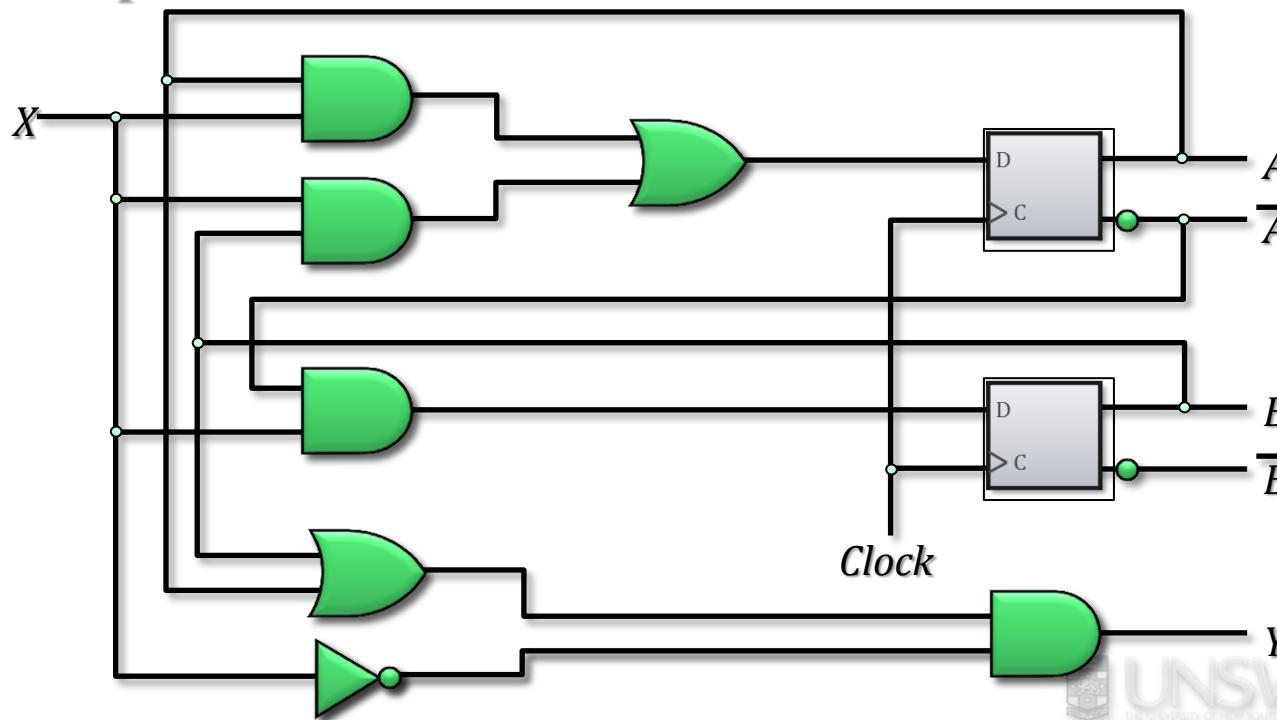
## State Equations (Transition Equation):

- A state equation (transition equation) specifies the next state as a Boolean function of the present state and inputs.



# State Equations

State Equations (Transition Equation):

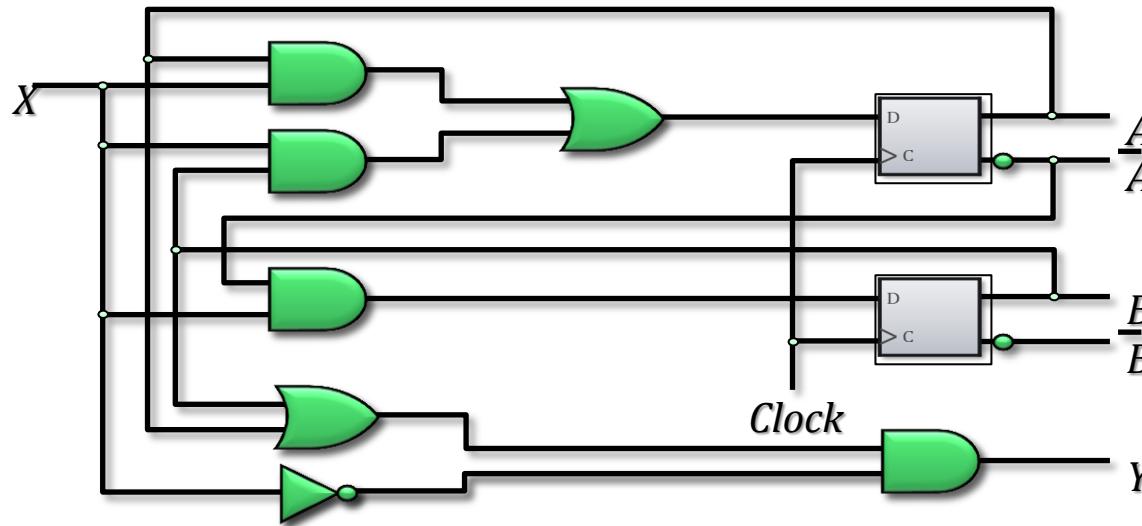

Since the D input of a flip-flop determines the value of the next state (i.e, the state reached after the clock transition)


$$A(t+1) = \bar{A}(t)x(t) + B(t)\bar{x}(t)$$
$$B(t+1) = \bar{A}(t)x(t)$$

The present-state value of the output can be expressed algebraically as

$$Y(t) = [A(t) + B(t)]\bar{x}(t)$$

# State Equations

State Equations (Transition Equation):

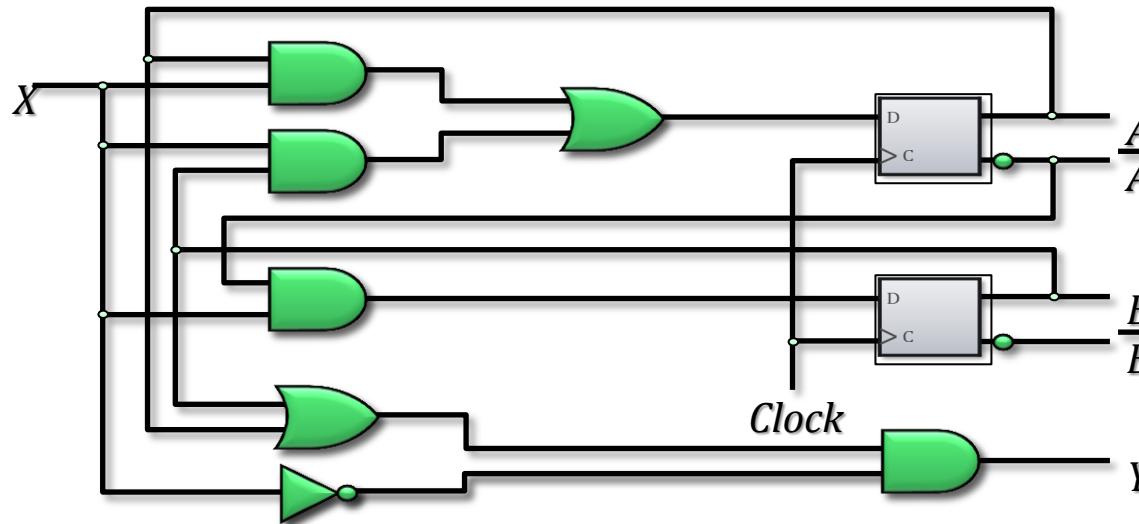

Since all variables in the Boolean expressions are a function of the present state, the designation of ( $t$ ) after each variable can be omitted

$$A(t+1) = Ax + Bx$$
$$B(t+1) = \bar{A}x$$

The present-state value of the output can be expressed algebraically as

$$Y(t) = [A + B]\bar{x}$$


# State table

**State table (Transition table):**

- It is possible to enumerate the time sequences of inputs, outputs and states of the sequential circuit using state table (transition table)
- The table consists of four sections labelled present state, input, next state and output.
- The derivation of a state table requires listing all possible binary combinations of present states and inputs.
- The next-states and the output values are then determined from the logic diagram or state equations for each possible binary combination.

# State table

State table (transition table):

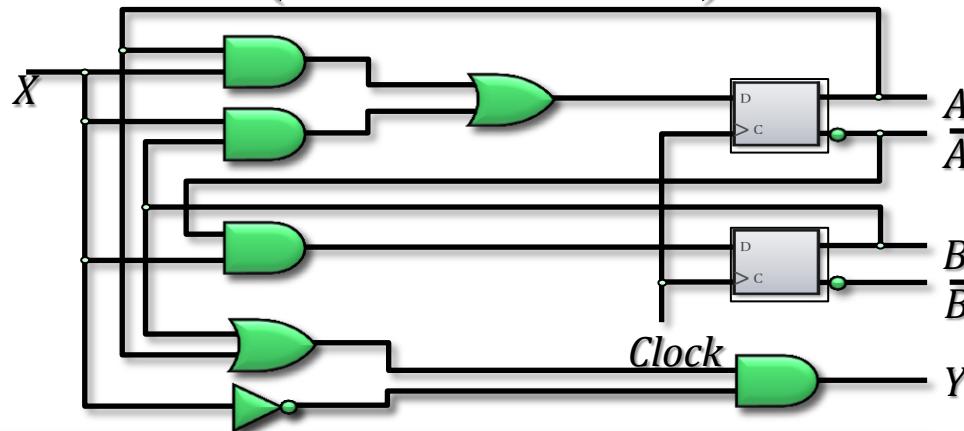

Present state		Input	Next state		Output
A	B	X	A	B	Y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

$$\begin{aligned}A(t+1) &= Ax + Bx \\B(t+1) &= \bar{A}x \\Y(t) &= [A + B]\bar{x}\end{aligned}$$

# State table

State table (transition table):

- The state transition may be conveniently expressed in a slightly different form having only three sections: present state, next state and output.

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
A B	A	B	A	B
0 0	0	0	0	1
0 1				
1 0				
1 1				

$$\begin{aligned}A(t+1) &= Ax + Bx \\B(t+1) &= \bar{A}x \\Y(t) &= [A + B]\bar{x}\end{aligned}$$


# State diagram

- The information available in state tables can be represented graphically in the form of a state diagram.
- In a state diagram, a state is indicated by a circle and the transitions between the states are represented by directed lines connecting the circles.
- The directed lines are labeled with two binary numbers separated by a slash. The first binary number is for the input value and the second number shows the output value for the given input value during the present state which is represented by a circle from which the directed line emanates.

# State diagram

- The state diagram for the following state table can be drawn as:

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
A B	A	B	A	B
0 0	0	0	0	1
0 1	0	0	1	1
1 0	0	0	1	0
1 1	0	0	1	0

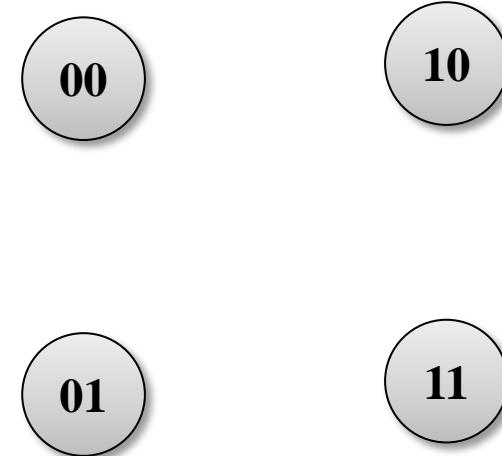

- The same information is conveyed by both state diagram and state table.
- State diagrams provides pictorial representation that is easier for human representation.

# State and output time sequence


- Find state and output time sequence for input sequence of 010100110 assuming the sequential is initially in state 00

Clk											
X	0	1	0	1	0	0	1	1	0	0	
A	0	0	0								
B	0	0	1								
Y	0	0									

Present state	Next state		Output	
	X=0	X=1	X=0	X=1
A B	A	B	A	B
0 0	0	0	0	1
0 1	0	0	1	1
1 0	0	0	1	0
1 1	0	0	1	0
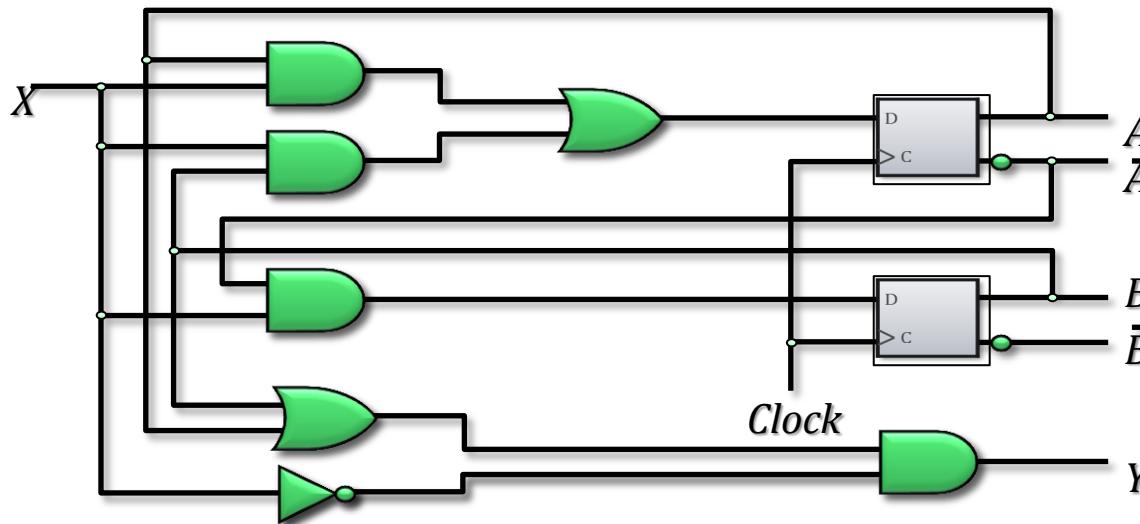
# Flip-flop input equations

- The set of Boolean functions that describes the part of the sequential circuit that generates the inputs to flip-flops.




$$D_A = Ax + B\bar{x}$$
$$D_B = \bar{A}x$$
$$Y = [A + B]\bar{x}$$

- The three equations provide the necessary information for drawing the logic diagram of the sequential circuit.
- The symbol  $D_A$  specifies a D flip-flop labeled A and  $D_B$  is for another D flip-flop labeled B.
- The flip-flop equations specify the combination circuit that drives the flip-flops and the type of flip-flops used.


# Analysis with D flip-flops

- Steps in analyzing clocked sequential circuits with D flip-flops:
  - Find the flip-flop input equations.
  - The state equations are the same as the flip-flop input equations for D flip-flops.
  - Derive the state table from the state equations.
  - Draw the state diagram from the state table

Example:

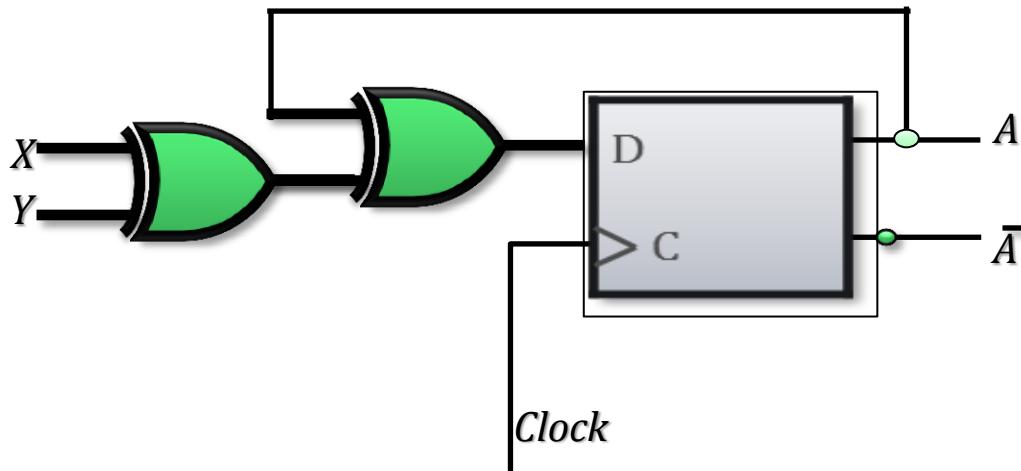

# Analysis with D flip-flops

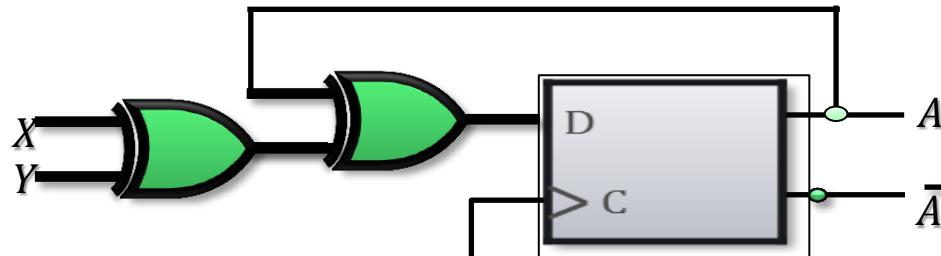

- State table:

*Clock*


State Diagram:

Present state	Input		Next state
A	X	Y	A
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Analysis with JK flip-flops

- Steps in analyzing clocked sequential circuits with JK flip-flops:
  - Find the flip-flop input equations in terms of present state and inputs.
  - List the binary values of each input equation.
  - Use the JK flip-flop characteristic table to determine the next states in the state table.
  - Use K-map to obtain minimized state equations

Example:

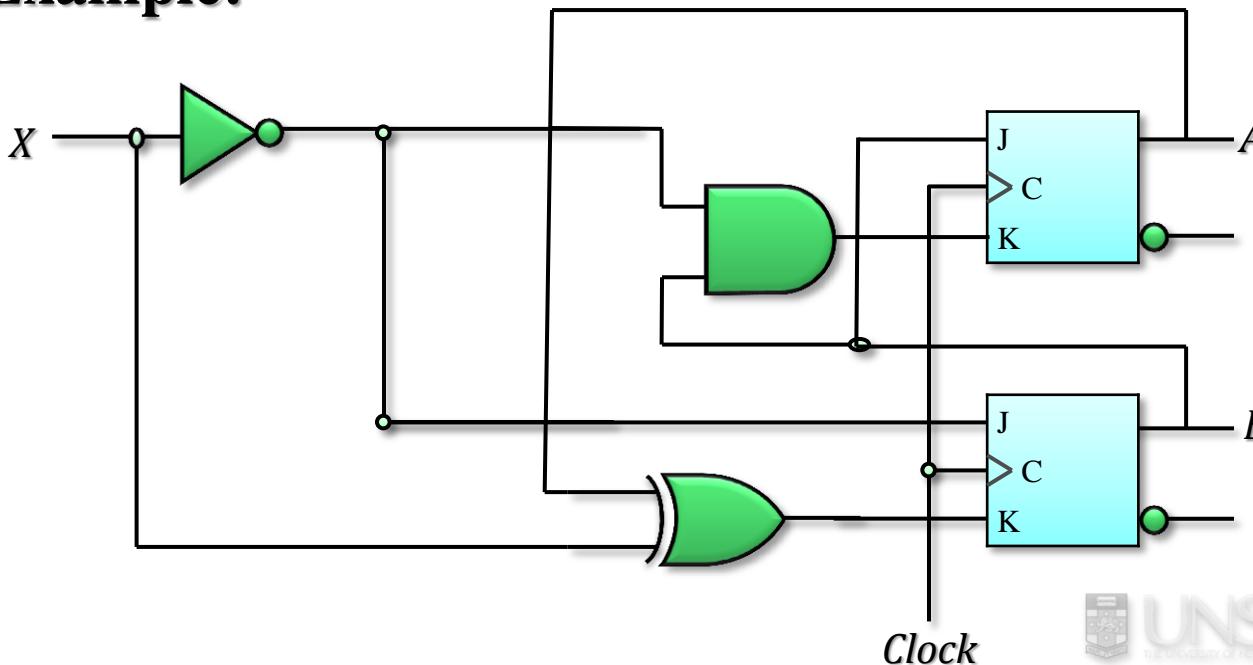

# Analysis with JK flip-flops

- Flip-flop input equations:

$$J_A =$$

$$J_B =$$

$$K_A =$$

$$K_B =$$

Present state	Input	Next state		Flip-Flop inputs			
		A	B	$J_A$	$K_B$	$J_B$	$K_B$
0 0	0						
0 0	0						
0 1	1						
0 1	1						
1 0	0						
1 0	0						
1 1	1						
1 1	1						

# Analysis with JK flip-flops

- Steps in analyzing clocked sequential circuits with JK flip-flops:
  - Find the flip-flop input equations in terms of present state and inputs.
  - Substitute the input equations into the flip-flop characteristic equation to obtain the state equations.
  - Use the corresponding state equations to determine the next-values in the state table and state diagrams

For previous example:

$$J_A = B$$

$$K_A = B\bar{X}$$

$$J_B = \bar{X}$$

$$K_B = \overline{A \oplus x}$$

Characteristic equation for JK flip-flop:

$$A(t+1) = J_A \bar{A} + \overline{K_A} A$$

$$B(t+1) = J_B \bar{B} + \overline{K_B} B$$

# Analysis with JK flip-flops

State Table:

Present state		Next State					
		X=0		X=1			
A	B	A	B	A	B		
0	0						
0	1						
1	0						
1	1						

State Diagram:

# Analysis with T flip-flops


- The same procedure as JK flip-flop is to be followed:
  - Find the flip-flop input equations in terms of present state and inputs.
  - List the binary values of each input equation.
  - Use the T flip-flop characteristic table to determine the next states in the state table.
  - Use K-map to obtain minimized state equations

OR

- Find the flip-flop input equations in terms of present state and inputs.
- Substitute the input equations into the flip-flop characteristic equation to obtain the state equations.
- Use the corresponding state equations to determine the next-values in the state table and state diagrams

# Analysis with T flip-flops

Example:

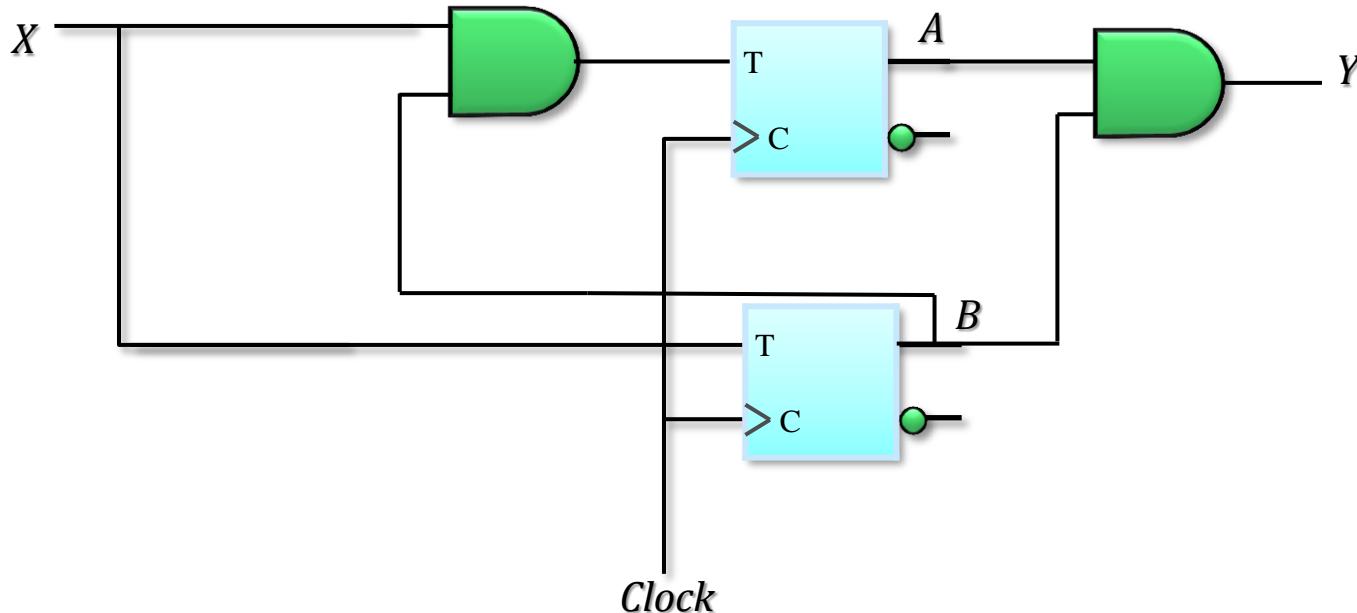

Flip-flop input equations:

$$T_A =$$

$$T_B =$$

Output equation:

$$Y = AB$$

# Analysis with T flip-flops

Present state		Input	Next state		Flip-Flop inputs	
A	B	X	A	B	$T_A$	$T_B$
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

# Analysis with T flip-flops

For previous example:

$$T_A =$$

$$K_A = B \bar{X}$$

$$T_B =$$

Characteristic equation for T flip-flop:

$$A(t+1) = \overline{T_A \oplus A}$$

$$B(t+1) = \overline{T_B \oplus B}$$

# Analysis with T flip-flops

State Table:

Present state		Next State				Output state	
		X=0		X=1		X=0	X=1
A	B	A	B	A	B	Y	Y
0	0						
0	1						
1	0						
1	1						

State Diagram: