



Lecture 12: Op-Amps – Part II

ELEC1111 Electrical and Telecommunications Engineering


Never Stand Still

Faculty of Engineering


School of Electrical Engineering and Telecommunications

Op-Amp Differentiator


Operational amplifiers can be combined with reactive elements in such a manner that the output voltage is the time derivative of the input voltage.

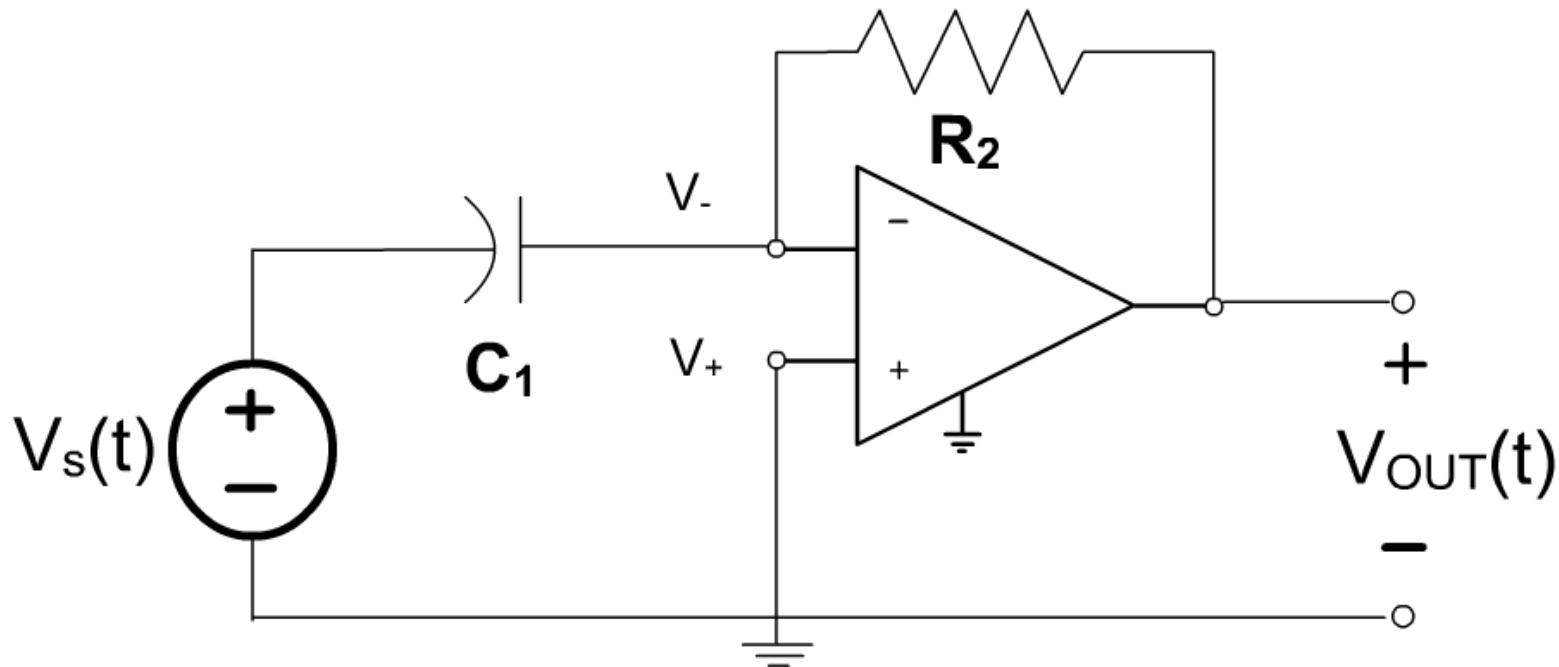

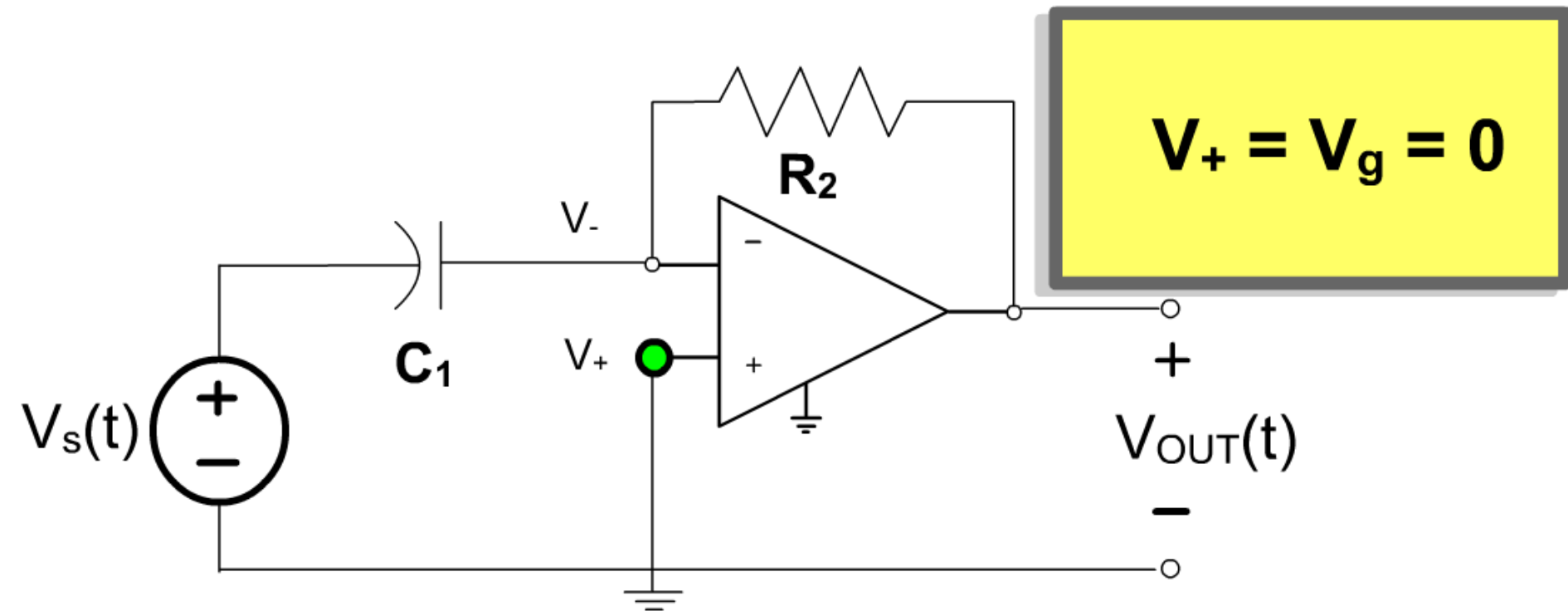
Since V_- is grounded, the node has a potential of zero volts.



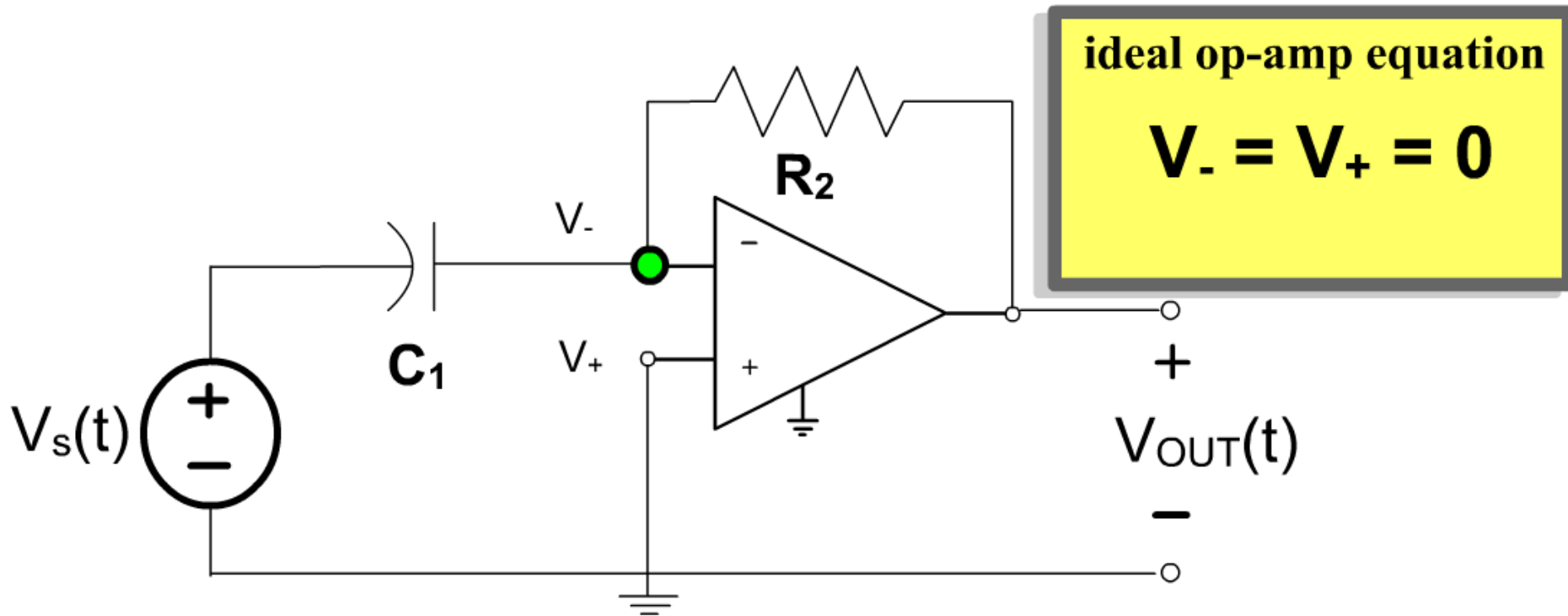From the first ideal op-amp relation, $V_- = V_+$.




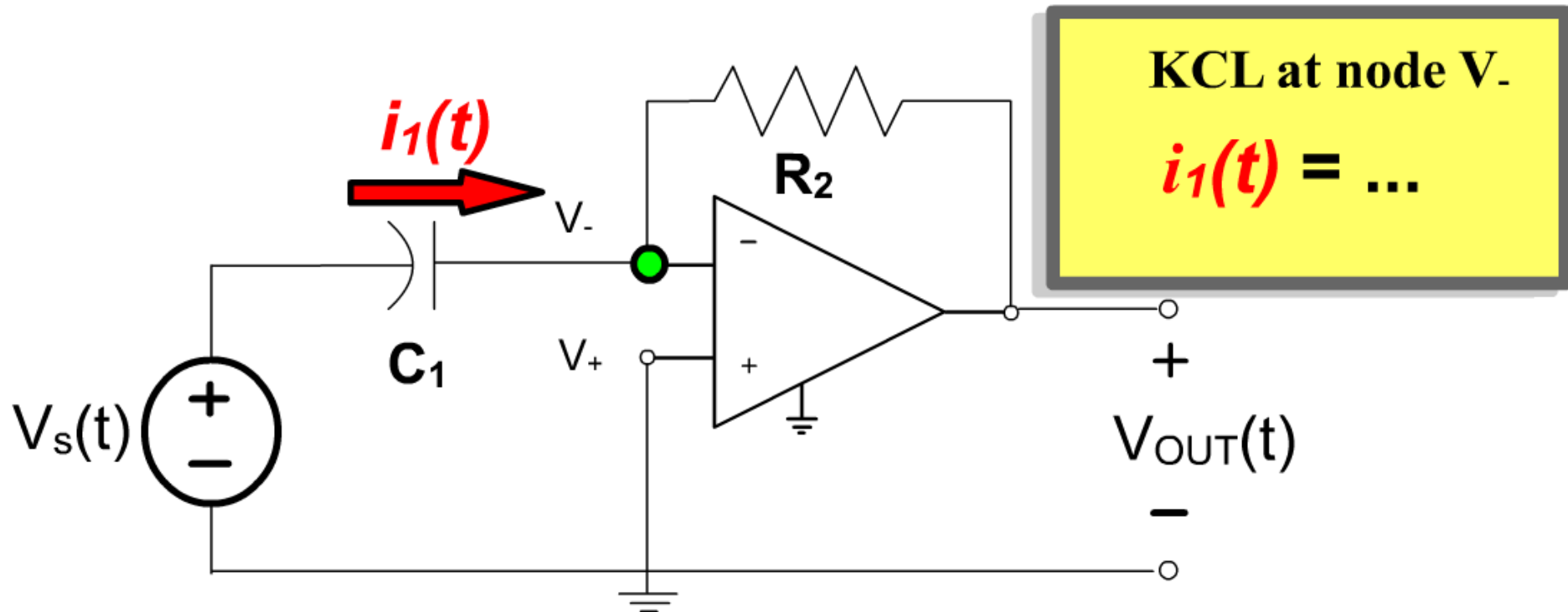Now write KCL at node V_- . The current across C_1 will be denoted as $i_1(t)$.




The other two currents will be labeled as $i_2(t)$ and i_- , which is denoted as leaving the node V_- . The KCL equation is


$$i_1(t) = i_2(t) + i_-.$$

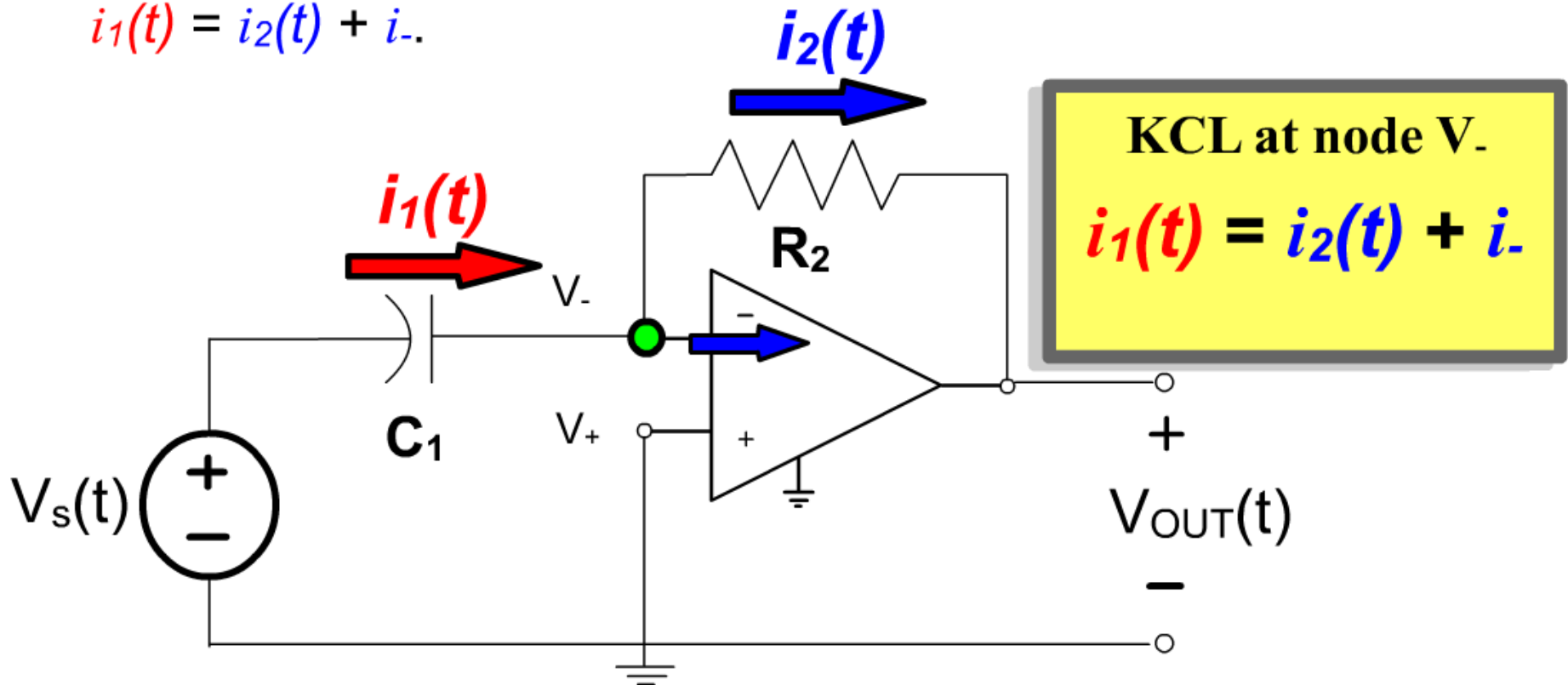

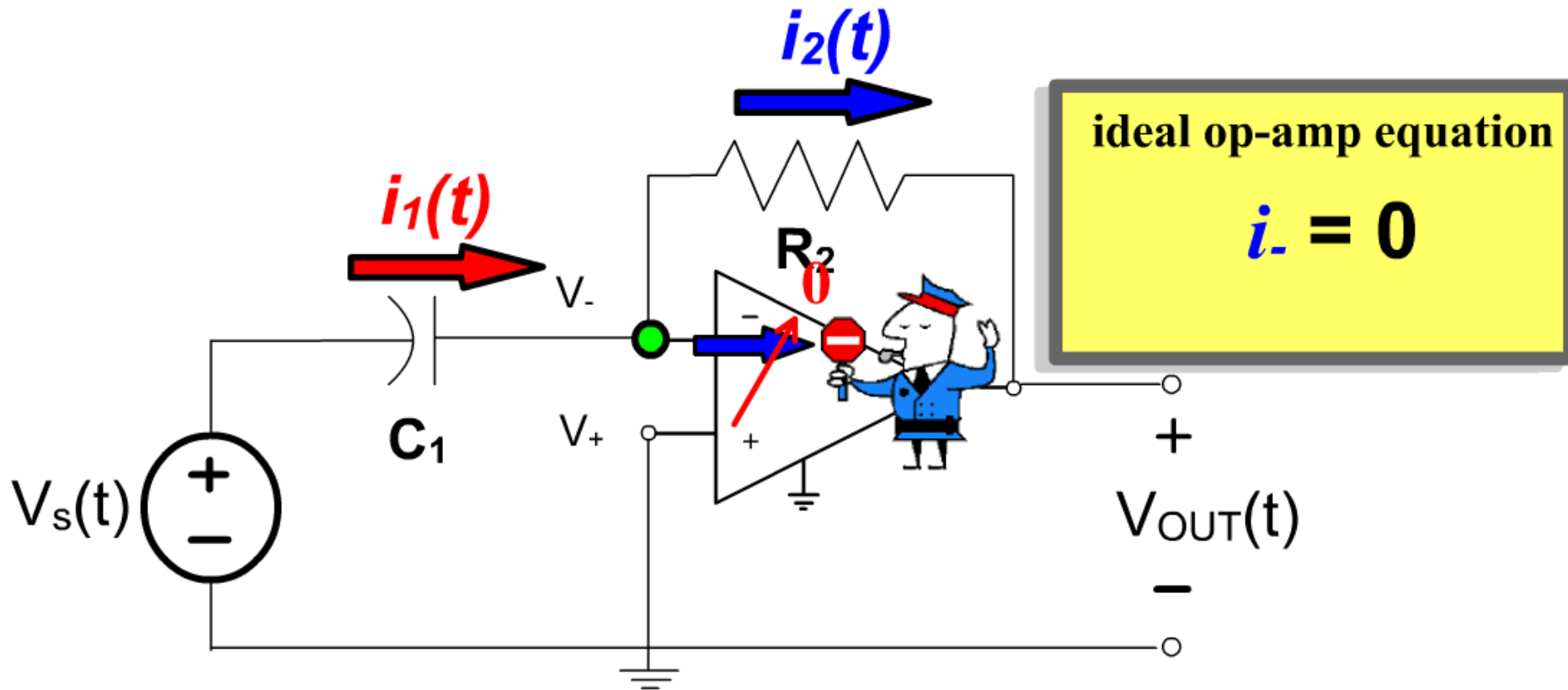
The second ideal op-amp equation requires that the $i_- = 0$.
No current enters this terminal.



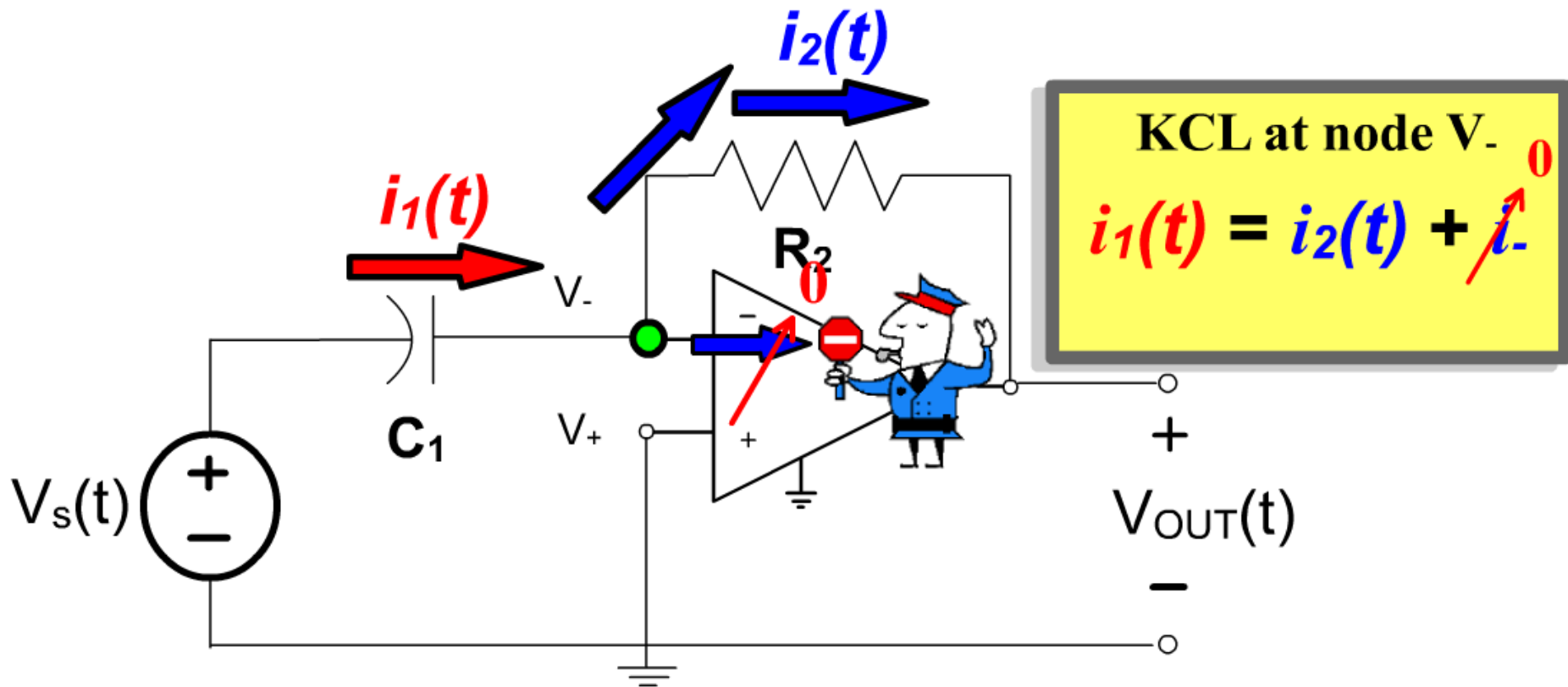
The KCL equation can be simplified to $i_1(t) = i_2(t)$.



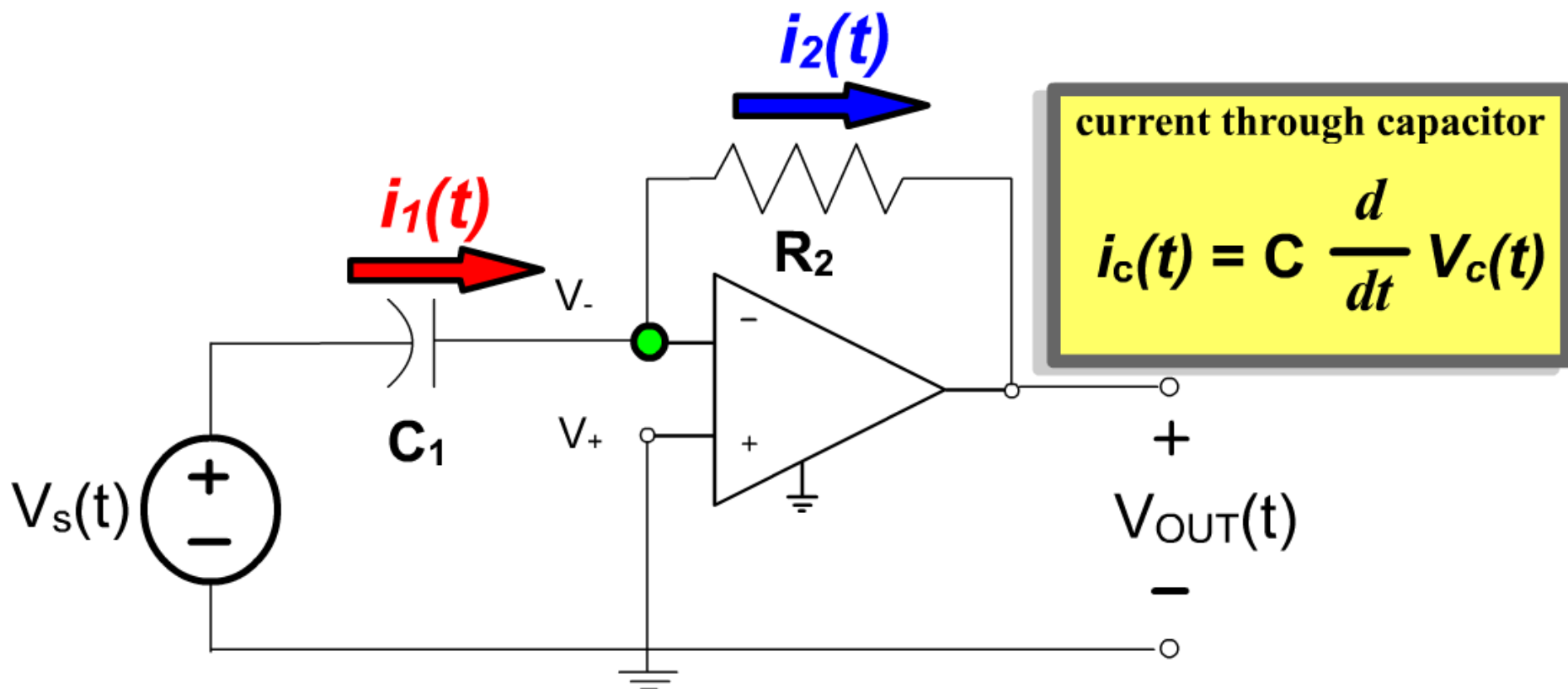
To solve for $i_1(t)$, recall that the current through a capacitor is proportional to the time derivative of the capacitor voltage.



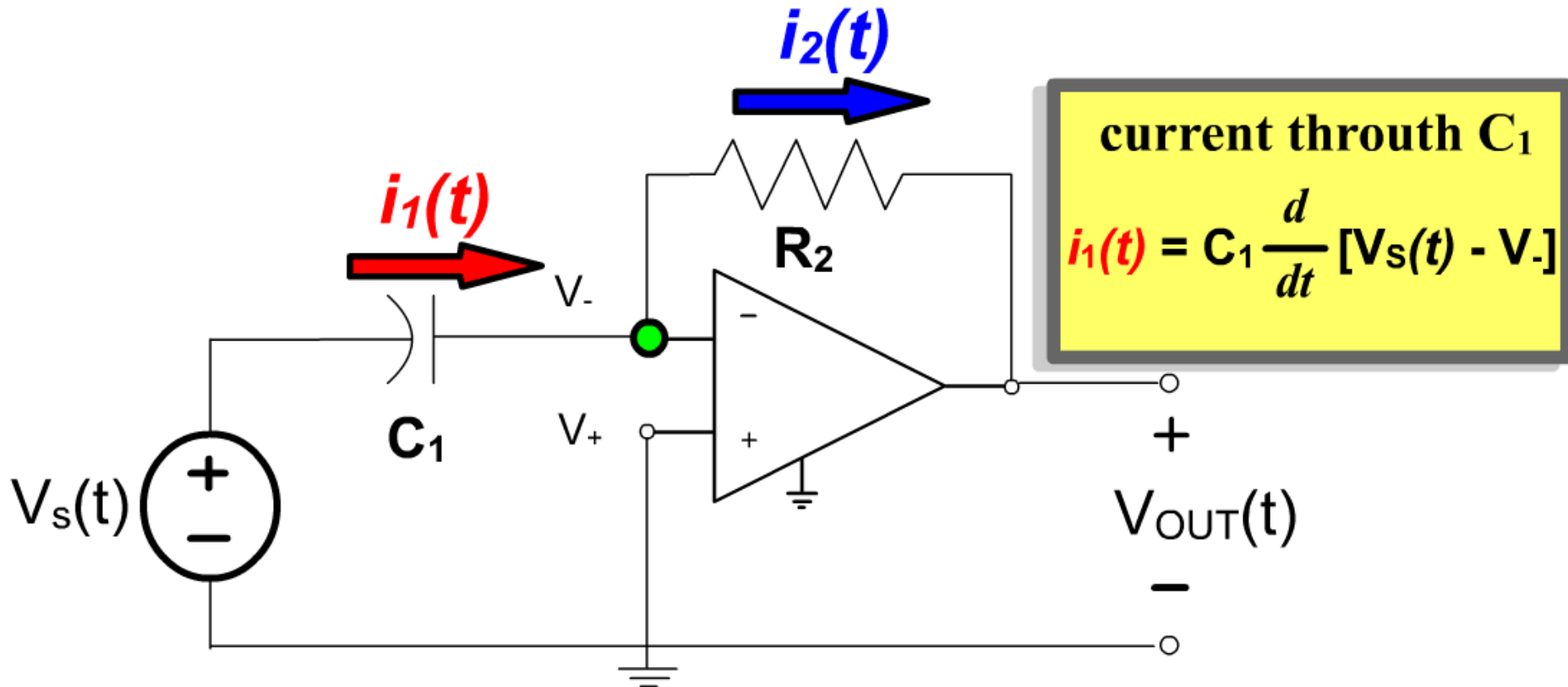
The current $i_1(t)$ through C_1 is the capacitance times the time derivative of the potential difference.



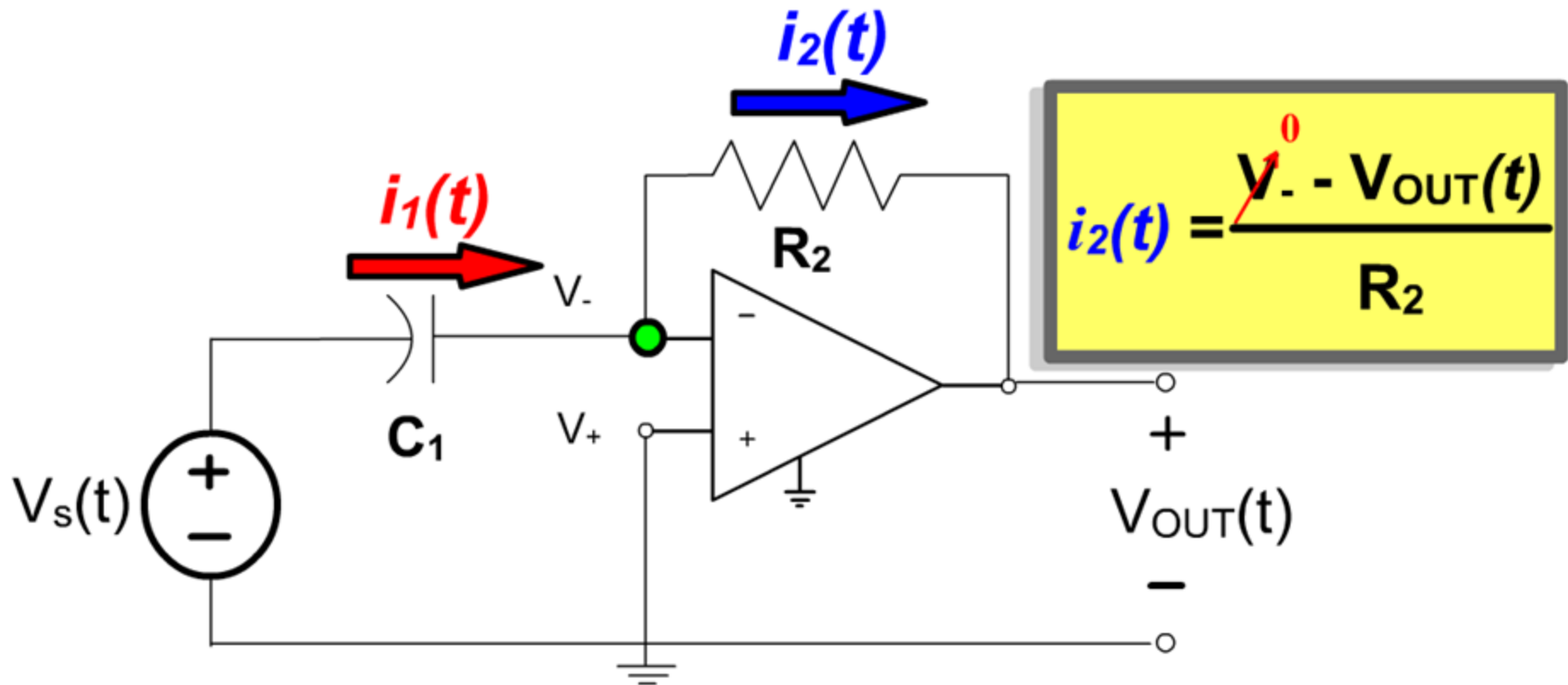
The current through $i_2(t)$ is found using Ohm's law.





By writing KCL at node V₋ we then have

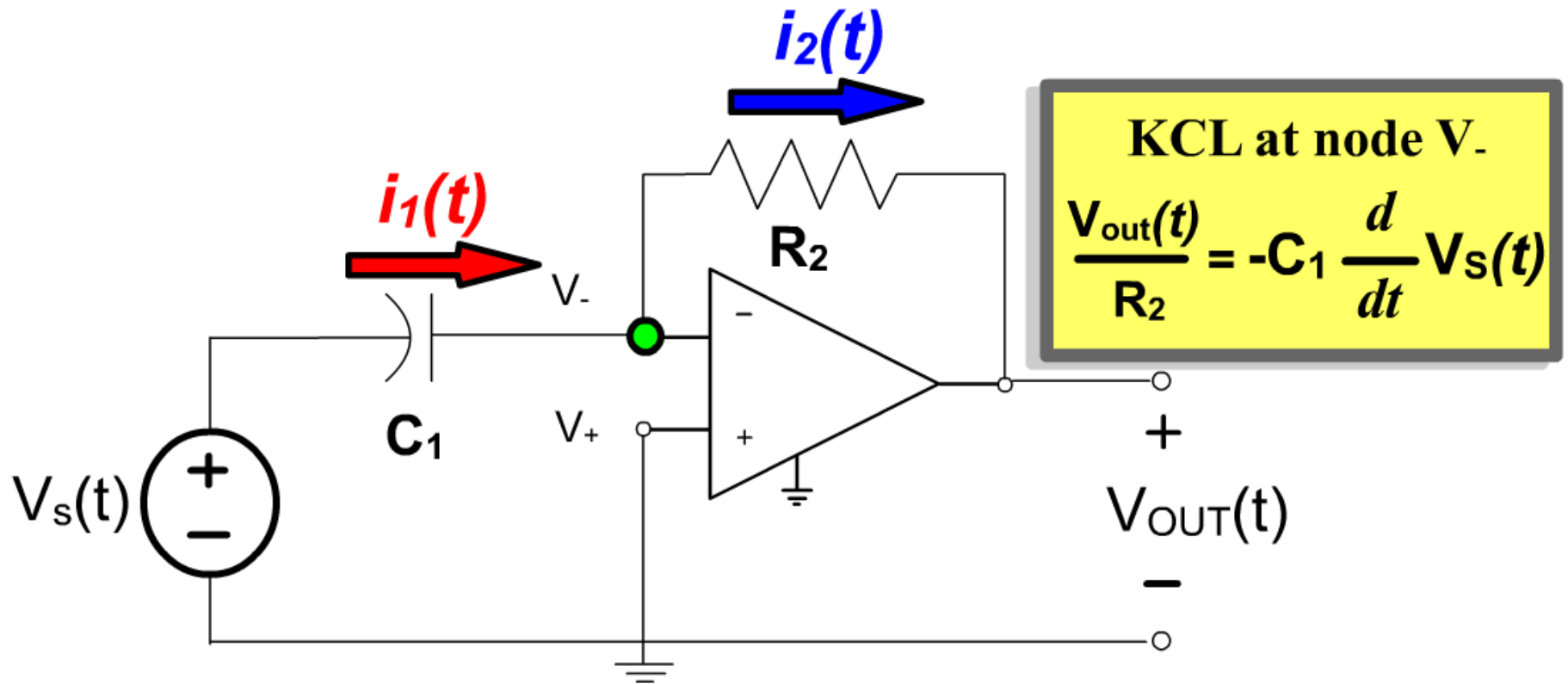

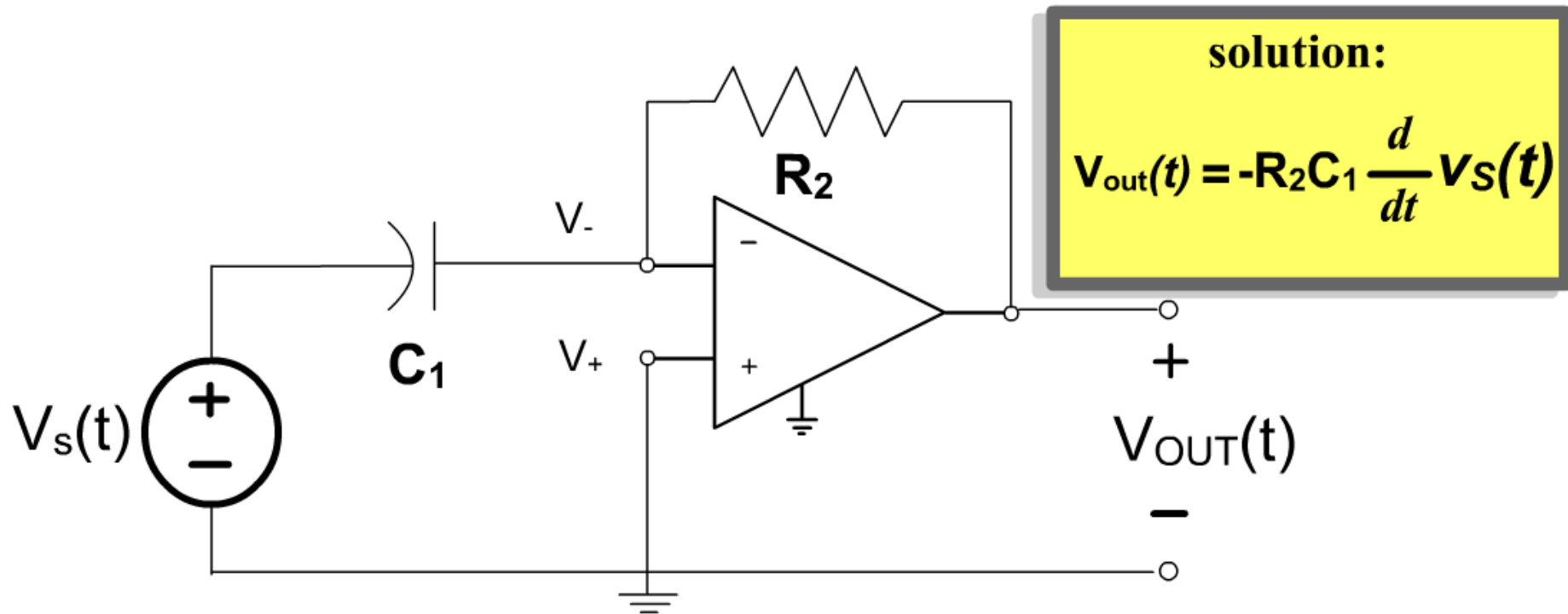
Rearranging the equation yields the solution



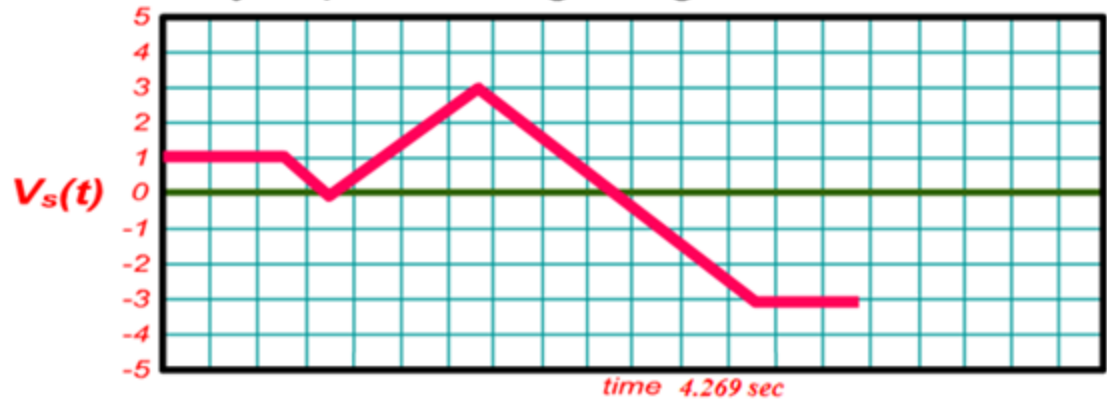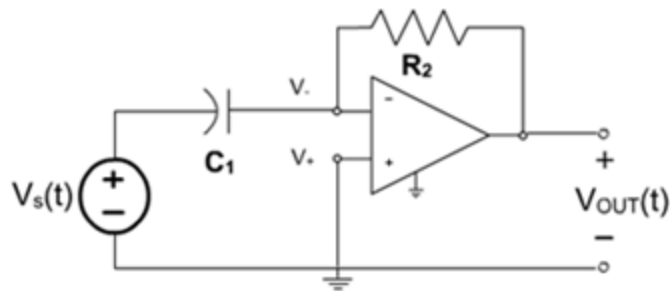The graphs below show the differentiation performed by the op-amp circuit for an arbitrary input voltage signal.



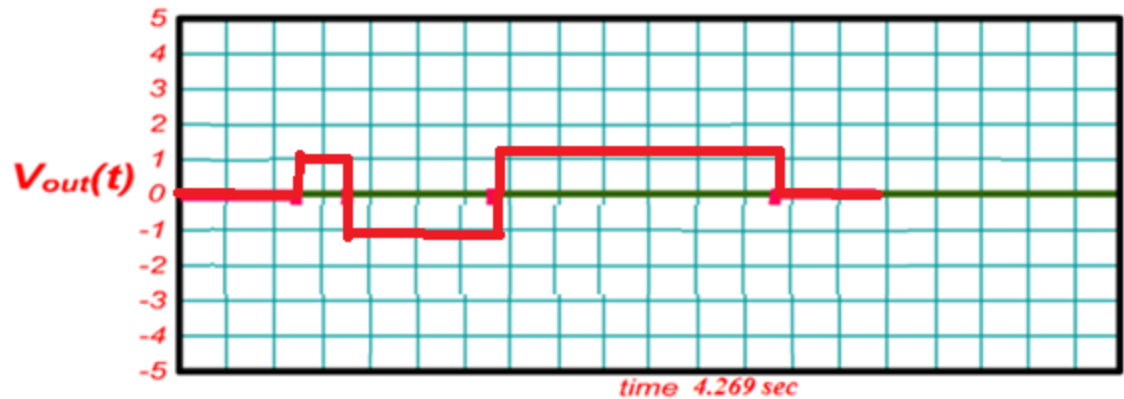
$$V_{out}(t) = -R_2 C_1 \frac{d}{dt} V_s(t)$$




Op-Amp Integrator

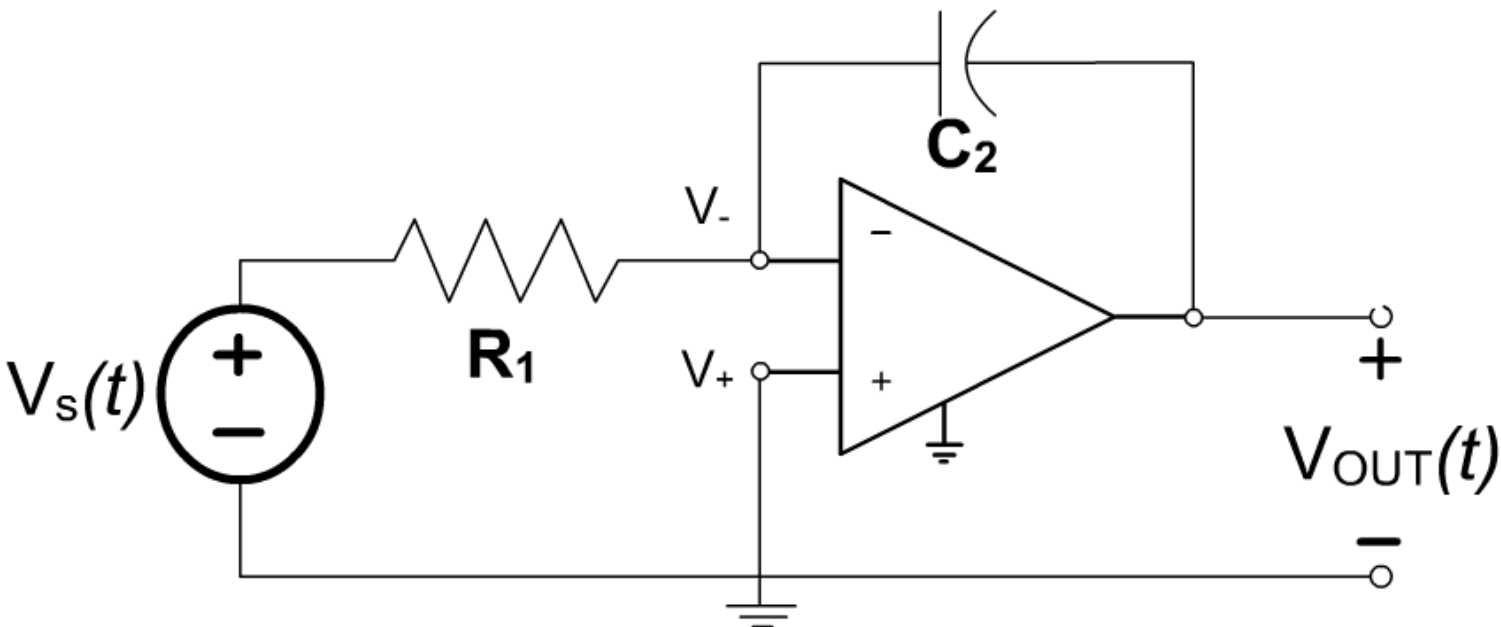Operational Amplifiers can be combined with reactive elements in such a manner that the output voltage is the time integral of the input voltage.




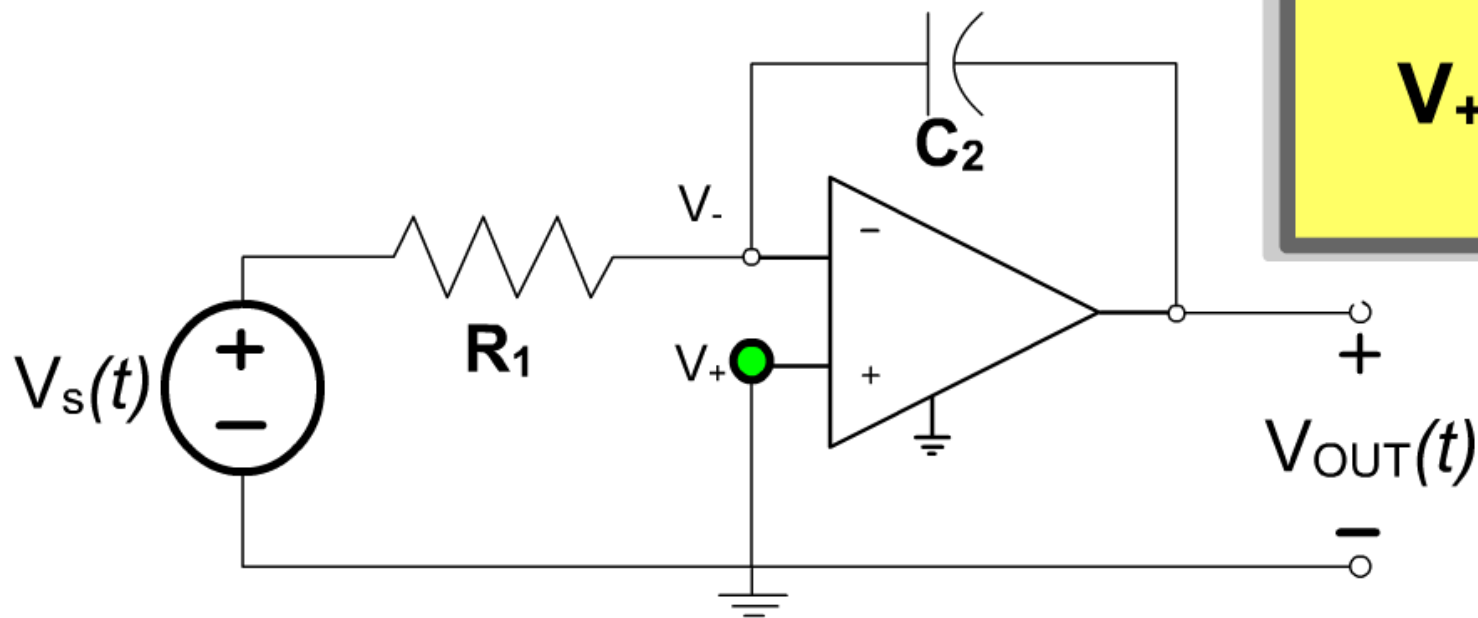Notice that V_+ is connected to ground, and has a potential of zero volts.



$$V_+ = V_g = 0$$

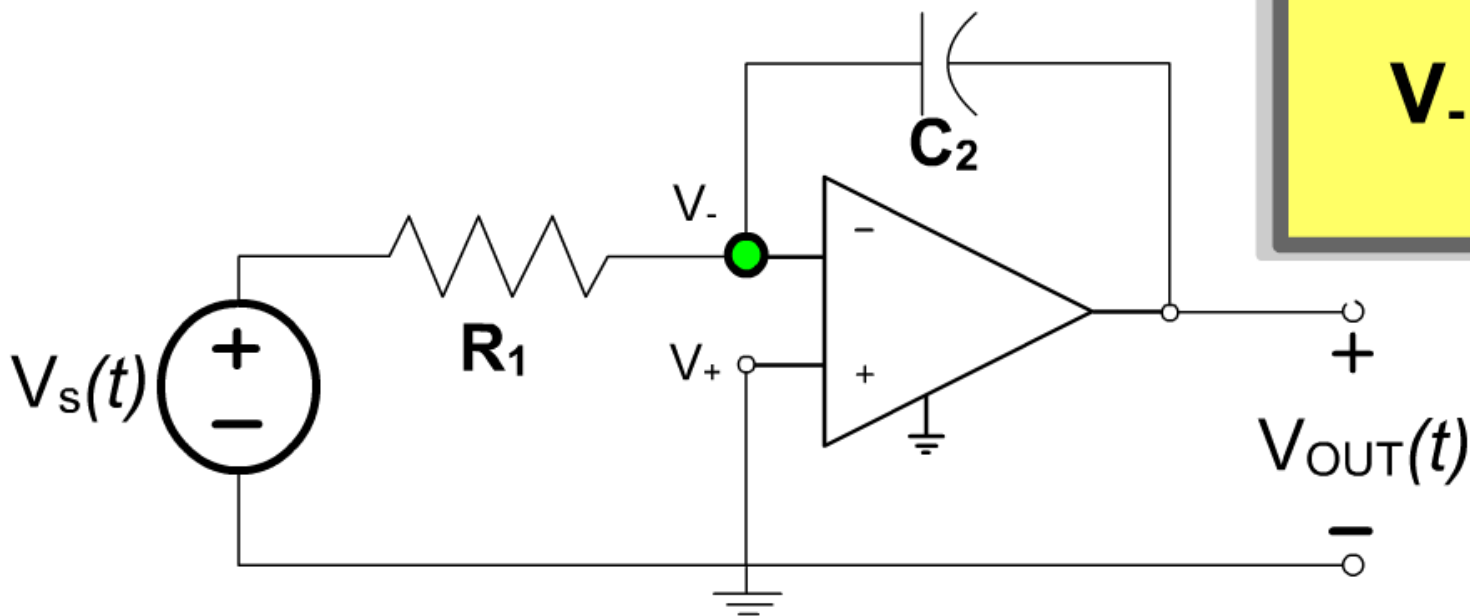
From the first ideal op-amp equation, $V_- = V_+$.



ideal op-amp equation

$$V_- = V_+ = 0$$

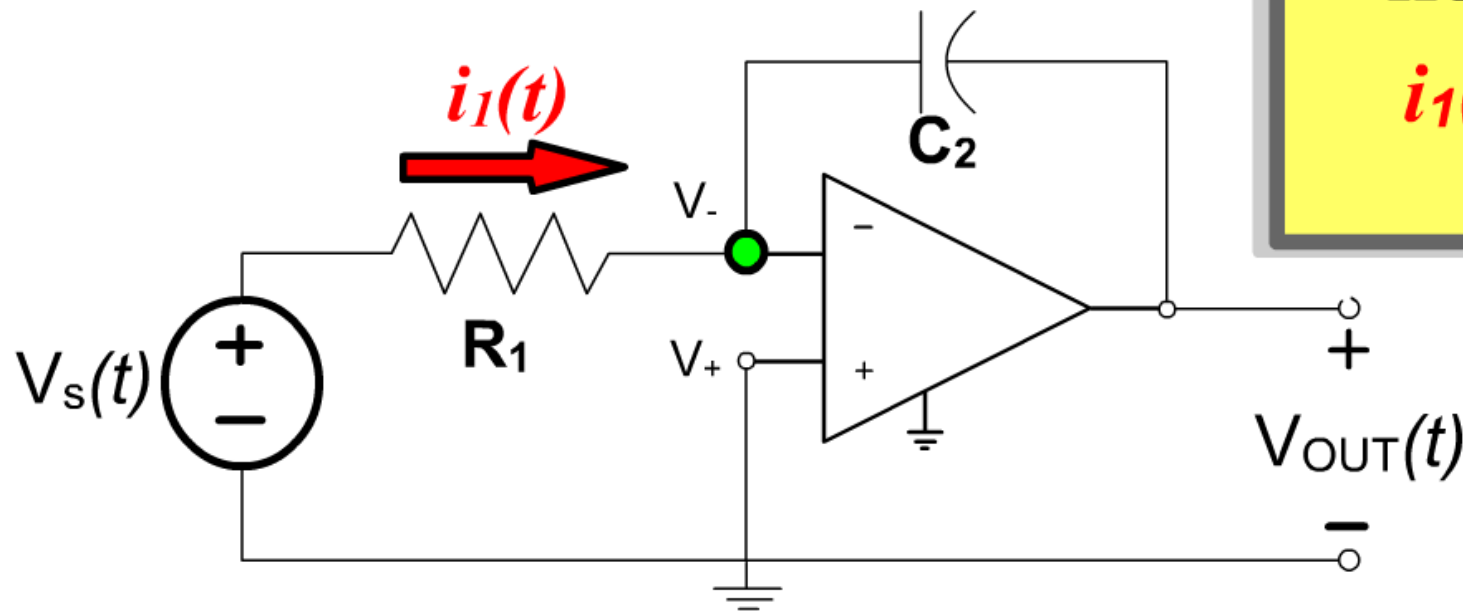
Now write KCL at node V_- . For convenience, the current across R_1 will be labeled as $i_1(t)$ and indicated as entering the node.



KCL at node V_-

$$i_1(t) = \dots$$

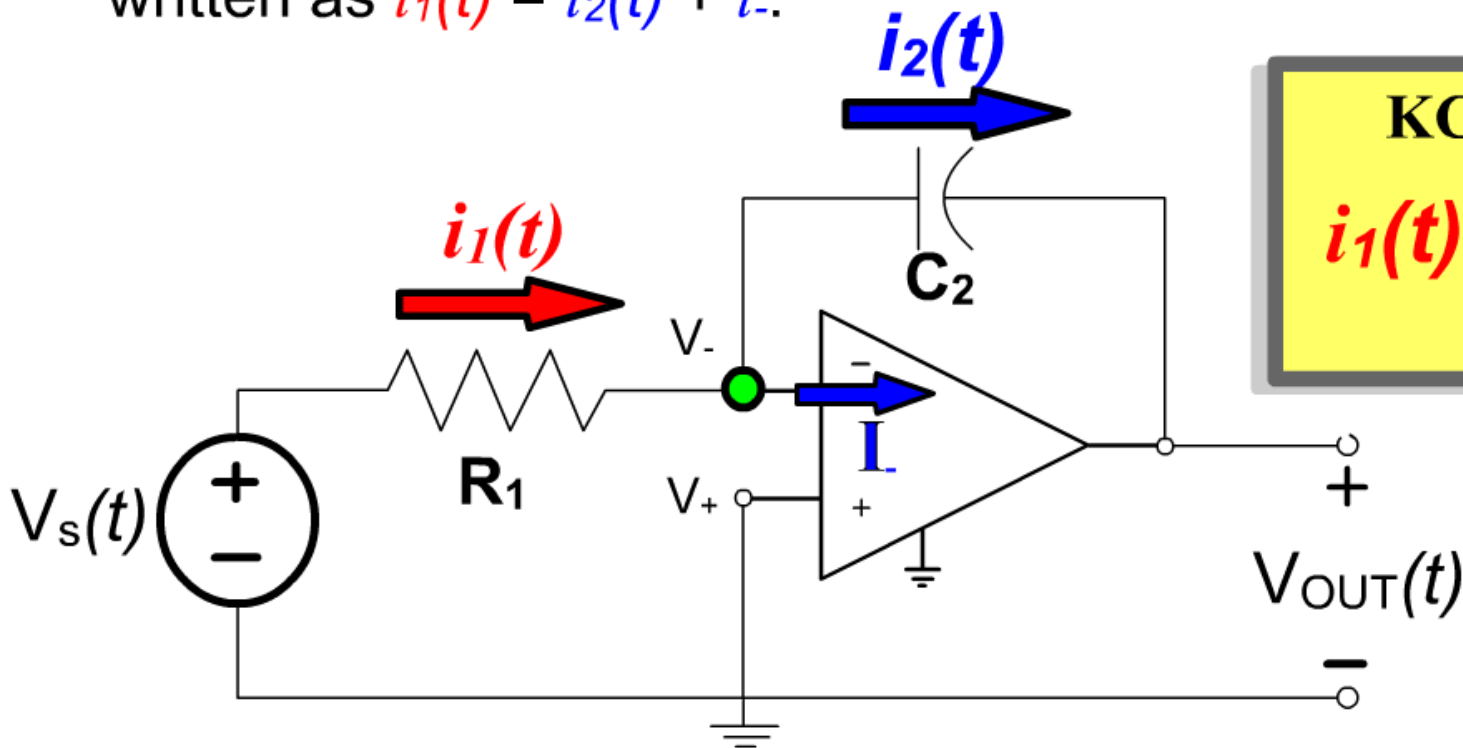
The other two currents are labeled as $i_2(t)$ and i_- , which is denoted as leaving the node V_- . The KCL equation can be written as $i_1(t) = i_2(t) + i_-$.



KCL at node V_-

$$i_1(t) = i_2(t) + i_-$$

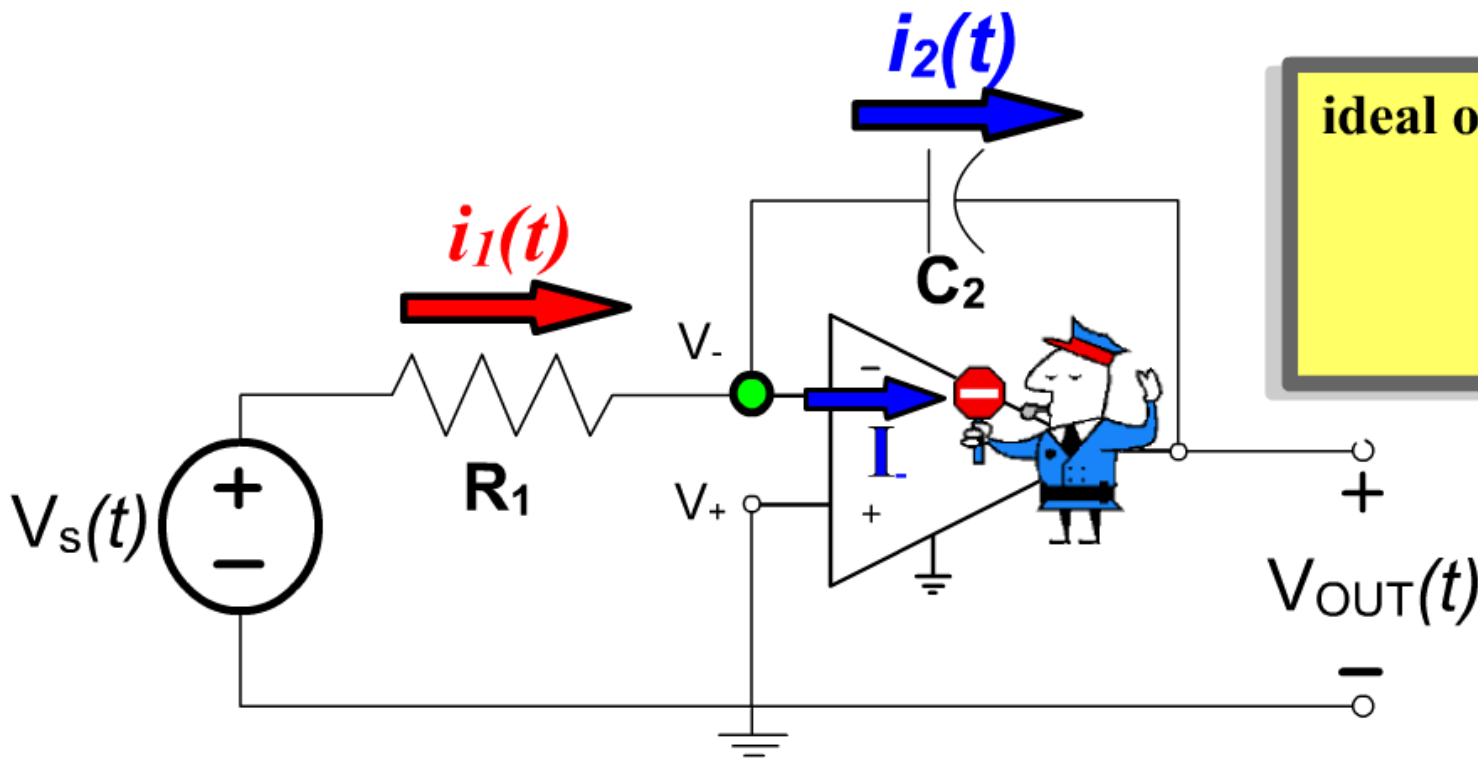
The second ideal op-amp equation requires that the $i_- = 0$.
No current enters this terminal.




ideal op-amp equation

$$i_- = 0$$

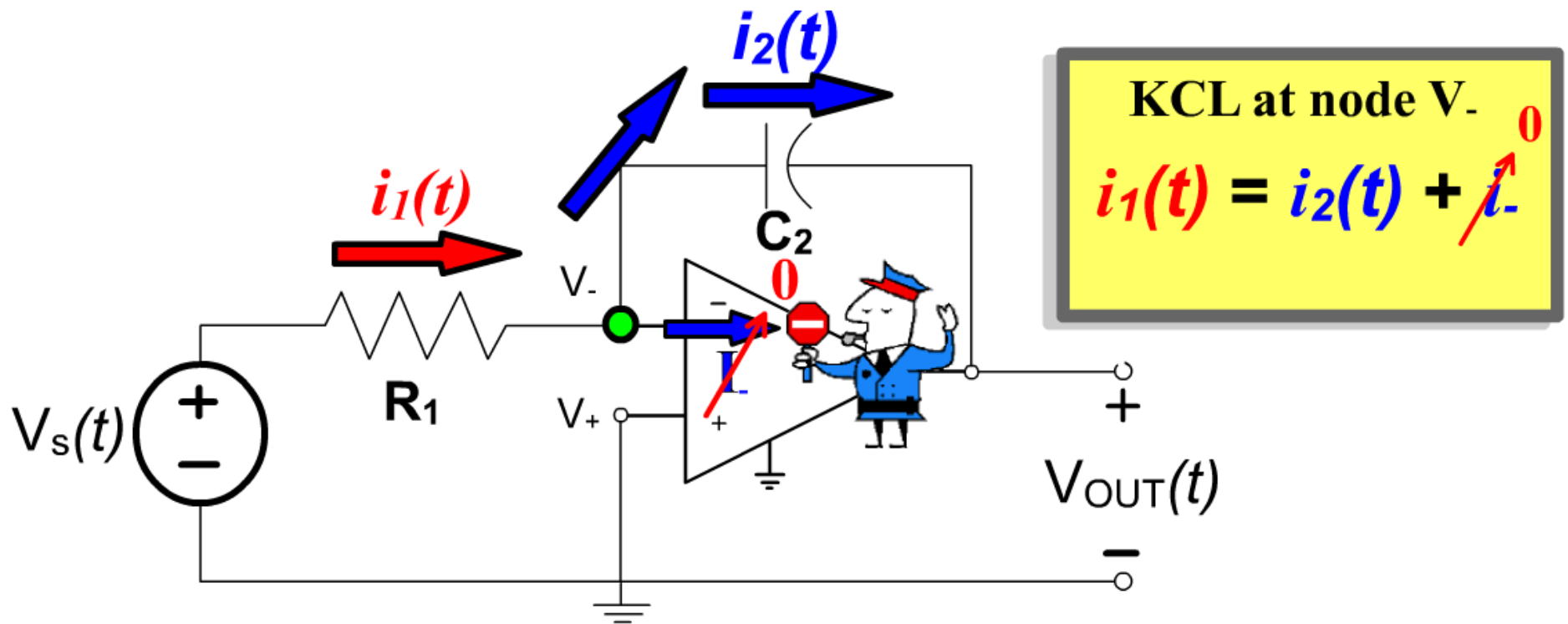The KCL equation can be simplified to $i_1(t) = i_2(t)$.




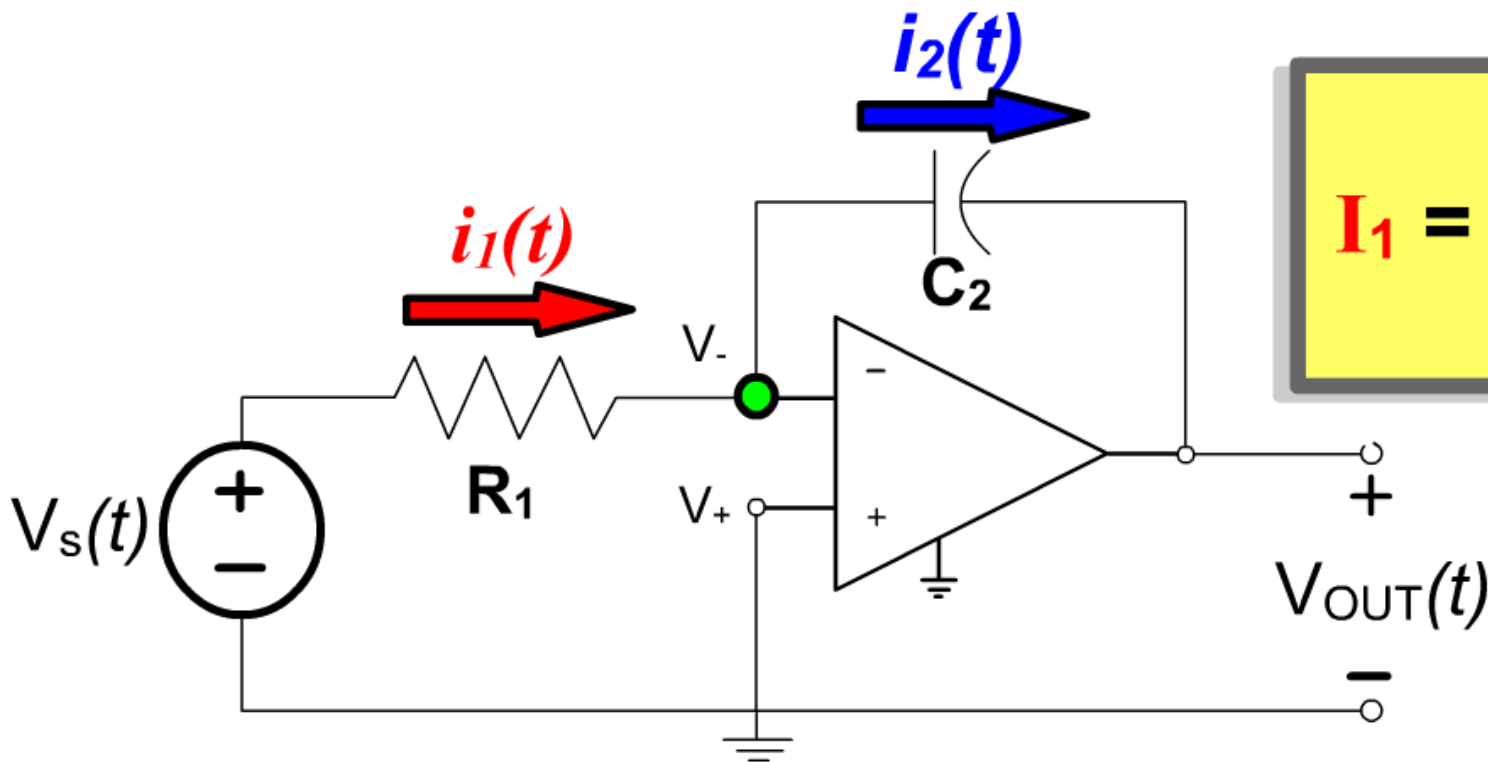The current $i_1(t)$ across element R_1 is the difference in potential $V_S(t) - V_- = V_S(t)$, divided by the resistance, R_1 .



$$I_1 = \frac{V_S(t) - V_-}{R_1}$$

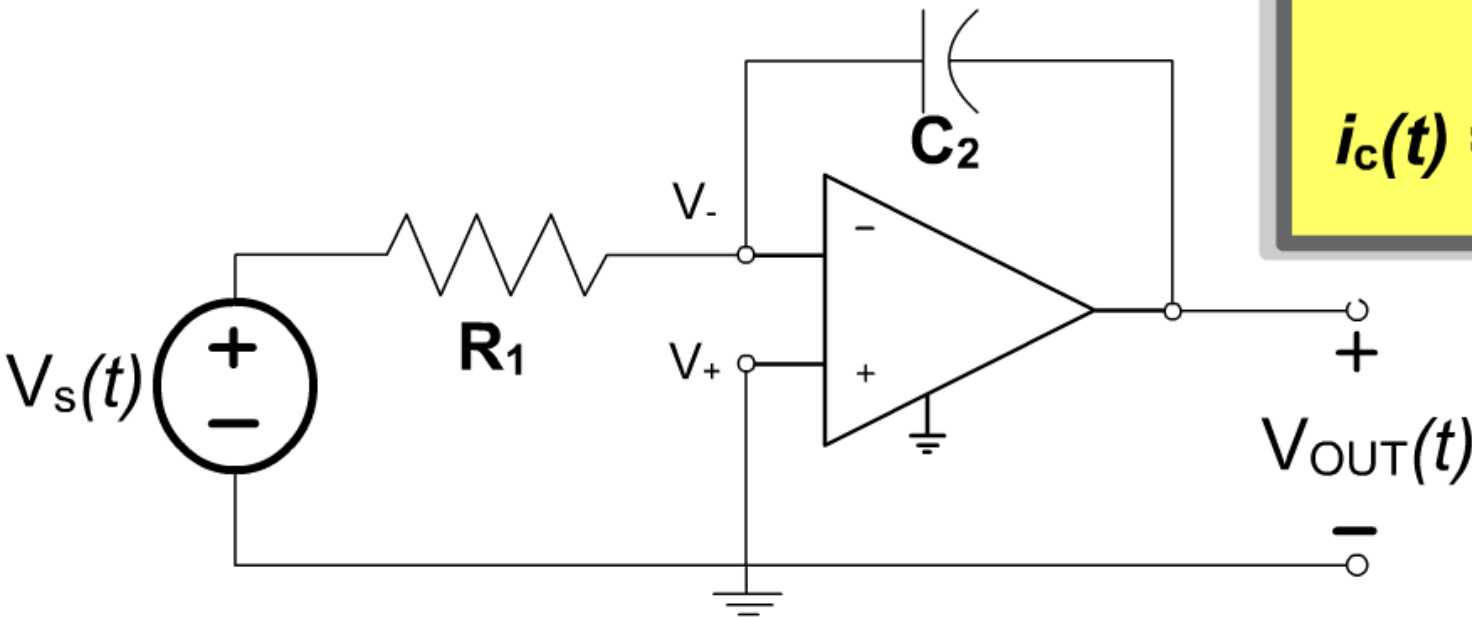
Recall that the current through a capacitor is proportional to the time derivative of the voltage across the capacitor.



current through capacitor

$$i_c(t) = C \frac{d}{dt} V_c(t)$$

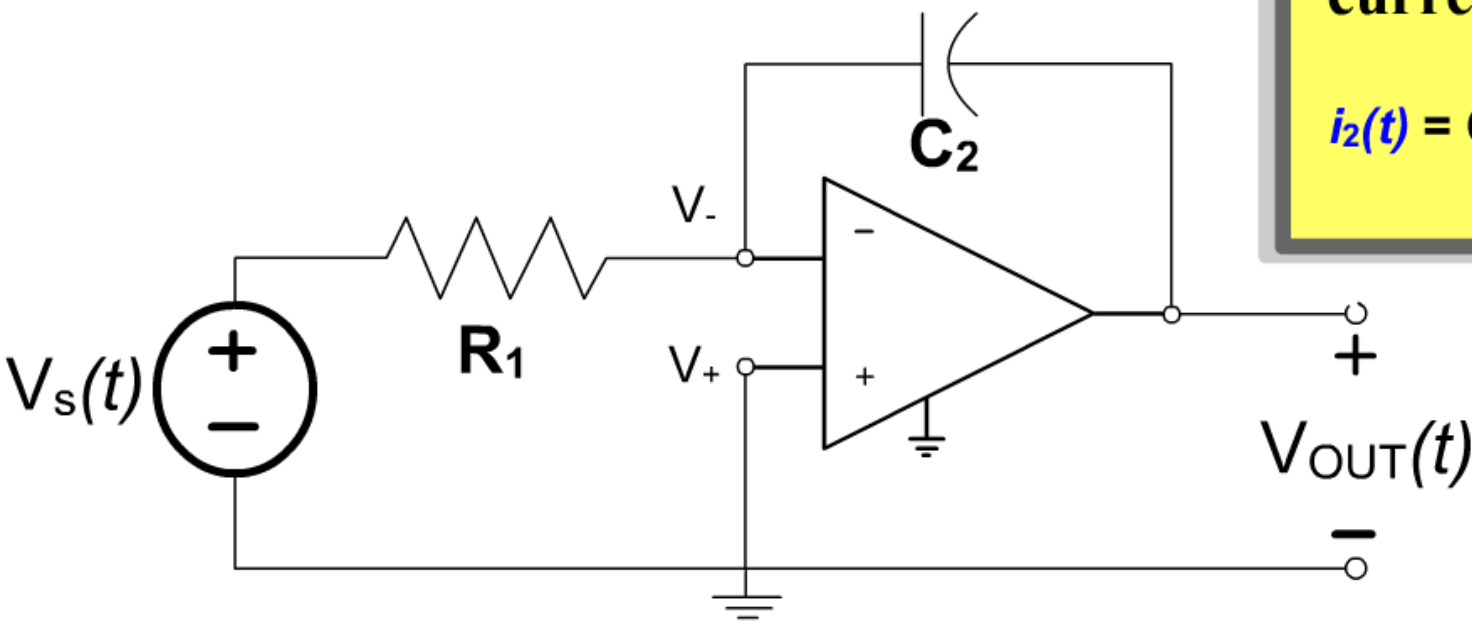
The current $i_2(t)$ through C_2 is the capacitance times the time derivative of the potential difference.



current through C_2

$$i_2(t) = C_2 \frac{d}{dt} [V_- - V_{out}(t)]$$

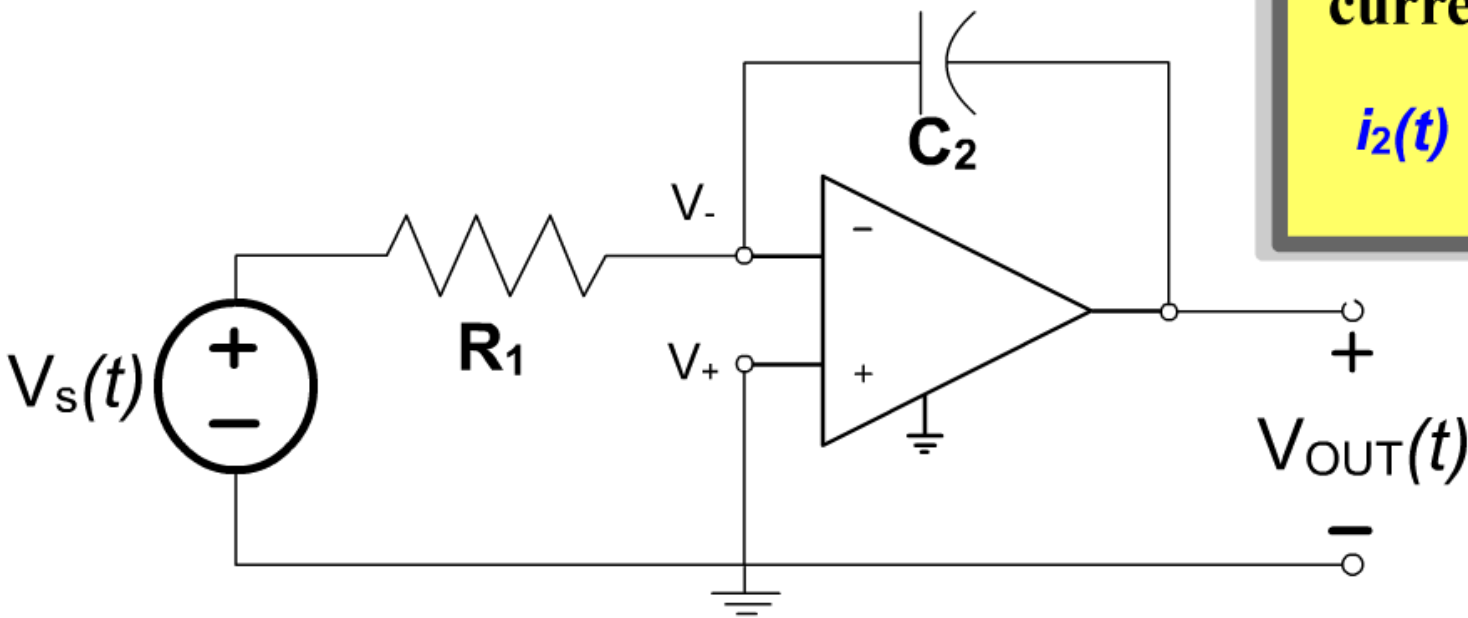
Since $V_- = 0$, the equation for $i_2(t)$ is simply



current through C_2

$$i_2(t) = -C_2 \frac{d}{dt} V_{out}(t)$$

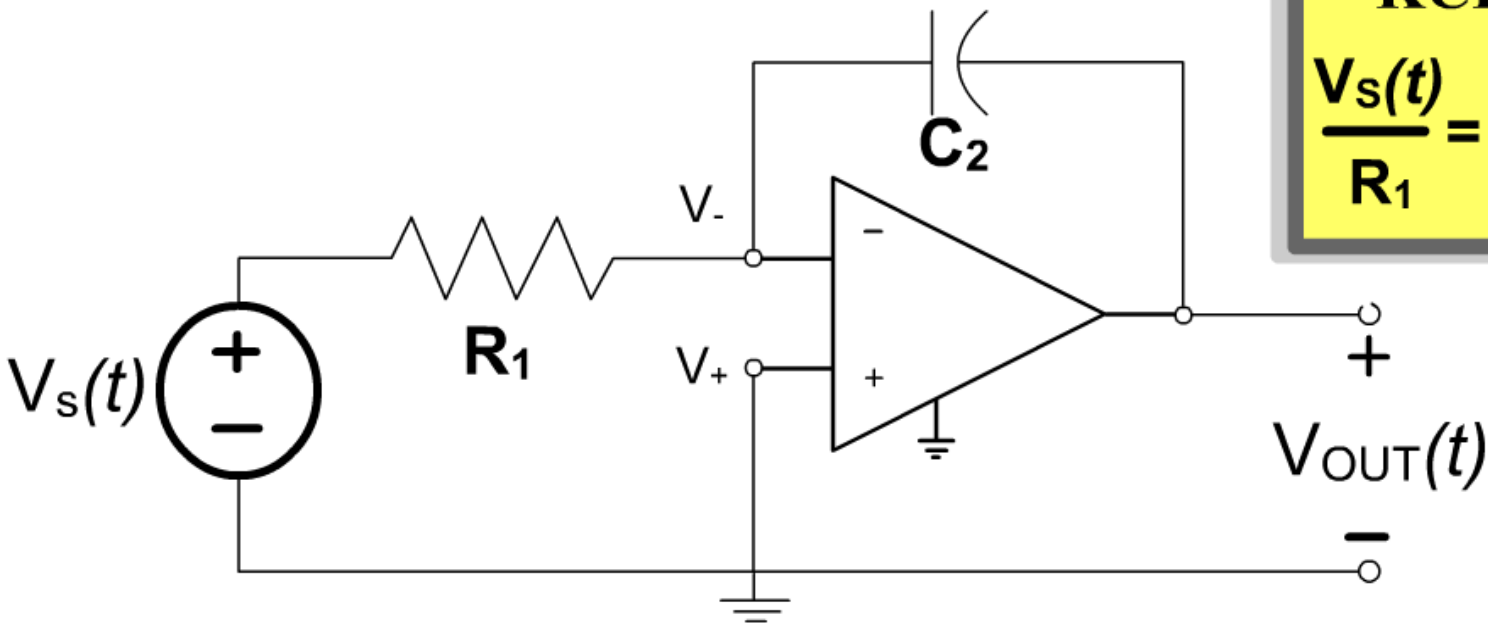
After substitution, KCL at node V_- is written as



KCL at node V_-

$$\frac{V_s(t)}{R_1} = -C_2 \frac{d}{dt} V_{out}(t)$$


The equation is rearranged

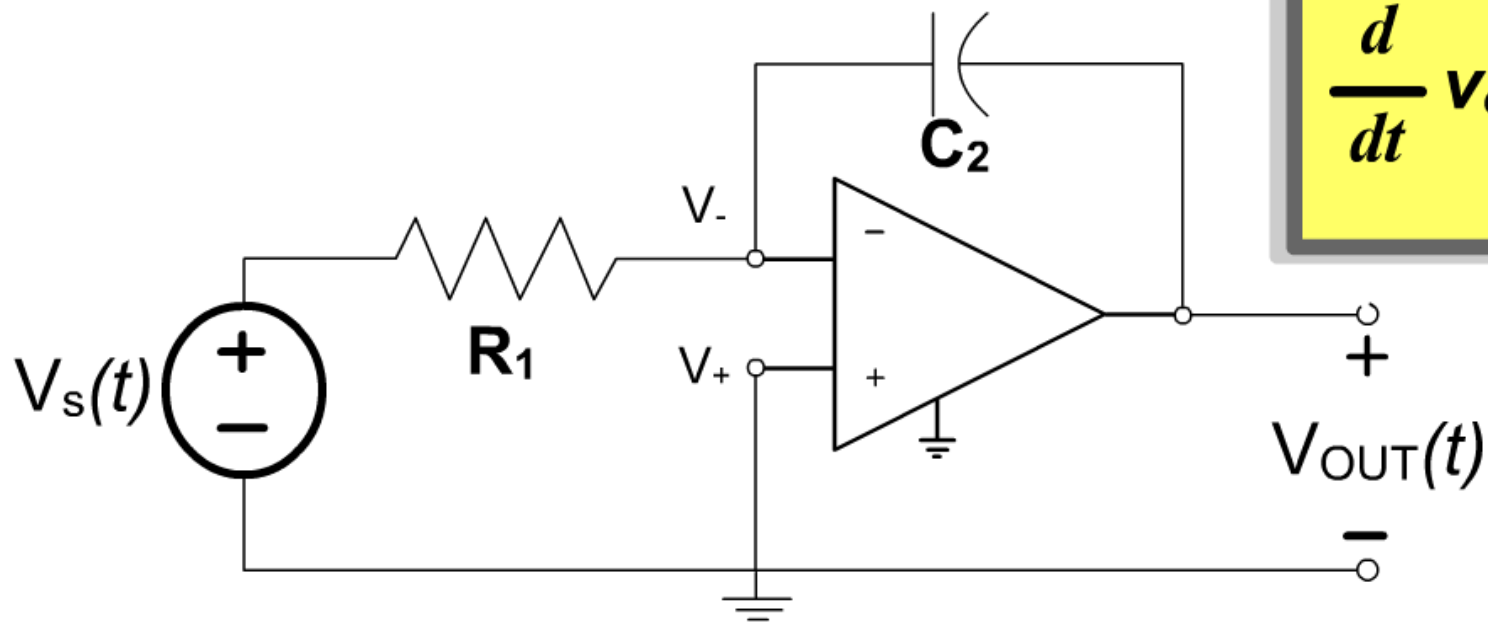




$$\frac{d}{dt} v_{out}(t) = \frac{-V_s(t)}{R_1 C_2}$$

Integrate both sides of the equation up to the present time
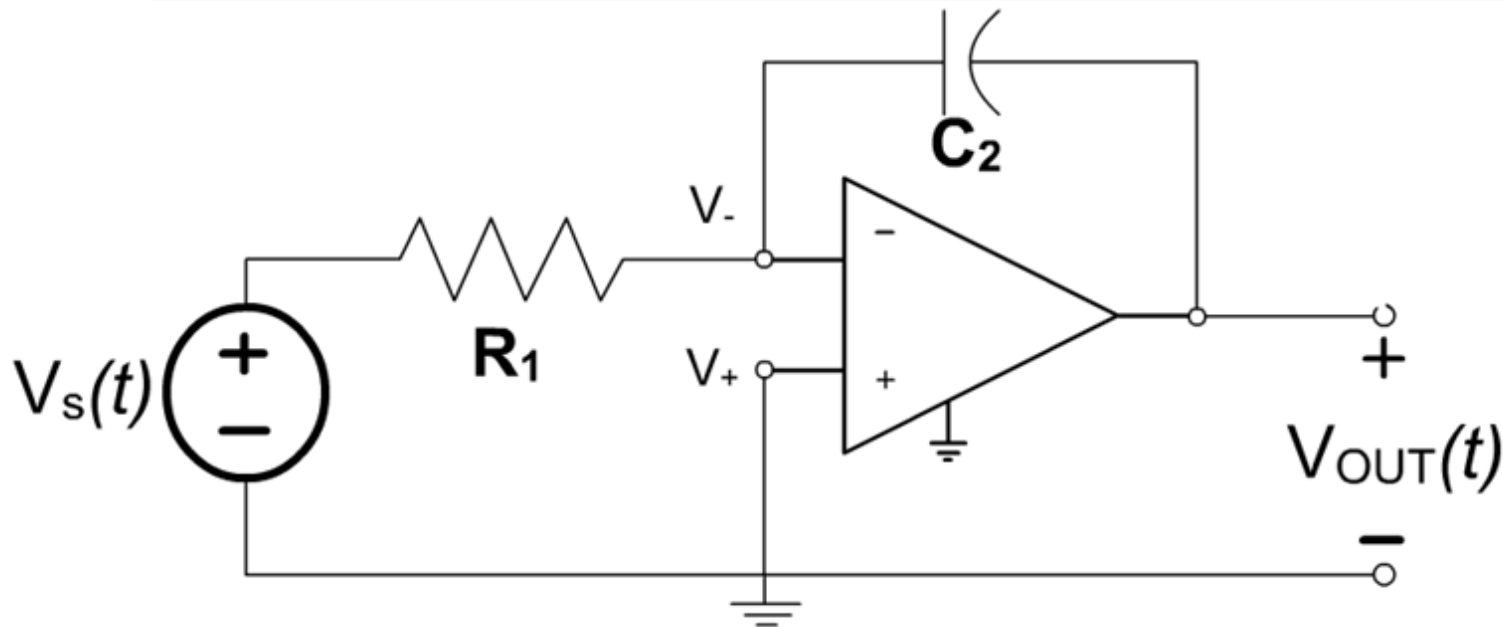
$$V_{out}(t) = \int_{-\infty}^t \frac{-V_s(t)}{R_1 C_2} dt$$





The graphs below show the integration performed by the op-amp circuit for an arbitrary input voltage signal.

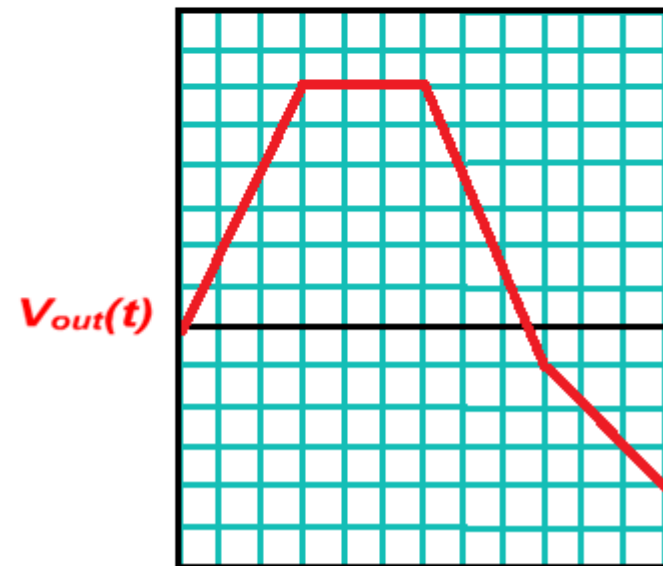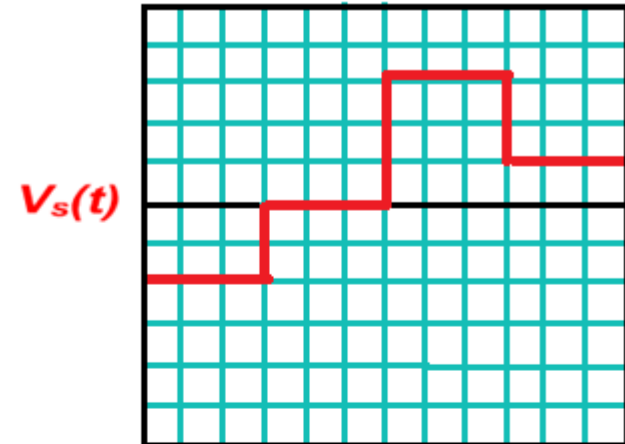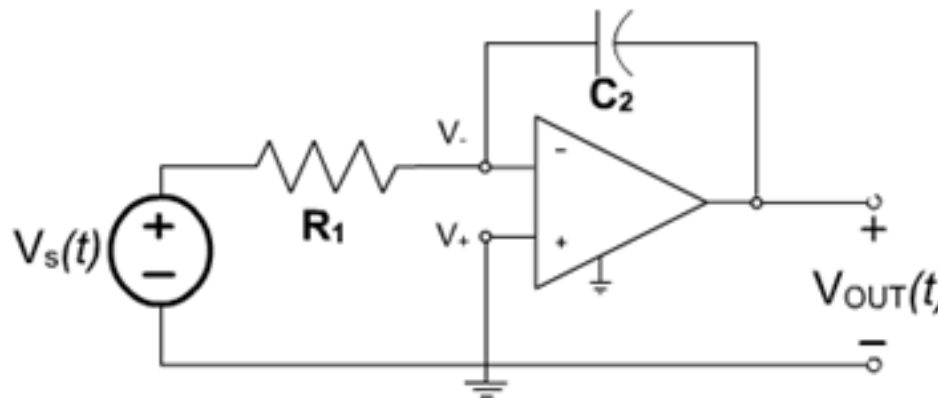

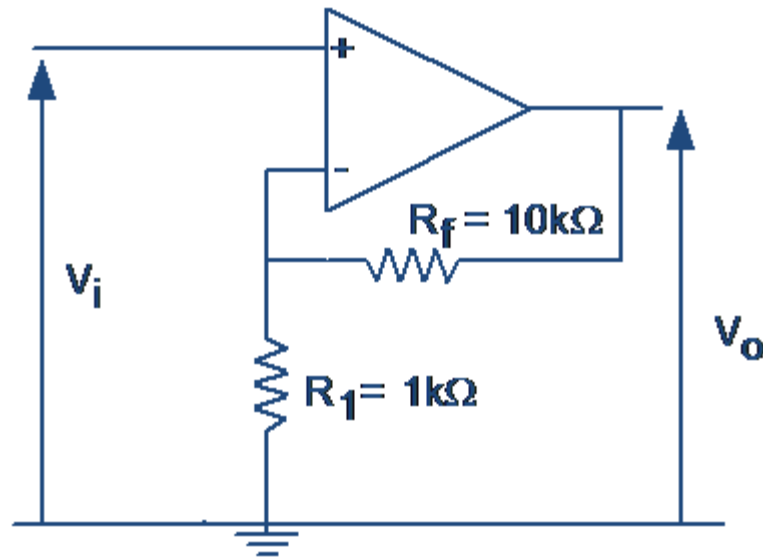Example 1


Given $V_i = \sin \omega t$, sketch V_o .



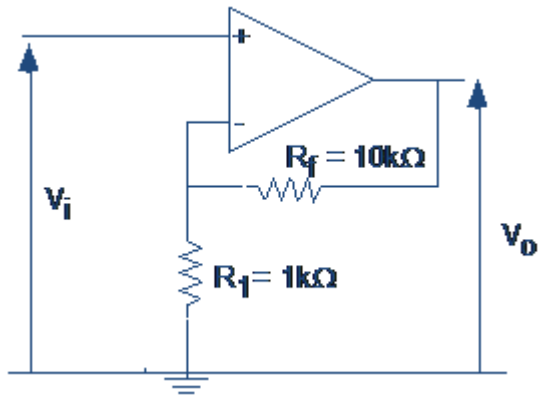


$$\frac{V_o}{V_{in}} = \frac{1+10}{1} = 11$$


Non Inverting Amp

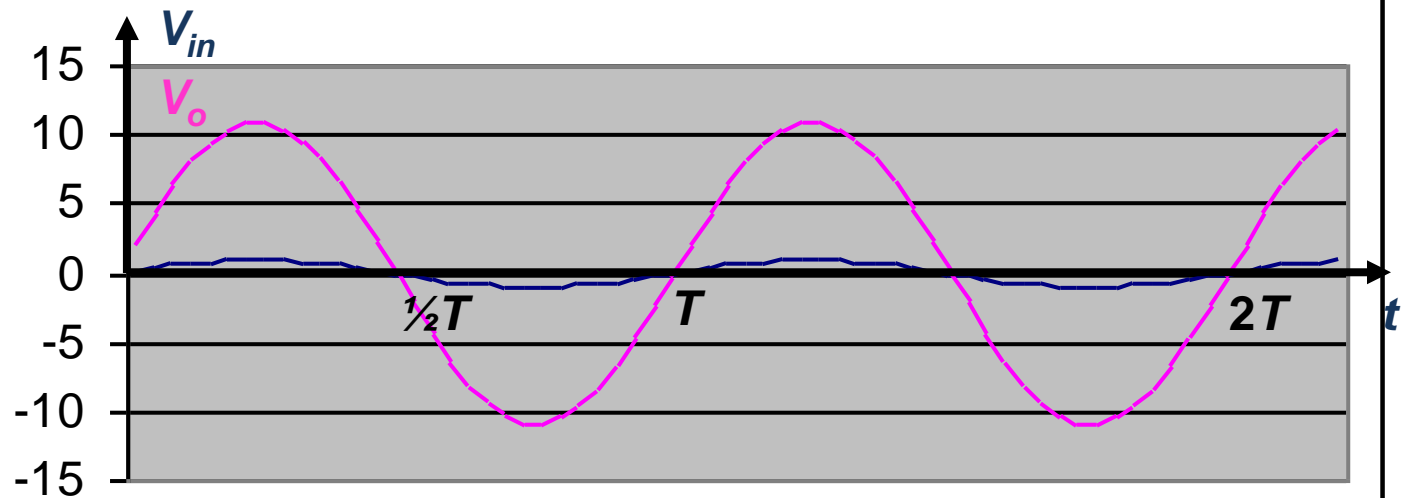

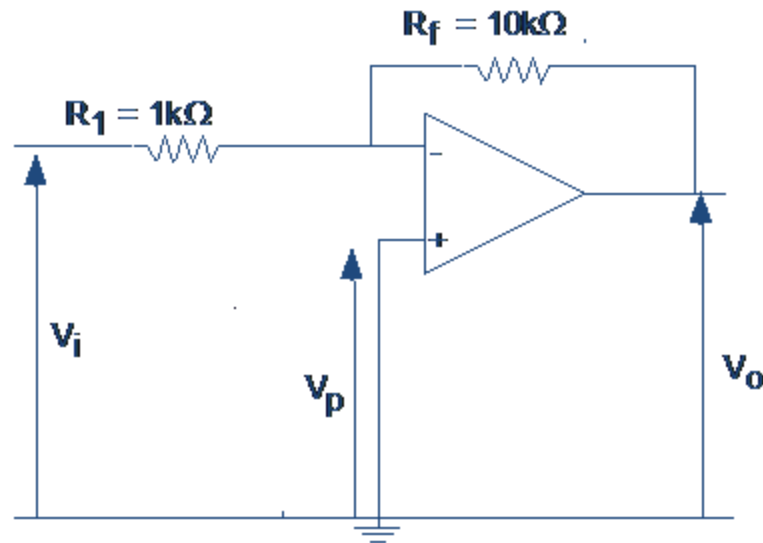Example 2


Given $V_i = \sin \omega t$, sketch V_o .



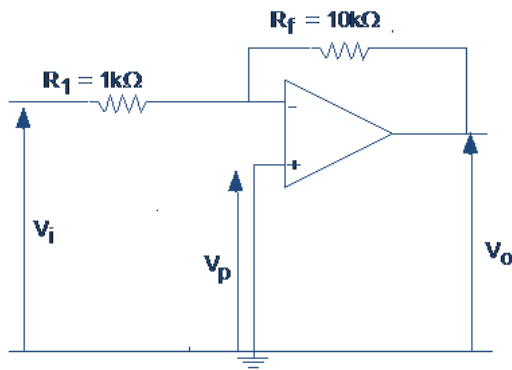


$$\frac{v_o}{v_i} = -\frac{R_f}{R_1} = -\frac{10}{1} = -10$$


Inverting Amp

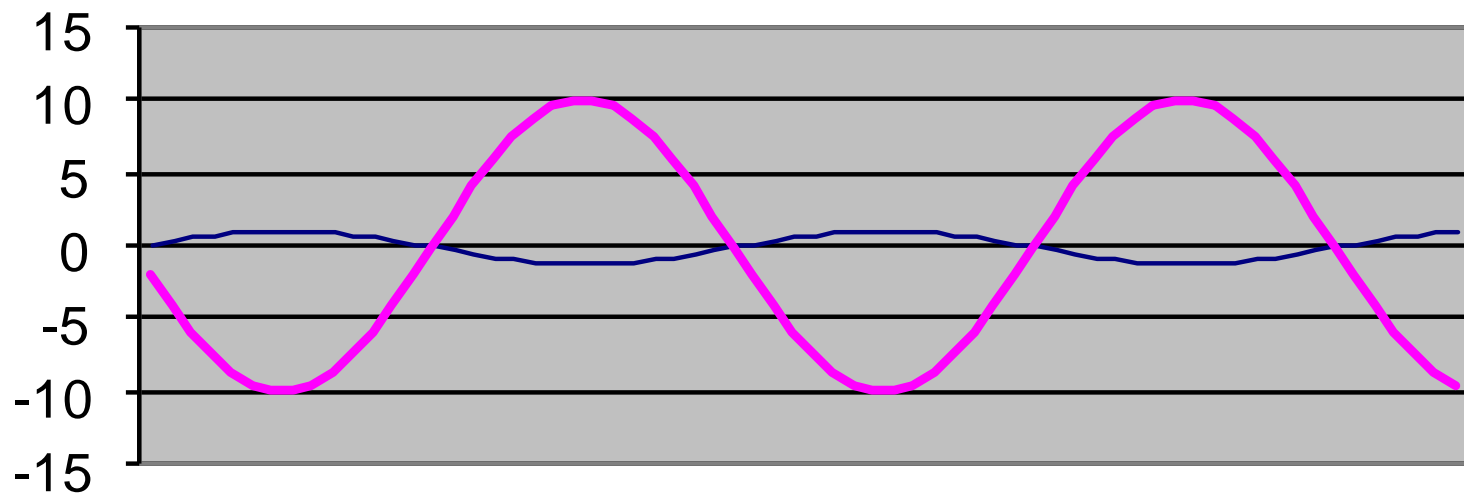

Example 3

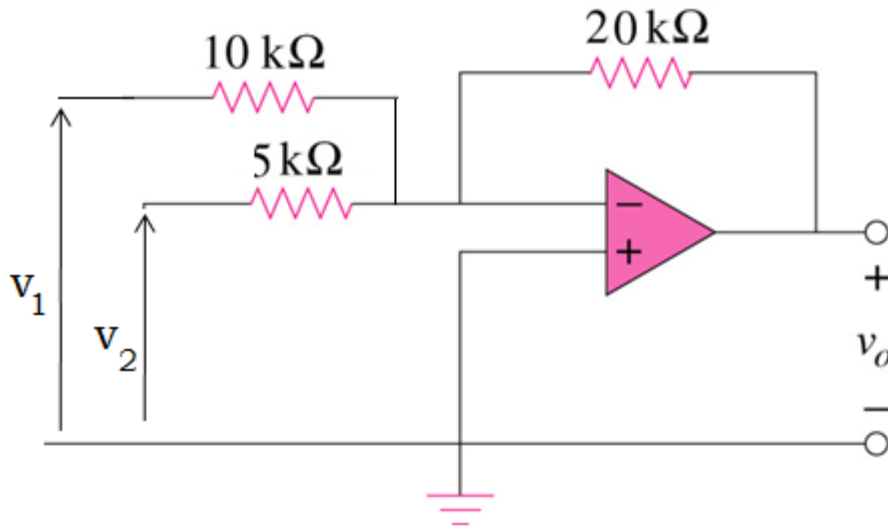



$$v_o = -\frac{20}{10}v_1 - \frac{20}{5}v_2 = -2v_1 - 4v_2$$

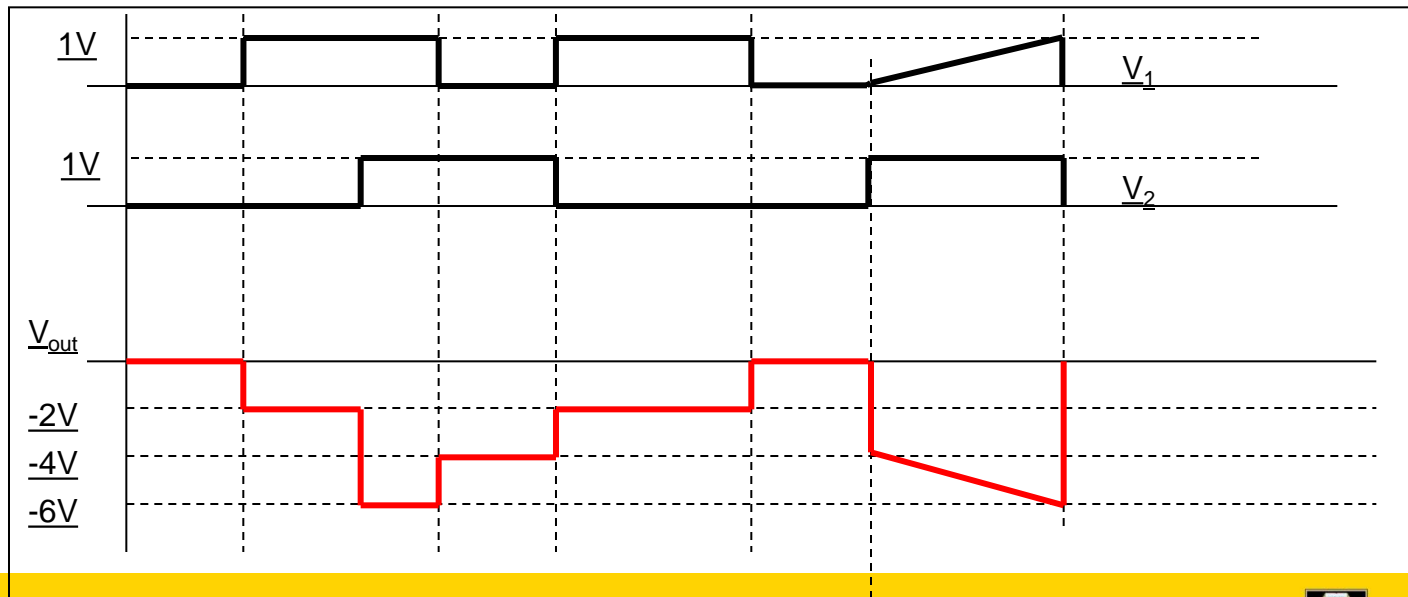

Example 4

Find the Transfer Function

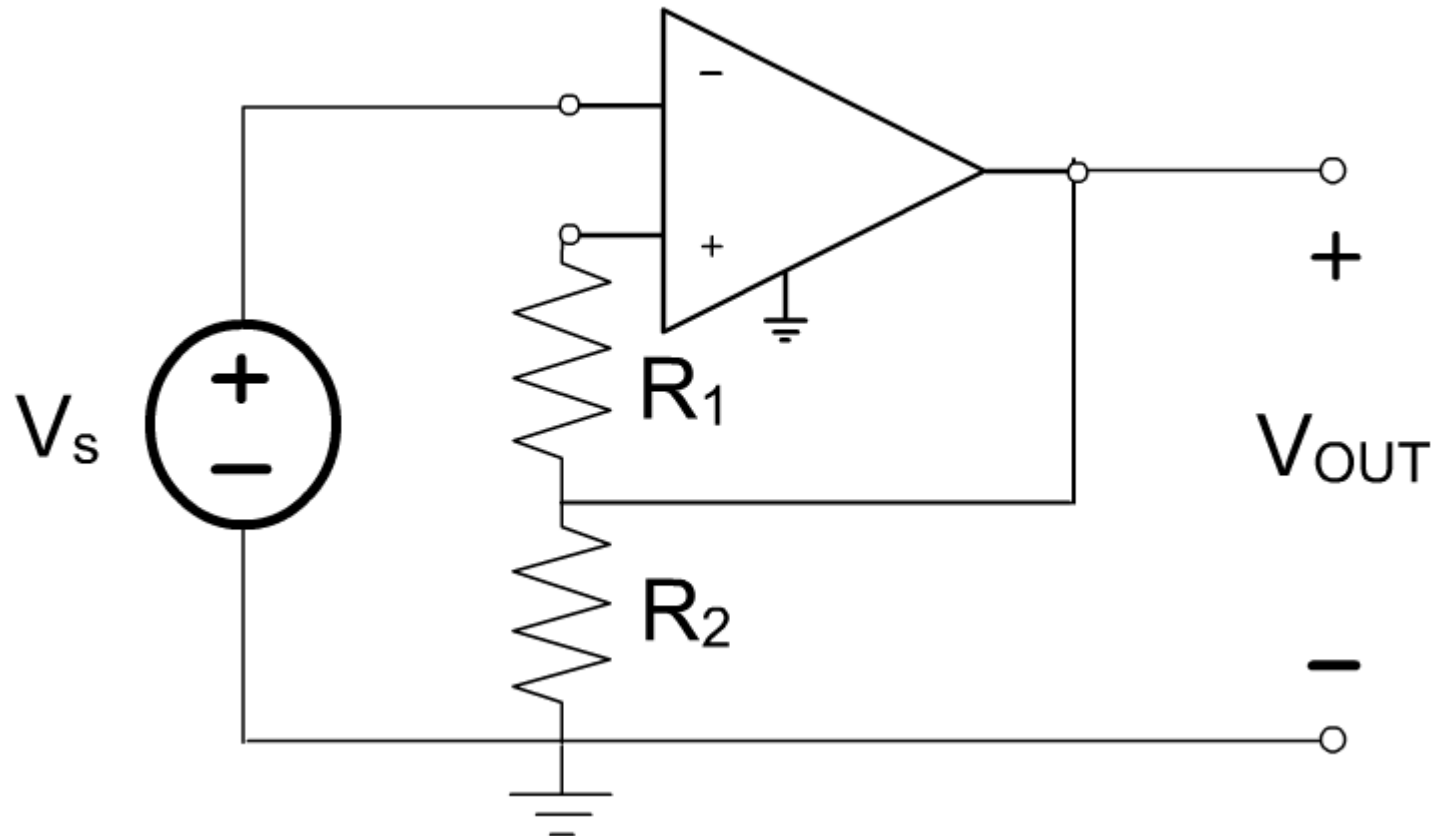

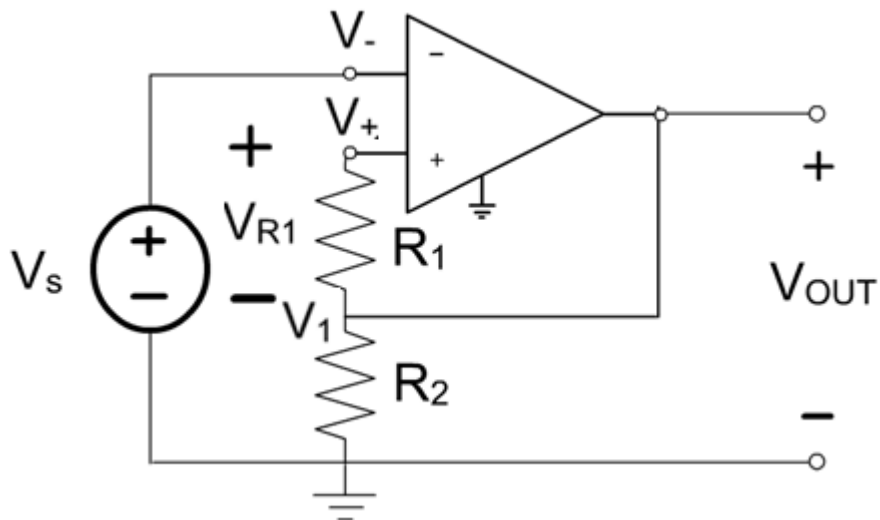

$$V_- = V_s$$

$$V_+ = V_-$$

$$I_+ = 0$$

$$V_{R1} = I_+ R_1 = 0$$

$$V_1 = V_+ + V_{R1} \\ = V_+$$

$$V_{OUT} = V_1 = V_s$$

So, Transfer Function = 1