

WEEK 2-2018

Combinational circuit I



Binary logic and Gates

- Transistors interconnected each other to form **logic gates**
- Each gate has inputs and an output. It performs a **specific logical operation** on its binary inputs and provides a binary value at the output.
- Inputs and output of a logic gate are designated by alphabetical variables .
- These variables can assume only 1 or 0 values and are known as **Binary variables**.

Basic logical operations

- There are three basic logical operations : **AND**, **OR**, and **NOT**.

AND

- represented by a dot or an absence of operation

$$Z = X \cdot Y = XY = X \wedge Y$$

- Z is 1 if and only if X=1 and Y=1; otherwise Z = 0

X · Y	X	Y	Z = X · Y
0 · 0 = 0	0	0	0
0 · 1 = 0	0	1	0
1 · 0 = 0	1	0	0
1 · 1 = 1	1	1	1

Truth Table
for AND gate

AND logical operation can be extended to more than two input binary variables.

Basic logical operations

OR

- represented by a plus symbol or “ \vee ”

$$Z = X + Y = X \vee Y$$

- Z is 1 if X=1 or Y=1; Z is 0 if X = 0 and Y= 0

X + Y	X	Y	X + Y
0+0 = 0	0	0	0
0+1 = 1	0	1	1
1+0 = 1	1	0	1
1+1 = 1	1	1	1

Truth Table
for OR gate

OR logical operation can be extended to more than two input binary variables.

Basic logical operations

NOT

- represented by a bar over the variable

$$Z = \bar{X}$$

- Z is 1 if X=0 and Z is 0 if X = 1

X
$\bar{0} = 1$
$\bar{1} = 0$

X	Z = \bar{X}
0	1
1	0

Truth Table
for NOT gate


Logic gates

- **Logical Gates** - Electrical circuits that implement logical operations.
- The input terminals accept voltage signals within allowable range (as a binary signals) and gives out at the output terminal a binary signals that also falls with in the allowable range.
- Intermediate values are crossed only during transitions from 0 to 1 or otherwise.
- Graphical (symbolical) representations of the three types of gates: **AND, OR, NOT**


Logic gates



AND gate

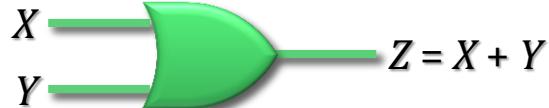

OR gate

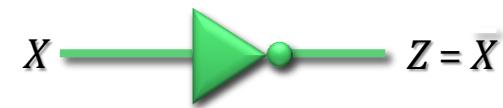


NOT gate (inverter)

- Time diagram (waveform behavior)



(AND) $X \cdot Y$

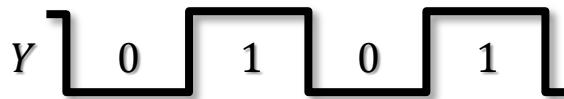


(OR) $X + Y$

(NOT) \bar{X}

Gate delay

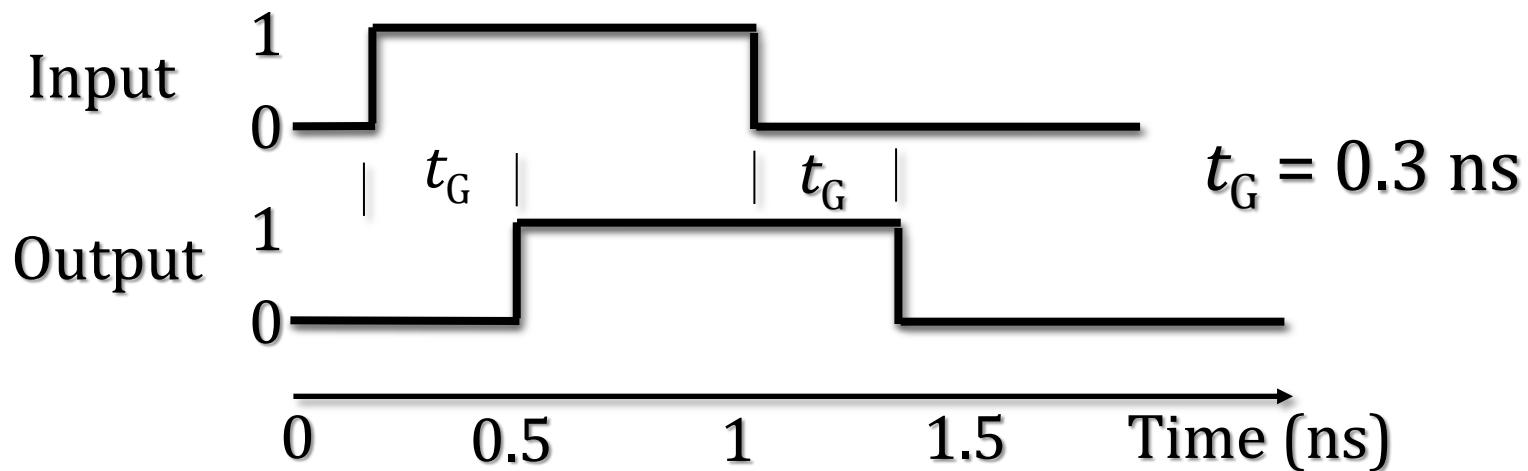- In reality, there is a gate delay
- Gate delay – the length of time it takes for an input changes to result in the corresponding output change.



- Gate delay is a function of **gate type, number of inputs, underlying technology, and circuit design of the gate.**

Boolean Algebra

- A *Boolean Algebra* is an algebra dealing with binary variables and logic operations.
- A *Boolean expression* is an algebraic expression formed by using binary variables, the constants 0 and 1, the logic operation symbols, and parentheses
- The order of evaluation in a Boolean expression:
(), NOT, AND, OR

Boolean function

- A *Boolean function* is a boolean equation consisting of a binary variable identifying the function followed by an equal sign and a boolean expression.

Boolean expression


$$L(D,X,A) = \underbrace{D\bar{X} + A}_{}$$

Boolean function or Boolean equation

- A boolean function can be transformed into a circuit diagram (logic diagram) composed of logic gates and interconnected by wires.

Boolean function

Logic Diagram

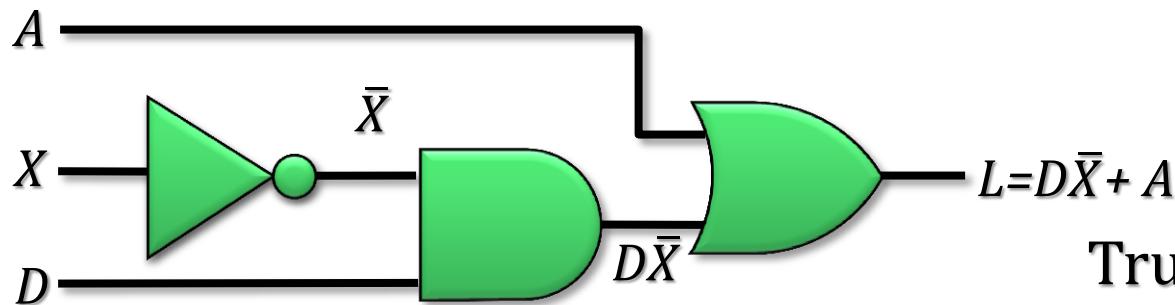

Truth Table

- A boolean function can be represented by a **truth table**

D	X	A	$L = D\bar{X} + A$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Boolean function

- There is **only one way** that a boolean function can be represented by a truth table
- The Boolean function, however, can be expressed by various boolean equations, which are not the same but equivalent. Eg. L and F have the same function.

$$L(D,X,A) = D\bar{X} + A$$

$$F(D,X,A) = D\bar{X} + AD + A\bar{D}$$

- The boolean equation dictates the interconnection of gates in the logic circuit diagram.
- Simpler expression reduces the number of gates and the number of inputs into the gates

Basic identities of boolean algebra

1. $X + 0 = X$	2. $X \cdot 1 = X$	Identity
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	Null
5. $X + X = X$	6. $X \cdot X = X$	Idempotence
7. $X + \bar{X} = 1$	8. $X \cdot \bar{X} = 0$	Complementarity
9. $\bar{\bar{X}} = X$		Involution

Basic identities of boolean algebra

$$10. Y+X = X+Y$$

$$11. Y \cdot X = X \cdot Y$$

Commutative

$$12. X + (Y + Z) = (X+Y) + Z$$

$$13. (XY)Z = X(YZ)$$

Associative

$$14. X (Y + Z) = XY + XZ$$

$$15. X + Y Z = (X + Y) (X + Z)$$

Distributive

$$16. \overline{X + Y} = \overline{X}\overline{Y}$$

$$17. \overline{XY} = \overline{X} + \overline{Y}$$

De morgan's law

Basic identities of boolean algebra

- Any expression can replace the variable X in all boolean identity.

Eg. $X + 1 = 1$

with $X = AB + C$

$$AB + C + 1 = 1$$

- Identity 10 -14 are similar to ordinary algebra.
However, Identity 15 does not hold in ordinary algebra.
- Identity 16 and 17 are De' morgan's rule and they are very important rules

X	Y	$\bar{X} + \bar{Y}$	\bar{XY}	$\overline{X+Y}$	$\bar{X}\bar{Y}$
0	0	1		1	
1	0	1		0	
0	1	1		0	
1	1	0		0	

Basic identities of boolean algebra

- De'morgan's law can be extended to three or more variables. The general De'morgan's theorem can be expressed as

$$\overline{X_1 + X_2 + \dots + X_n} = \overline{X_1} \overline{X_2} \dots \overline{X_n}$$

$$\overline{X_1 X_2 \dots X_n} = \overline{X_1} + \overline{X_2} + \dots + \overline{X_n}$$

Duality

- The *dual* of an algebraic expression is obtained by interchanging + and · and interchanging 0's and 1's
- Any Boolean theorem that can be proven is thus also proven for its dual!
- Note that previous identities appear in dual pairs
- Example:

$$XY + \bar{X}Z + YZ = XY + \bar{X}Z$$

Dual $(X+Y)(\bar{X} + Z)(Y+Z) = (X+Y)(\bar{X} + Z)$

Useful theorems of Boolean algebra

$X + XY = X$	$X(X + Y) = X$	Absorption
$XY + X\bar{Y} = X$	$(X + Y)(\bar{X} + Y) = X$	Minimization
$X + \bar{X}Y = X + Y$	$X(\bar{X} + Y) = XY$	Simplification
$XY + \bar{X}Z + YZ = XY + \bar{X}Z$	$(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$	Consensus

Proof of consensus theorem

- Example: Prove the Consensus Theorem

$$\begin{aligned} XY + \bar{X}Z + YZ &= XY + \bar{X}Z + YZ \cdot 1 && (2) \\ &= XY + \bar{X}Z + YZ(X + \bar{X}) && (7) \\ &= XY + \bar{X}Z + XYZ + \bar{X}YZ && (14) \\ &= XY + XYZ + \bar{X}Z + \bar{X}YZ && (10) \\ &= XY(1 + Z) + \bar{X}Z(1 + Y) && (14) \\ &= XY + \bar{X}Z && (3) \end{aligned}$$

Expression simplification

- A *literal* is a complemented or uncomplemented variable in a term
- Simplify the following expression to contain the smallest number of literals:

$$\begin{aligned} & AB + ACD + \overline{A}BD + A\overline{C}\overline{D} + \overline{A}\overline{B}CD \\ &= AB + \overline{A}BCD + ACD + A\overline{C}\overline{D} + \overline{A}BD \\ &= AB + \overline{A}BCD + AC(D + \overline{D}) + \overline{A}BD \\ &= AB + AC + \overline{A}BD = B(A + \overline{A}D) + AC \\ &= B(A + D) + AC \end{aligned}$$

- Only 5 literals!

Complement of a function

- The complement of a function F , \overline{F} , can be obtained in two ways:
 - By applying DeMorgan's theorem
 - By taking the dual of the function and complementing each literal

Example: $F = \overline{X}Y\overline{Z} + \overline{X}\overline{Y}Z$

Standard Forms

- *Standard forms* are standard ways to express Boolean functions
- Contain product terms (**Minterms**) and sum terms (**Maxterms**)
- Result in more desirable expression for circuit implementation

Minterms:

- Minterms are AND terms with every variable present in either true or complement form
- Every variable combination in a truth table has a corresponding minterm

Minterms

- For a function with n variables, there will be 2^n minterms
- The literals are listed in the same order for all minterms (usually alphabetically)

X	Y	Z	Product Term	symbols	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\bar{X}\bar{Y}\bar{Z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\bar{X}\bar{Y}Z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\bar{X}YZ$	m_2	0	0	1	0	0	0	0	0
0	1	1	$\bar{X}Y\bar{Z}$	m_3	0	0	0	1	0	0	0	0
1	0	0	$X\bar{Y}\bar{Z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$X\bar{Y}Z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$XY\bar{Z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	XYZ	m_7	0	0	0	0	0	0	0	1

Minterms

X	Y	Z	Product Term	symbols	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\bar{X}\bar{Y}\bar{Z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\bar{X}\bar{Y}Z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\bar{X}YZ$	m_2	0	0	1	0	0	0	0	0
0	1	1	$\bar{X}Y\bar{Z}$	m_3	0	0	0	1	0	0	0	0
1	0	0	$X\bar{Y}\bar{Z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$X\bar{Y}Z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$XY\bar{Z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	XYZ	m_7	0	0	0	0	0	0	0	1

- A variable in a minterm *is complemented for 0 and is not complemented for 1*
- The symbol index corresponds to the binary combination of the variables

Sum-of-Minterms Canonical Form

- Express a function as a sum of minterms
- Logical sum (*OR*) of all minterms where the function value is 1

- Example:

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Maxterms

- Similarly, maxterms are OR terms with every variable present
- In maxterms, a variable *is complemented for a 1 and not complemented for a 0*

X	Y	Z	Sum Term	symbols	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X + Y + Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X + Y + \bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X + \bar{Y} + Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X + \bar{Y} + \bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X} + Y + Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X} + Y + \bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X} + \bar{Y} + Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Maxterms

- The symbol index corresponds to the binary combination of the variables
- For a function with n variables, there will be 2^n maxterms

X	Y	Z	Sum Term	symbols	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X + Y + Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X + Y + \bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X + \bar{Y} + Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X + \bar{Y} + \bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X} + Y + Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X} + Y + \bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X} + \bar{Y} + Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Maxterms

- The literals are listed in the same order for all minterms (usually alphabetically)
- Every variables combination in a truth table has a corresponding minterm

X	Y	Z	Sum Term	symbols	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X + Y + Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X + Y + \bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X + \bar{Y} + Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X + \bar{Y} + \bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X} + Y + Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X} + Y + \bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X} + \bar{Y} + Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Product-of-Maxterms Canonical Form

- Express a function as a product of maxterms
- Logical product (*AND*) of all maxterms where the function value is 0

- Example:

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Minterms and Maxterms Relationship

- Review: DeMorgan's Theorem
- Two-variable example:

Function Complements

- The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the expression
- Alternatively, the complement of a function expressed as a sum of minterms is simply the product of maxterms with the same indices

Function Complement Example

- Find complement expressions for the function:

$$G(X, Y, Z) = \sum m(1, 3, 5, 7)$$

- As a sum of minterms:

- As a product of maxterms:

X	Y	Z	G
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Sum-of-Products

- *Sum of Products* form: equations are written as an OR of AND terms
- Similar to sum of minterms but does not need to contain all variables in every term
- Can be directly implemented as a *two-level circuit*

Sum-of-Products Implementation

- Example - the function:

$$F = \bar{Y} + \bar{X}YZ + XY$$

Product-of-Sums

- *Product of Sums* form: equations are written as an AND of OR terms
- Can also be implemented as a two-level circuit
- Example – the function:

$$F = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

is expressed as a POS

Cost Criteria

- Need a method to measure the complexity of a logic circuit
- Define the *Gate-Input Cost* as the number of inputs to the gates in the implementation
- Can be calculated directly from the equation corresponding to the circuit
- Only count distinct terms and complemented literals

Gate-Input Cost

- **Example:**

$$F = AB + \bar{C}(D + E)$$

- **The corresponding logic diagram:**

