
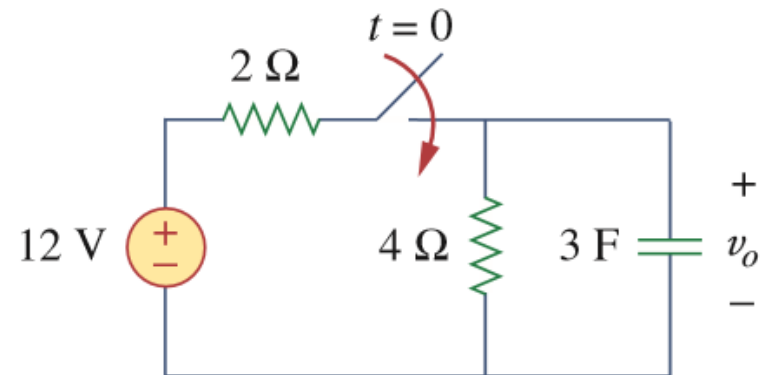


Weeks 1-6 Revision

Basis methods for circuit analysis

- Ohm's Law
- Voltage/Current Division Laws
- Kirchhoff's Current Law (KCL)
- Kirchhoff's Voltage Law (KVL)
- Nodal Analysis
- Mesh Analysis
- Superposition
- Source Transformation
- Thévenin's Theorem
- Norton's Theorem
- Maximum Power Transfer
- Capacitor, Inductor, Transient analysis

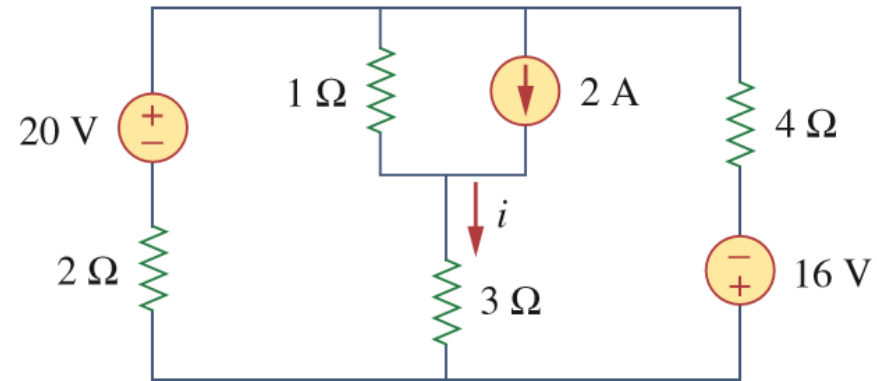


Weeks 7-12 Contents

AC signals (sinusoid signal)

- Phasor
- AC Power

$$20 \cos(4t - 15^\circ) \text{ V}$$

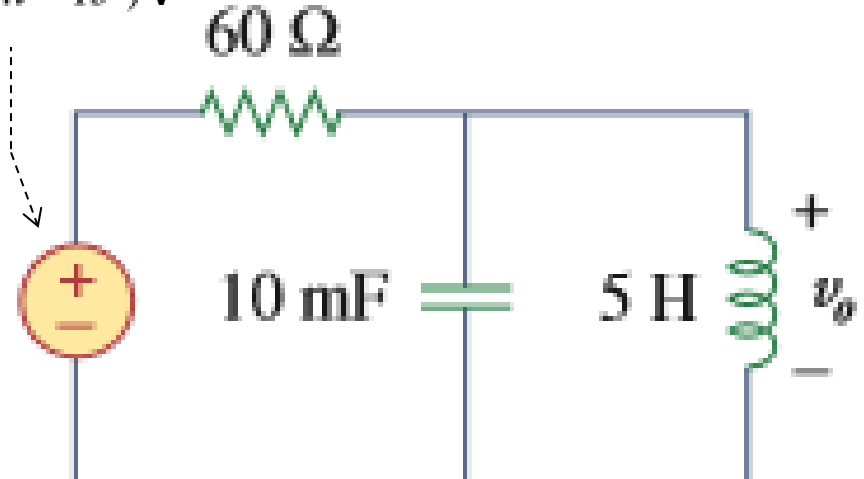

Other electrical/electronic elements

- OpAmp
- Transformers

Combination logic, digital circuit analysis

The basic laws & analysis methods in weeks 1-4 can be applied in all electrical circuits and will be used to analyse the circuit with AC input source



Lecture 9: Sinusoids and Phasors

ELEC1111 Electrical and Telecommunications Engineering

Never Stand Still

Faculty of Engineering

School of Electrical Engineering and Telecommunications

Objectives

- Introduce sinusoids and phasors for AC circuit analysis
- Derive phasor relationships for circuit elements
- Introduce Impedance and Admittance
- Derive Kirchhoff's current and voltage laws in the frequency domain

Sinusoids

➤ Time varying signals with the form of a sine or cosine function

- Common in nature:
 - Pendulum motion
 - Vibration of a string
 - Natural response of second order systems
- Easy to generate and transmit
 - Electrical machines (generators)
 - Oscillators
- Used in Fourier analysis,
- Easy to handle mathematically

$$v(t) = V_m \sin \omega t \qquad \text{period } T = \frac{2\pi}{\omega}$$

Sinusoids



$$v(t) = V_m \sin \omega t$$

➤ Sinusoids are periodic functions, satisfying

$$v(t + nT) = v(t)$$

for all t and all integer values of n .
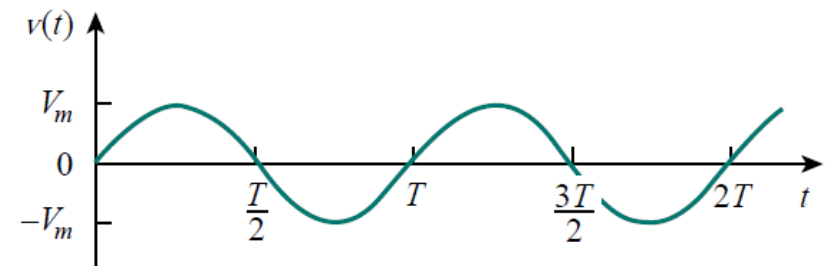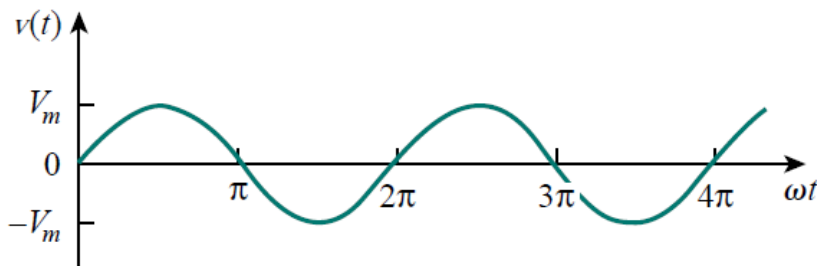
$$\begin{aligned} v(t + nT) &= V_m \sin \omega(t + nT) = V_m \sin \omega(t + n \frac{2\pi}{\omega}) \\ &= V_m \sin(\omega t + 2\pi n) = V_m \sin(\omega t) = v(t) \end{aligned}$$



Sinusoids

- Can be expressed in either a sine or a cosine form.

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

- Sine to cosine form transformation and vice-versa

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

How to Sum Sinusoids


➤ Sum DC voltages: $V_o = V_1 + V_2 = 3V + 5V = 8V$

➤ Sum Sinusoid voltages:

$$v_o(t) = v_1(t) + v_2(t) = 3\sin(4\omega t + \pi/3) + 5\sin(4\omega t + \pi/4) = ?$$

Sinusoids

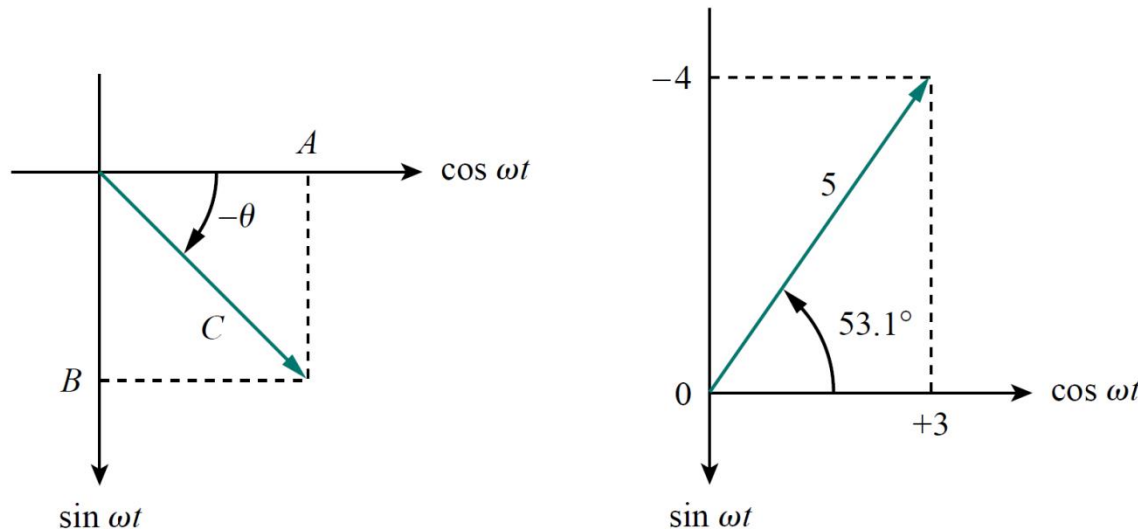- Sinusoids can be added and subtracted using a graphical approach



$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$

$$C = \sqrt{A^2 + B^2} \quad \theta = \tan^{-1} \frac{B}{A}$$

Phasors

- A phasor is a complex number that represents the amplitude and the phase of a sinusoid
 - A convenient way to express sinusoids.

- A complex number can be written in three forms

- Rectangular


$$z = x + jy$$

- Polar

$$z = r \angle \phi$$

- Exponential

$$z = re^{j\phi}$$

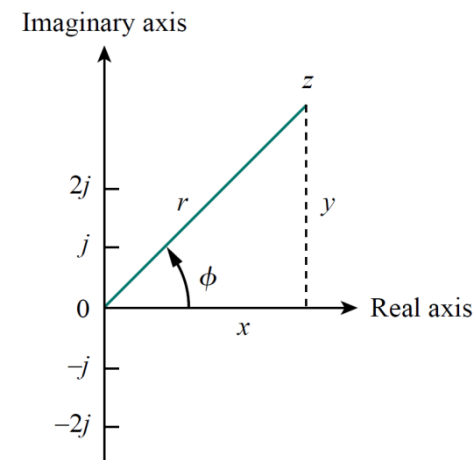

Phasors

- Rectangular to polar

$$r = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1} \frac{y}{x}$$


- Polar to rectangular

$$x = r \cos \phi \quad y = r \sin \phi$$

$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

- Euler's Identity
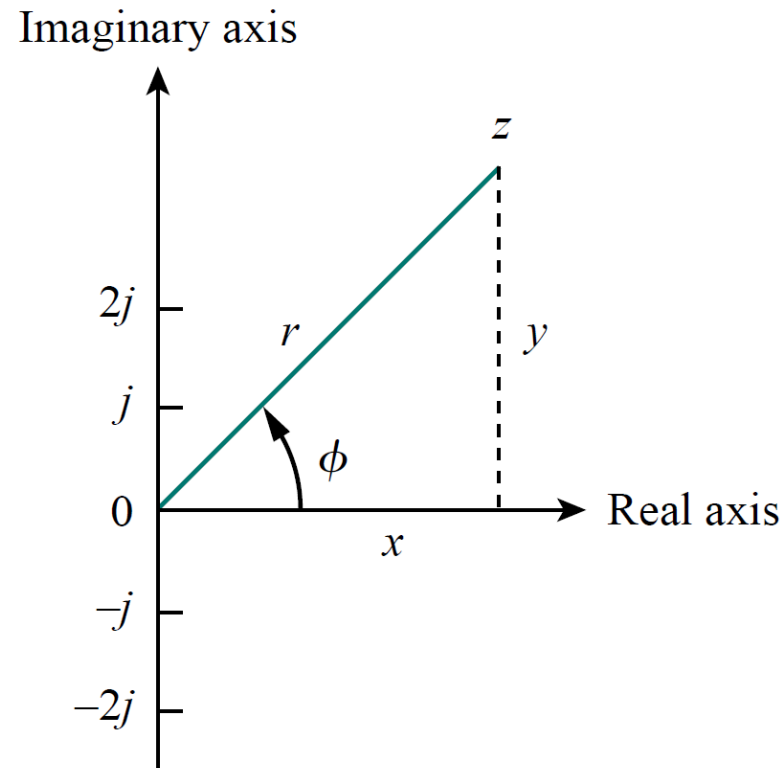
$$e^{\pm j\phi} = \cos \phi \pm j \sin \phi$$



Example

- Show the following numbers in phasor diagram

$$\mathbf{V}_1 = 5\angle 30^\circ$$

$$\mathbf{V}_2 = 5\angle -60^\circ$$

$$\mathbf{V}_3 = 3 + j2$$

$$\mathbf{V}_4 = -3 + j2$$


$$\mathbf{V}_5 = -3 - j2$$

Phasors

$$V_m e^{j(\omega t + \phi)} = \underbrace{V_m \cos(\omega t + \phi)}_{\text{Real}} + j \underbrace{V_m \sin(\omega t + \phi)}_{\text{Imaginary}}$$

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re}(V_m e^{j(\omega t + \phi)}) = \text{Re}(V_m e^{j\phi} e^{j\omega t})$$
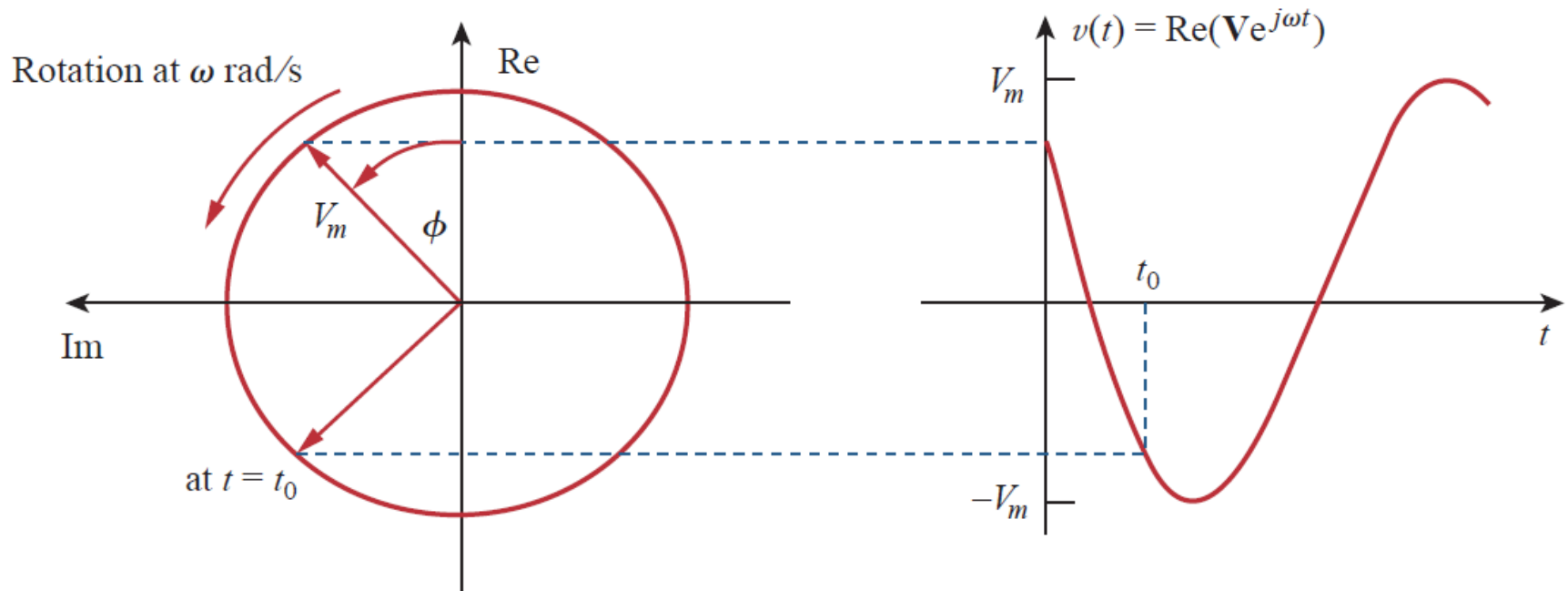
$$v(t) = \text{Re}(\mathbf{V} e^{j\omega t})$$




Phasor diagram

- A phasor has a magnitude and phase, behaves as a vector and can be represented graphically in a phasor diagram

$$v(t) = V_m \cos(\omega t + \phi) \Leftrightarrow \mathbf{V} = V_m \angle \phi$$

time domain

phasor domain

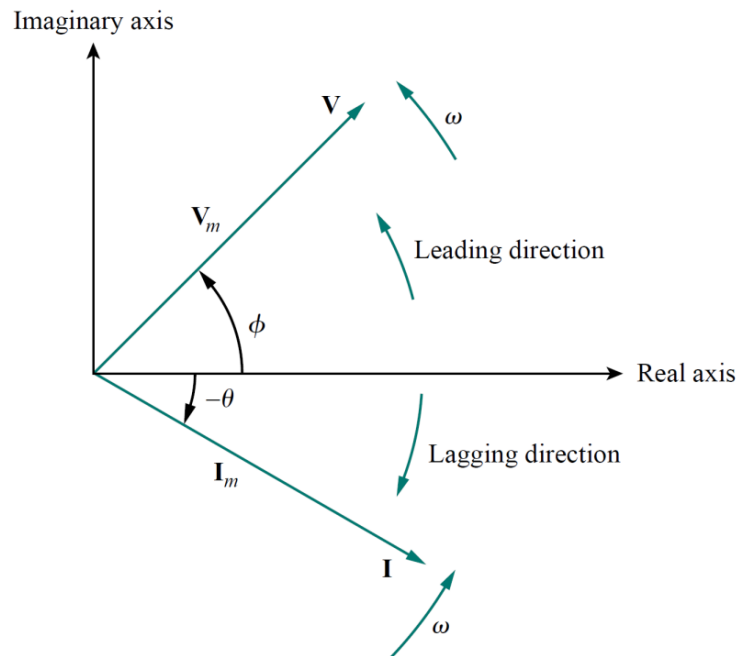

Phasor diagram

$$v(t) = V_m \cos(\omega t + \phi)$$

- Differentiating a sinusoid is equivalent to multiplying its corresponding phasor by $j\omega$


$$\frac{dv}{dt} = -\omega V_m \sin(\omega t + \phi) = \omega V_m \cos(\omega t + \phi + 90^\circ)$$

$$= \text{Re}(\omega V_m e^{j\omega t} e^{j\phi} e^{j90^\circ}) = \text{Re}(j\omega \mathbf{V} e^{j\omega t})$$

- Integrating a sinusoid is equivalent to dividing its corresponding phasor by $j\omega$.
- Adding sinusoids of the same frequency is equivalent to adding their corresponding phasors.

Phasor diagram

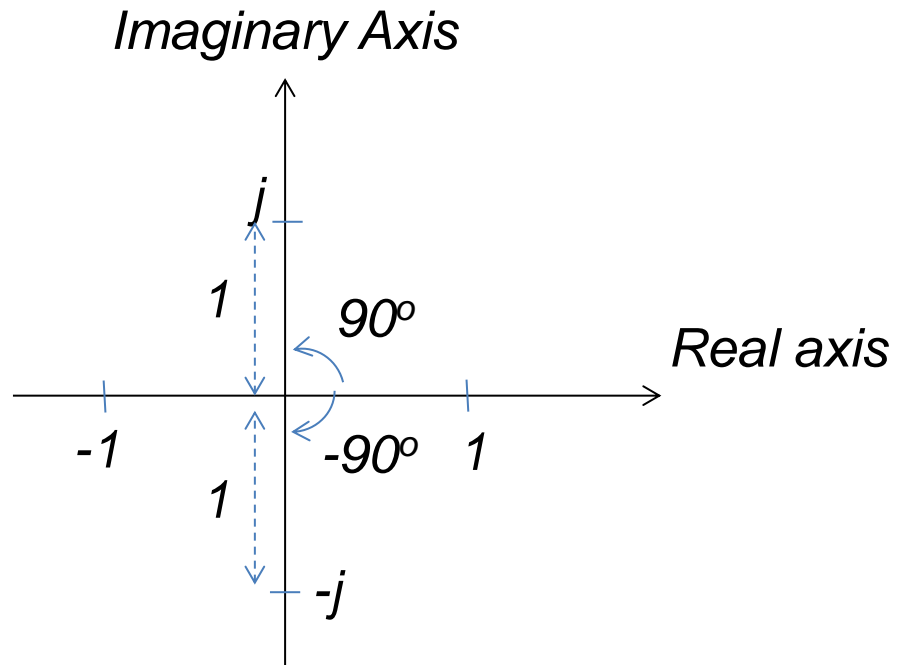➤ Note: $-\sin(\omega t + \phi) = \cos(\omega t + \phi + 90^\circ) = j \cos(\omega t + \phi)$



$$e^{j90^\circ} = \cos(90^\circ) + j \sin(90^\circ) = j = 1 \angle 90^\circ$$

$$e^{-j90^\circ} = \cos(-90^\circ) + j \sin(-90^\circ) = -j = 1 \angle -90^\circ$$

$$-1 = \cos(180^\circ) + j \sin(180^\circ) = e^{j180^\circ} = 1 \angle 180^\circ = 1 \angle -180^\circ$$

Phasor relationships for circuit elements

- Transform the voltage-current relationship of circuit elements from the time domain to the frequency domain.




- Resistor

$$i = I_m \cos(\omega t + \phi) \rightarrow I = I_m \angle \phi$$

$$v = iR = RI_m \cos(\omega t + \phi)$$

$$\mathbf{V} = RI_m \angle \phi$$

$$\mathbf{V} = R\mathbf{I}$$

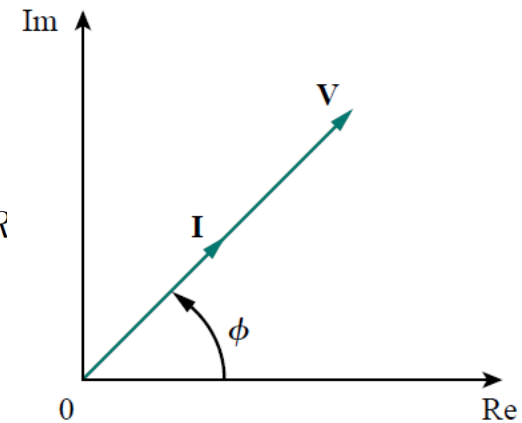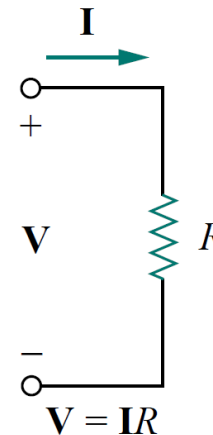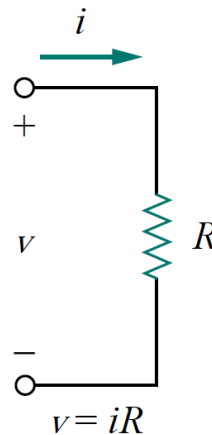

Phasor relationships for circuit elements

➤ Inductor



$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

$$v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

$$\mathbf{V} = \omega L I_m e^{j(\phi + 90^\circ)} = \omega L I_m e^{j\phi} e^{j90^\circ} = \omega L I_m \angle(\phi + 90^\circ)$$

$$\mathbf{V} = j\omega L \mathbf{I}$$

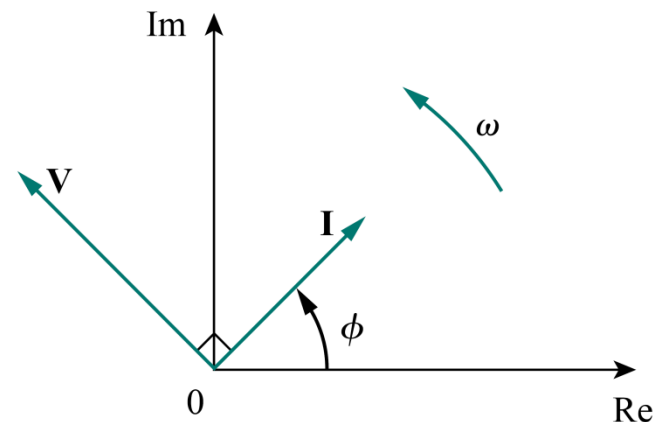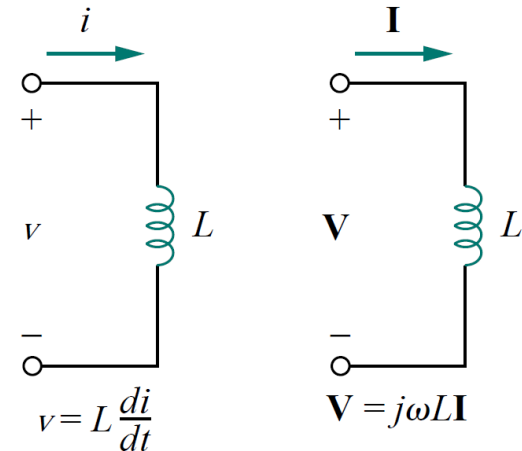➤ Current lags (behind) the voltage by 90 degrees





Phasor relationships for circuit elements

➤ Capacitor

$$i = C \frac{dv}{dt}$$

$$\mathbf{I} = j\omega C \mathbf{V} \Rightarrow \mathbf{V} = \frac{\mathbf{I}}{j\omega C}$$

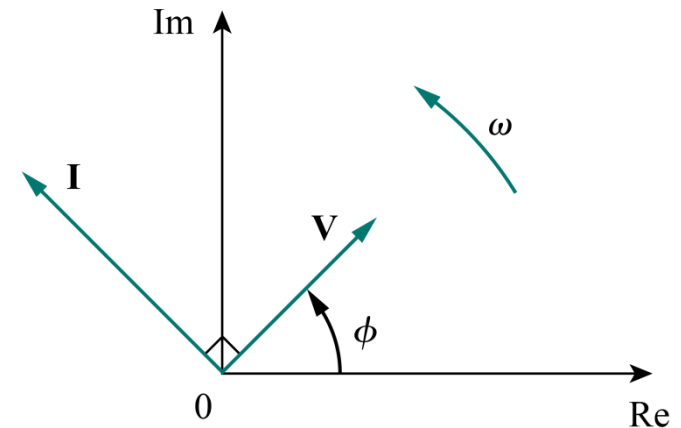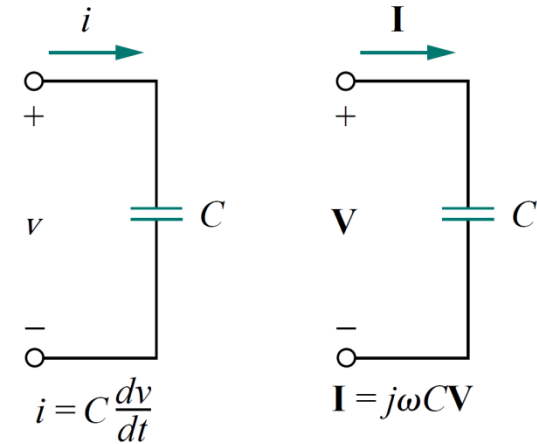- The current leads (advances) the voltage 90 degrees.
- Convention to give the current relative to the voltage.



Impedance and Admittance

- Impedance **Z** of a circuit is defined as the ratio of the phasor voltage **V** to the phasor current **I**, measured in Ohms (Ω).

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}}$$

- The impedance represents the opposition of the circuit to the flow of sinusoidal current.
- Admittance is the reciprocal of impedance, measured in Siemens (S).

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{\mathbf{I}}{\mathbf{V}}$$

Impedance and Admittance

Resistor

$$\mathbf{V} = R\mathbf{I}$$

$$\frac{\mathbf{V}}{\mathbf{I}} = R$$

Inductor



$$\mathbf{V} = j\omega L\mathbf{I}$$

$$\frac{\mathbf{V}}{\mathbf{I}} = j\omega L$$

Capacitor

$$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$$
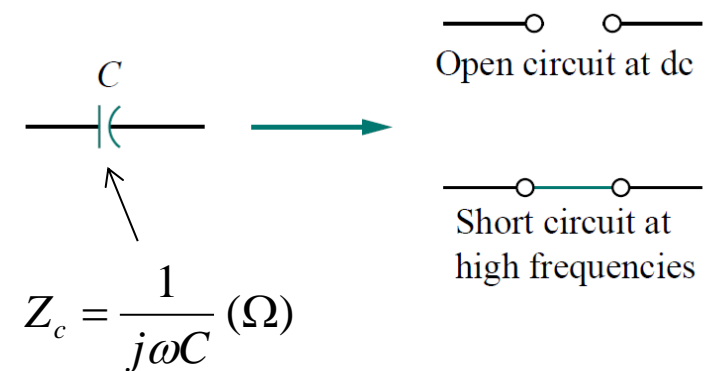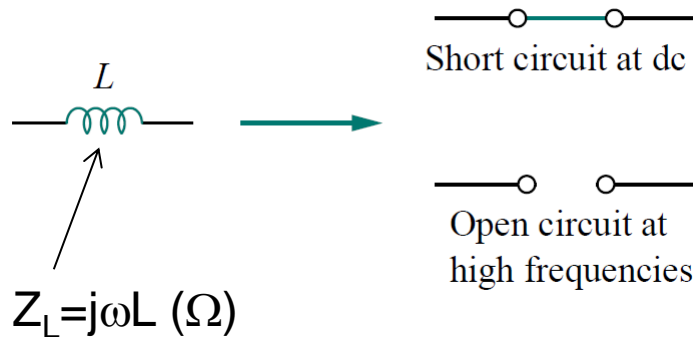
$$\frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C}$$



Impedance and Admittance

➤ Impedance

$$\mathbf{Z} = R + jX$$

Where R is the resistance and X is the reactance

Impedance and Admittance

➤ Admittance

$$\mathbf{Y} = G + jB$$

Where G is the conductance and B the susceptance.

$$G + jB = \frac{1}{R + jX}$$

$$G = \frac{R}{R^2 + X^2} \qquad B = -\frac{X}{R^2 + X^2}$$

Kirchhoff's laws in the frequency domain

➤ Kirchhoff's Voltage Law

- Considering the voltages across a closed loop

$$v_1 + v_2 + \dots + v_n = 0$$

- In the sinusoidal state

$$V_{m1} \cos(\omega t + \theta_1) + V_{m2} \cos(\omega t + \theta_2) + \dots + V_{mn} \cos(\omega t + \theta_n) = 0$$

which can be written as

$$\text{Re}[(\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n)e^{j\omega t}] = 0$$

And since the exponential term cannot be equal to zero

$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$$

Kirchhoff's laws in the frequency domain

➤ Kirchhoff's Current Law

- Similarly to KVL, considering the currents on a node

$$i_1 + i_2 + \dots + i_n = 0$$

and in the phasor form for frequency domain representation

$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0$$


- Based on the frequency domain forms of the KVL and KCL, impedance combination, nodal and mesh analysis, superposition and source transformation can be easily performed

Impedance combinations


➤ Impedances connected in series

$$\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_N = \mathbf{I}(\mathbf{Z}_1 + \mathbf{Z}_2 + \dots + \mathbf{Z}_N)$$
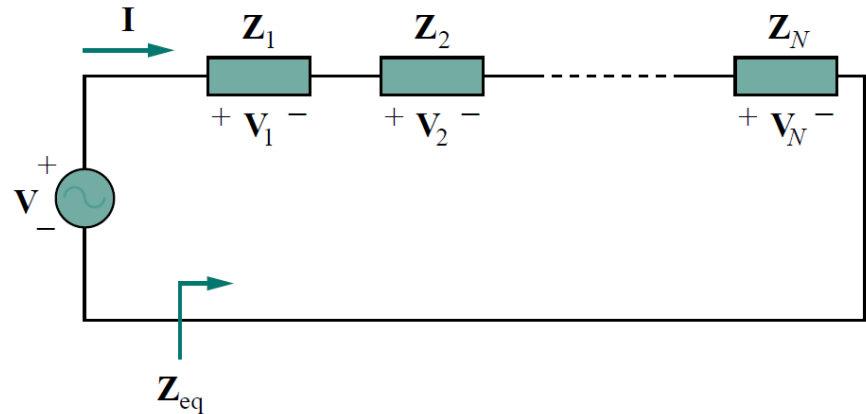
$$\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2 + \dots + \mathbf{Z}_N$$



➤ Voltage divider

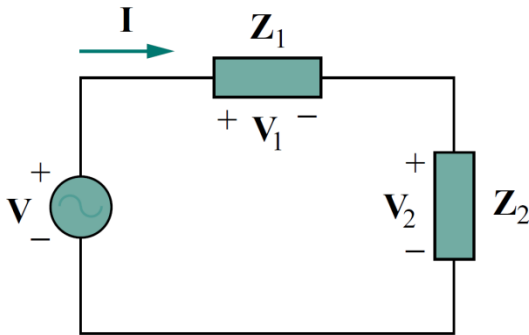

$$\mathbf{V}_1 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V} \quad \mathbf{V}_2 = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}$$



Impedance combinations

- Impedances connected in parallel

$$\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_N = \mathbf{V} \left(\frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \dots + \frac{1}{\mathbf{Z}_N} \right)$$

$$\frac{1}{\mathbf{Z}_{eq}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \dots + \frac{1}{\mathbf{Z}_N}$$

- Current divider

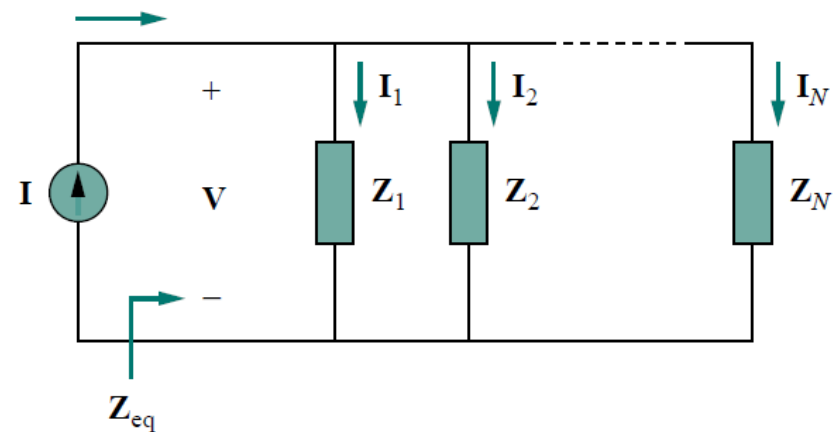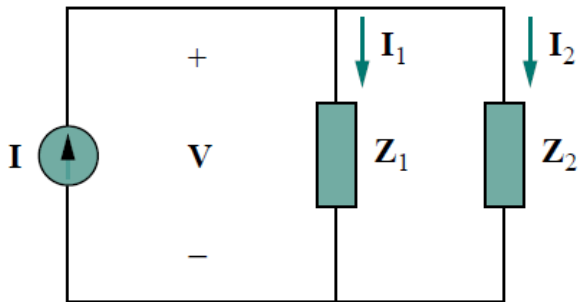


$$\mathbf{I}_1 = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I} \quad \mathbf{I}_2 = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{I}$$

Applications


➤ Phase shifters

- Used to correct undesirable phase-shift or to produce a required phase shift in signal.
- Simplest configuration of an RC circuit

$$\theta = \tan^{-1} \frac{X}{R}$$

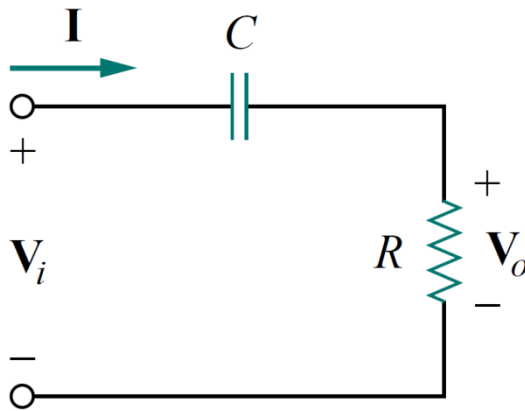

Leading arrangement

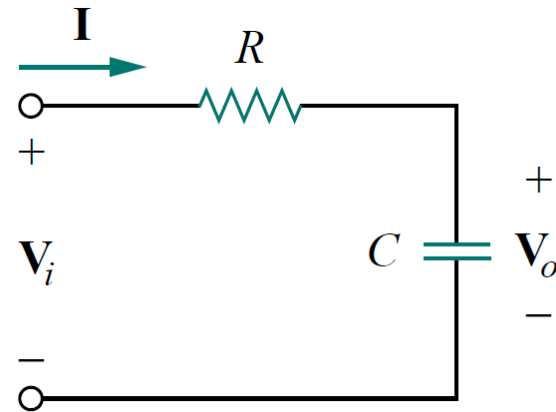


Lagging arrangement

Applications


➤ Phase shifters

- Used to correct undesirable phase-shift or to produce a required phase shift in signal.
- Simplest configuration of an RC circuit

$$\theta = \tan^{-1} \frac{X}{R}$$

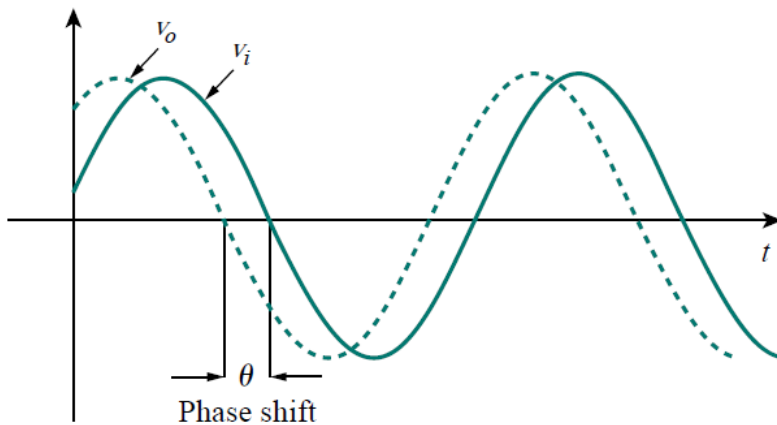

Leading arrangement

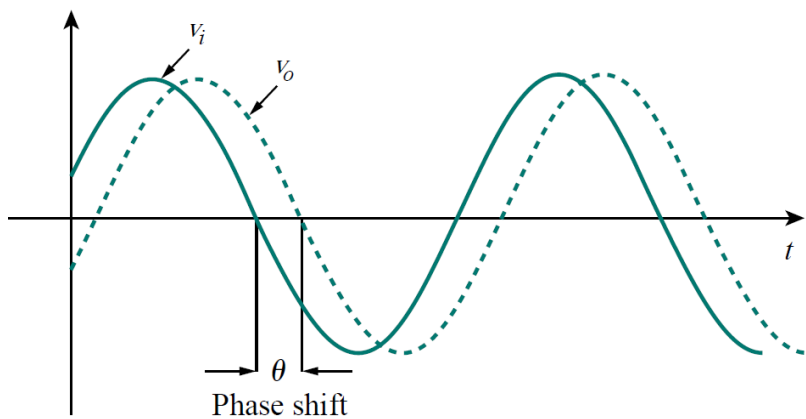

Lagging arrangement

Applications

➤ AC Bridges


- Used in measurements of inductances and capacitances of elements.
- In a general configuration, the bridge is balanced when no current flows through the meter.
- In a balanced bridge

$$\mathbf{V}_1 = \mathbf{V}_2$$

$$\mathbf{V}_1 = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}_s \quad \mathbf{V}_2 = \frac{\mathbf{Z}_x}{\mathbf{Z}_3 + \mathbf{Z}_x} \mathbf{V}_s$$

hence

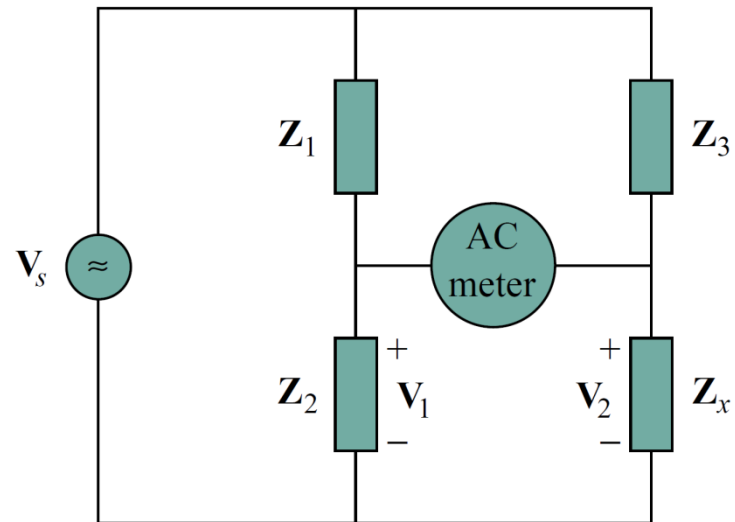
$$\frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{\mathbf{Z}_x}{\mathbf{Z}_3 + \mathbf{Z}_x} \Rightarrow \mathbf{Z}_x = \frac{\mathbf{Z}_3}{\mathbf{Z}_1} \mathbf{Z}_2$$



Applications

- AC bridge configuration for measuring capacitance (C)

$$C_x = \frac{R_2}{R_1} C_s$$

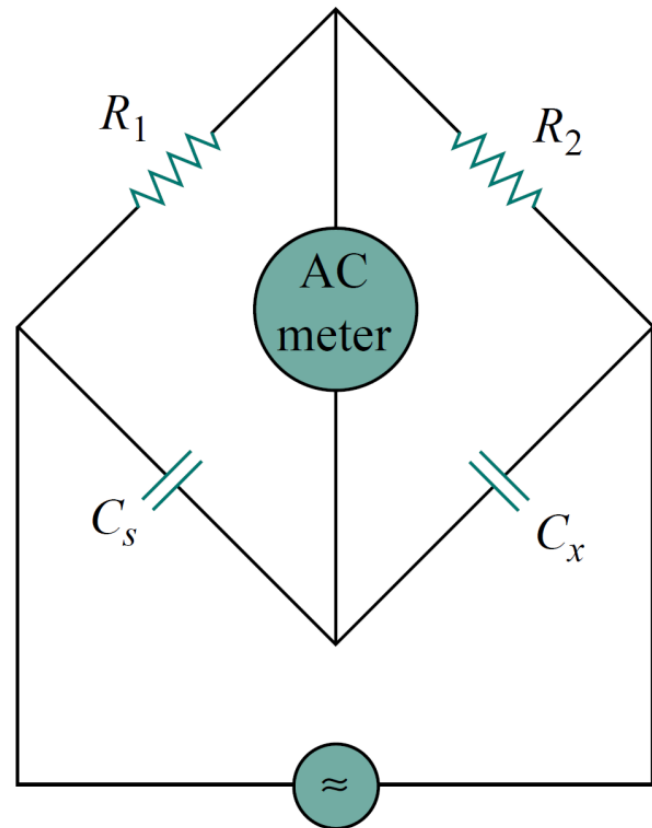


Applications

- AC bridge configuration for measuring inductance (L)

$$L_x = \frac{R_2}{R_1} L_s$$

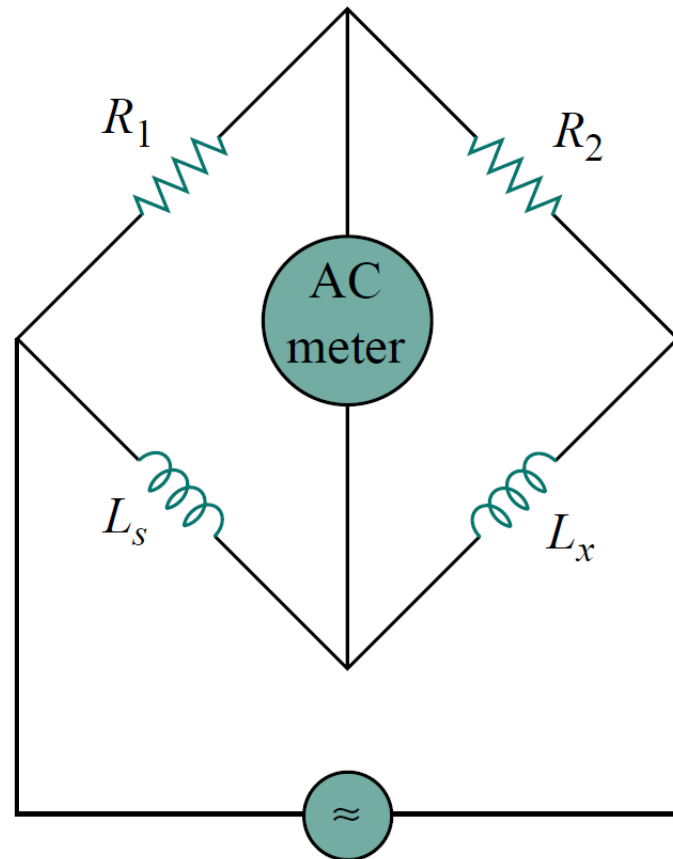- Balancing of the bridges is not affected by the frequency of the AC source.



Summary

- Sinusoids and phasors
 - Application in the analysis of AC circuits
- Phasor relations for circuit elements
 - Resistor
 - Inductor
 - Capacitor
- Impedance and Admittance
- KCL and KVL in the frequency domain
- Applications of RLC circuits with AC signals


Sinusoidal steady-state analysis

➤ Steps to analyze AC circuits

1. Transform the circuit to the frequency domain.
2. Solve the problem using circuit techniques learnt previously.
 - Analysis is similar to the DC circuit analysis but uses complex numbers.
3. Transform the resulting phasor to the time domain.


Example 1

Determine $v(t)$ and $i(t)$. Show V and I in phasor diagram

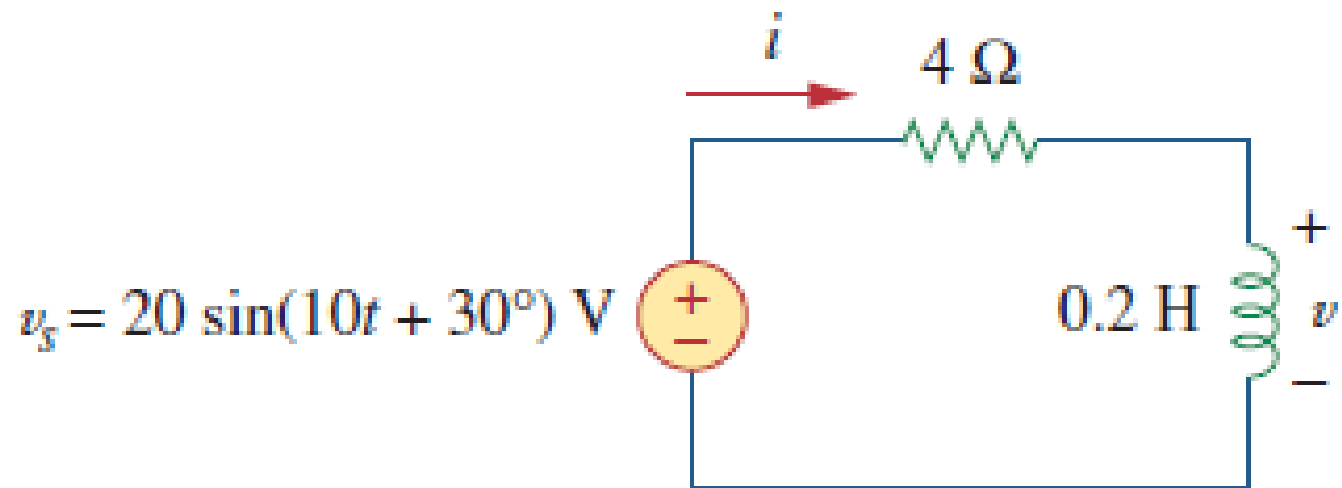


Example 2

Determine $v(t)$

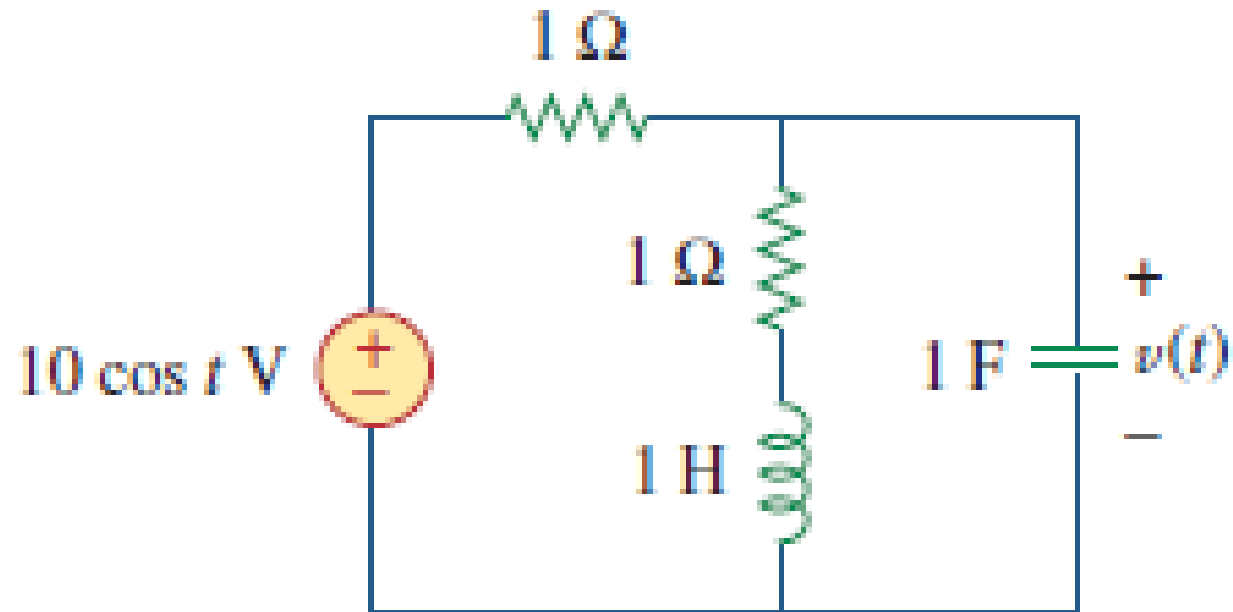

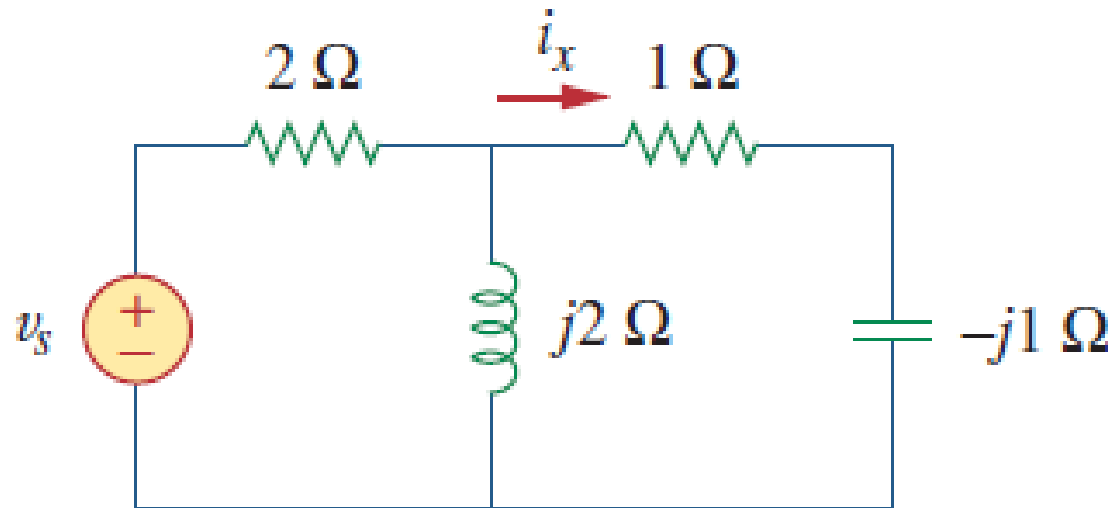Example 3

Find $v_s(t)$ in the following circuit if it is known that the current $i_x(t)=0.5\sin 200t$ A



Ans: $v_s(t)=1.41\sin(200t-15^\circ)V$

Example 4

$v_1(t) = 30\sin(10t + 60^\circ)\text{V}$ and

$v_2(t) = 40\cos(10t - 45^\circ)\text{V}$.

Which voltage is leading and in how many degree?

Ans: v_2 leads v_1 by 15°