



Lecture 3: Basic Circuit Laws

ELEC1111 Electrical and Telecommunications Engineering

Never Stand Still

Faculty of Engineering


School of Electrical Engineering and Telecommunications

CONTENTS

- 1. Circuit Elements**
- 2. Circuit Variables**
- 3. Ohm's Law**
- 4. Series and Parallel Resistors**
- 5. Voltage Division**
- 6. Current Division**

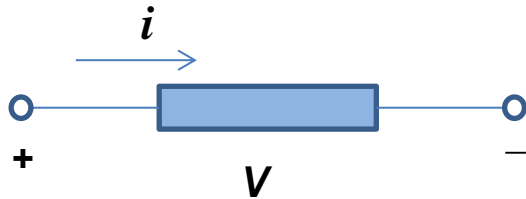1. CIRCUIT ELEMENTS


- ✓ **Passive element** – absorbs energy, so that the total energy delivered to it from the rest of the circuit is non-negative.



$$w = \int_{-\infty}^t v \cdot i \, d\tau \geq 0 \text{ for all values of } t$$

A resistor is a passive element

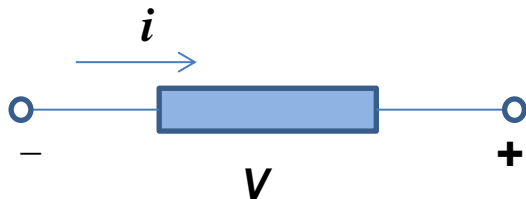- ✓ **Active element** – capable of supplying energy.




$$w = \int_{-\infty}^t v \cdot i \, d\tau > 0 \text{ for at least one value of } t$$

e.g. batteries and generators

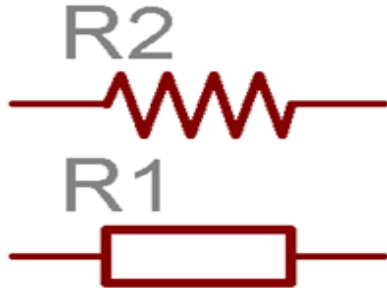1. CIRCUIT ELEMENTS

Resistors

- ✓ **Resistance** – physical property of a circuit element that impedes the flow of charge. The element is a **resistor**.



- ✓ **Resistivity** – a measure of the ability to resist the flow of charge by a certain material.

Copper – a good conductor, low resistivity


Polystyrene – a good insulator, high resistivity

Silicon – a good semi-conductor, intermediate resistivity

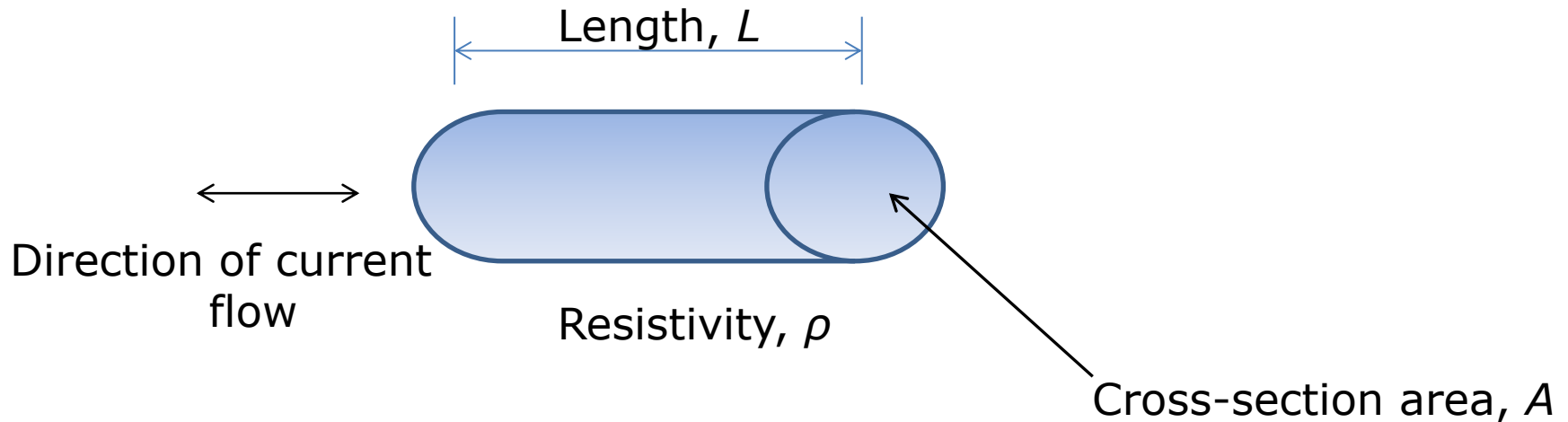1. CIRCUIT ELEMENTS

Resistors

- ✓ Resistance of a conducting wire of uniform cross-section:



$$R = \frac{\rho L}{A}$$


1. CIRCUIT ELEMENTS

Independent voltage source


- ✓ Provides a specified voltage which is **independent of current through it** or any other circuit variables.
- ✓ It is an **ideal source**, used to approximate a practical voltage source.
- ✓ No practical source is truly independent.

1. CIRCUIT ELEMENTS


Symbols

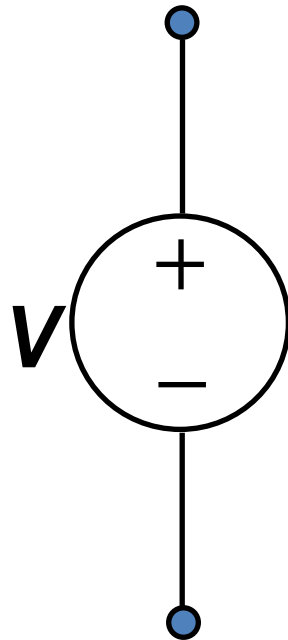

(DC)
voltage
source

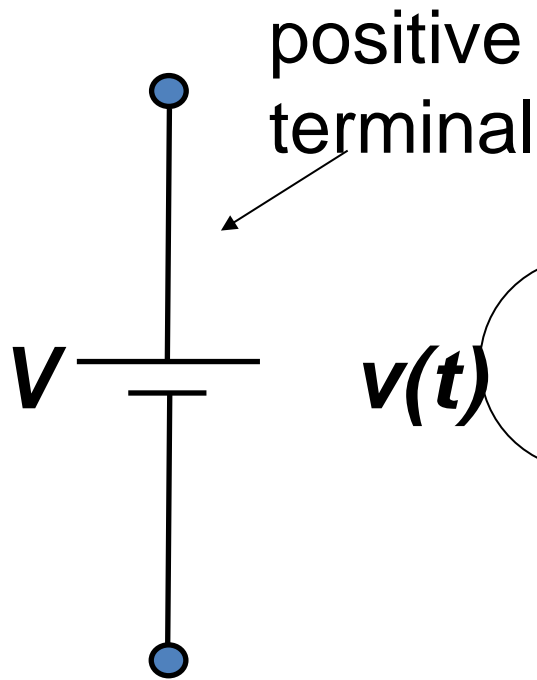

Battery

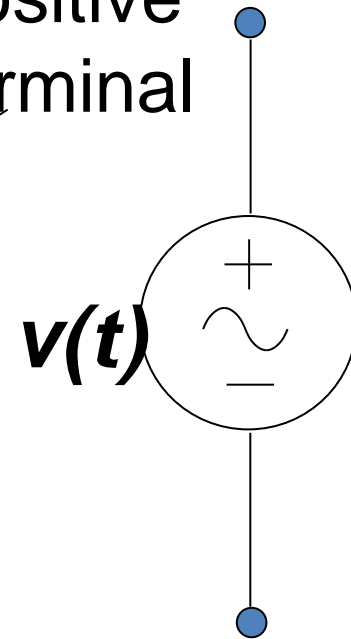


AC
voltage
source

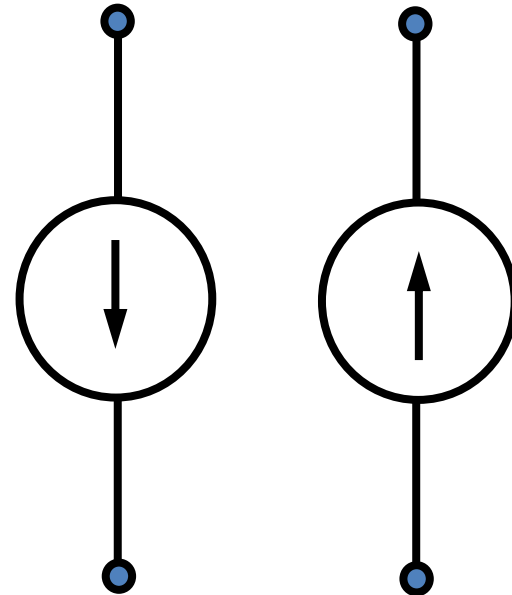
1. CIRCUIT ELEMENTS

Independent current source

- ✓ It provides a specified current which is independent of voltage across the source element or any other circuit variables.




1. CIRCUIT ELEMENTS

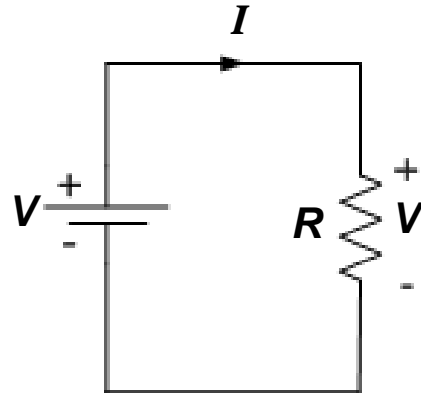


- Circuit Elements: Battery, resistor, conducting wire.
- Circuit variables: Voltage V , current I , resistor R .

	What is known	What is needed
Case 1	Battery voltage, V & resistor value, R	Current, I
Case 2	Battery voltage, V & current, I	Resistor, R
Case 3	Current, I & resistor, R	Battery voltage, V

2. OHM'S LAW

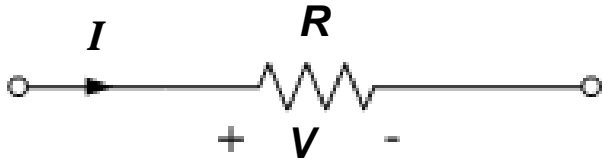

$$V \propto I$$

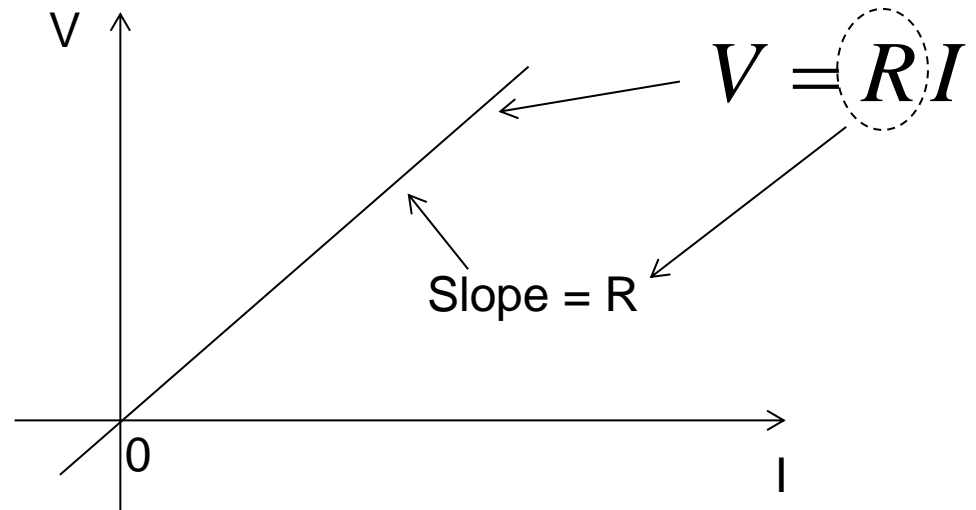

So the voltage across a resistor, V , is directly proportional to the current, I , flowing through the resistor.

$$V = IR$$

$$\text{or } I = \frac{V}{R} \quad \text{or } R = \frac{V}{I}$$

2. OHM'S LAW

- ✓ Ohm's law can also be written as

$$i = G \cdot v$$

- here, G denotes the **conductance** in siemens (S) or mhos

$$G \triangleq \frac{1}{R}$$

- ✓ Power delivered to a resistor



$$p = vi = v \cdot \left(\frac{v}{R}\right) \quad \longrightarrow \quad p = \frac{v^2}{R}$$

$$p = vi = (iR) \cdot i \quad \longrightarrow \quad p = i^2 R$$

- ✓ What about energy absorbed by a resistor? – a passive element.
- ✓ Example: energy delivery by car battery with lights on for 4 hours?

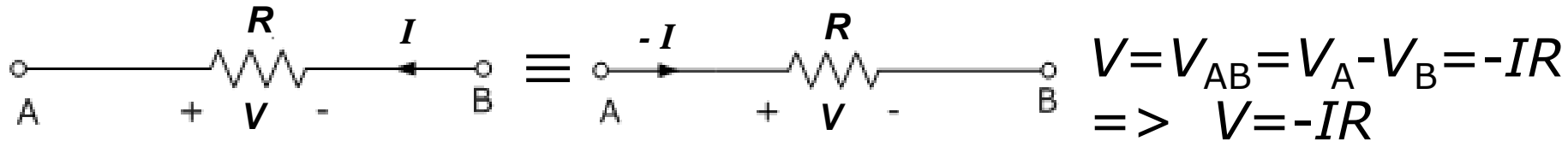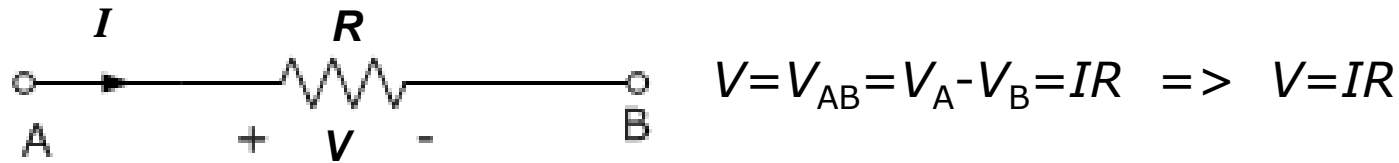
2. OHM'S LAW – POLARITY CONVENTION

Current flows in the direction from high potential (voltage) to low potential (voltage).




Actual (physical) current flow same in both cases

Example

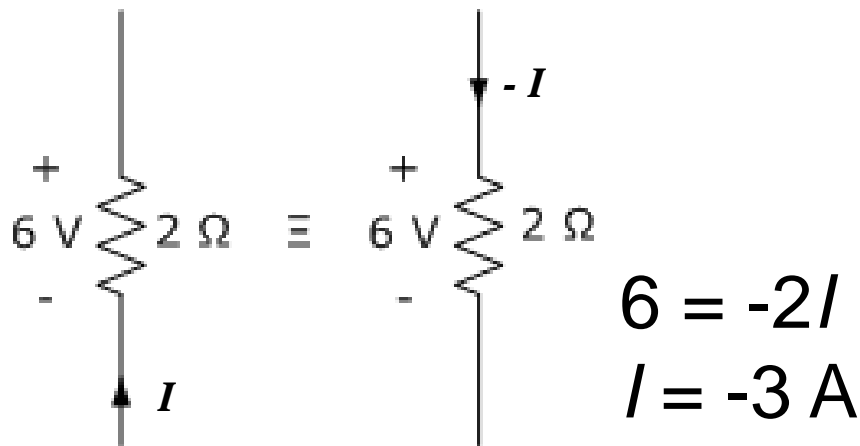

2. OHM'S LAW – SHORT & OPEN CIRCUIT


SHORT CIRCUIT

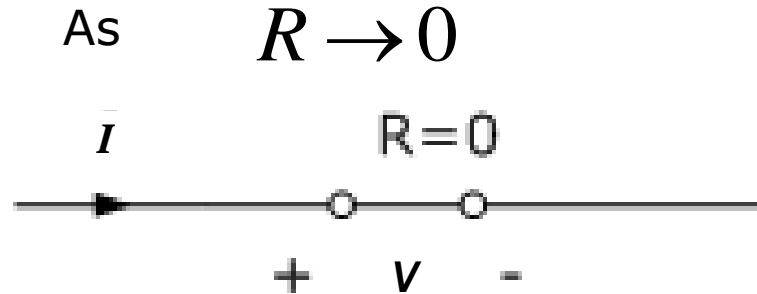

$$V = IR = 0$$

OPEN CIRCUIT


As $R \rightarrow \infty$

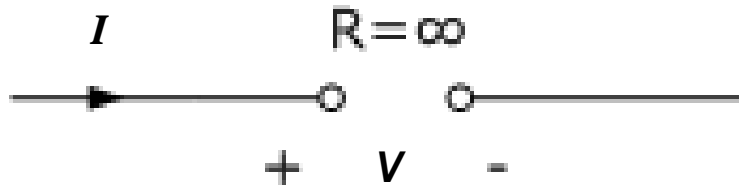

$$I = \frac{V}{R} = \lim_{R \rightarrow \infty} \frac{V}{R} = 0$$

3. SERIES AND PARALLEL RESISTORS

Series: *Must have the same current*

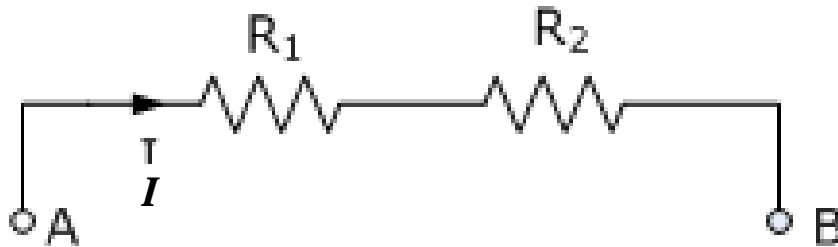


$$R_T = R_1 + R_2$$



R_T is the equivalent resistance looking into the terminals A & B

Parallel *Must have the same voltage*

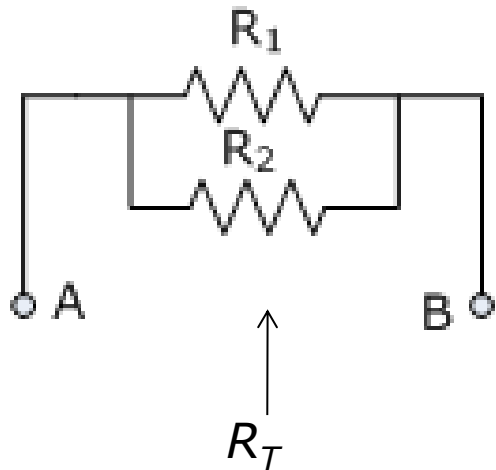

$$R_T = R_1 \parallel R_2$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\Rightarrow R_T = \frac{R_1 R_2}{R_1 + R_2}$$

3. SERIES AND PARALLEL RESISTORS

PROOF FOR SERIES RESISTORS


$$IR_1 + IR_2 = V_{AB}$$

$$\therefore I = \frac{V_{AB}}{R_1 + R_2}$$

$$\therefore \frac{V_{AB}}{I} = R_1 + R_2 = R_T$$

So

$$R_T = R_1 + R_2$$

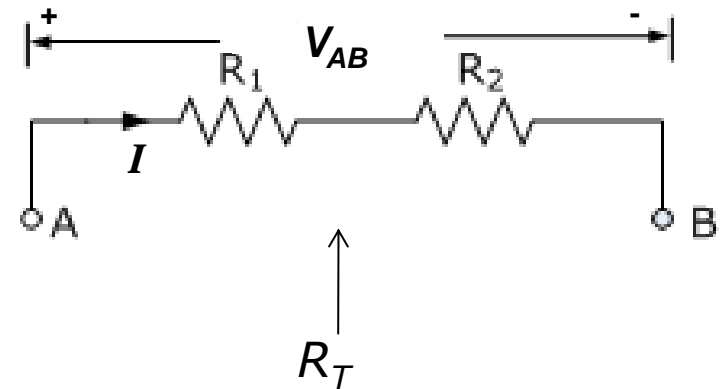

$$\begin{aligned} V_{AB} &= V_A - V_B \\ V_{BA} &= V_B - V_A \\ V_{AB} &= -V_{BA} \end{aligned}$$

3. SERIES AND PARALLEL RESISTORS

PROOF FOR PARALLEL RESISTORS

We have

$$I = I_1 + I_2$$

$$V_{AB} = I_1 R_1 \Rightarrow I_1 = \frac{V_{AB}}{R_1}$$

$$V_{AB} = I_2 R_2 \Rightarrow I_2 = \frac{V_{AB}}{R_2}$$

But

$$I = I_1 + I_2 = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2}$$


So

$$\therefore \frac{I}{V_{AB}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_T}$$

That is

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

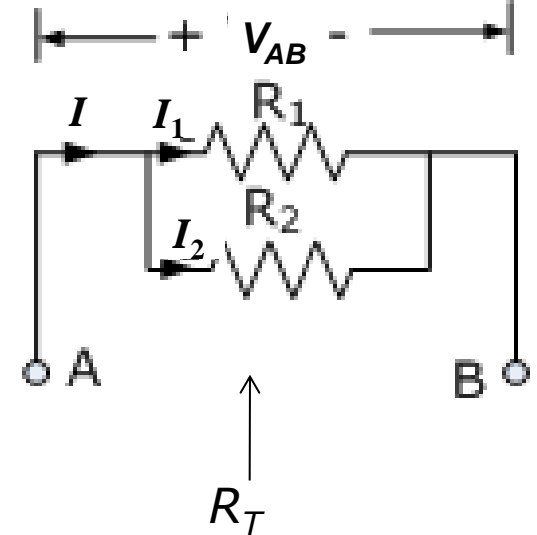
$$\Rightarrow R_T = \frac{R_1 R_2}{R_1 + R_2}$$




V_{AB} = Potential difference between A & B.

3. SERIES AND PARALLEL RESISTORS

EXAMPLE

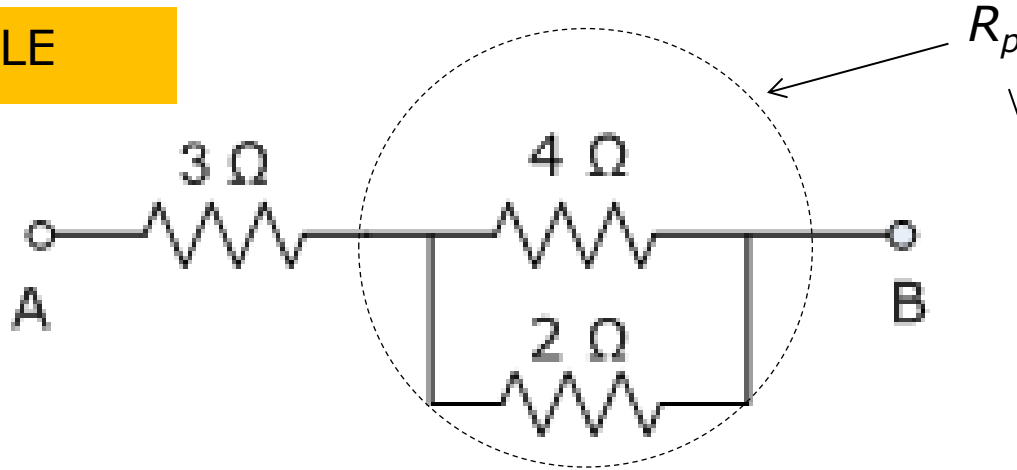

III

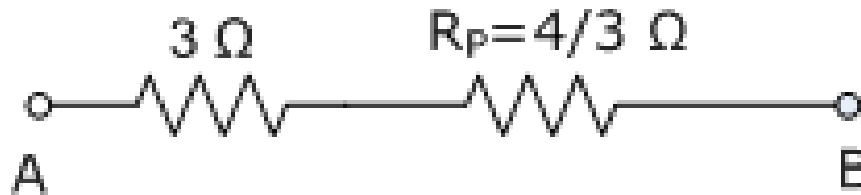

III



$$R_p = 4\ \Omega \parallel 2\ \Omega$$

$$\frac{1}{R_p} = \frac{1}{4} + \frac{1}{2}$$


$$R_p = \frac{4 \times 2}{4 + 2} \approx 1.33\ \Omega$$

$$R_T = R_{AB} = 3 + \frac{4}{3} \approx 4.33\ \Omega$$

3. SERIES AND PARALLEL RESISTORS

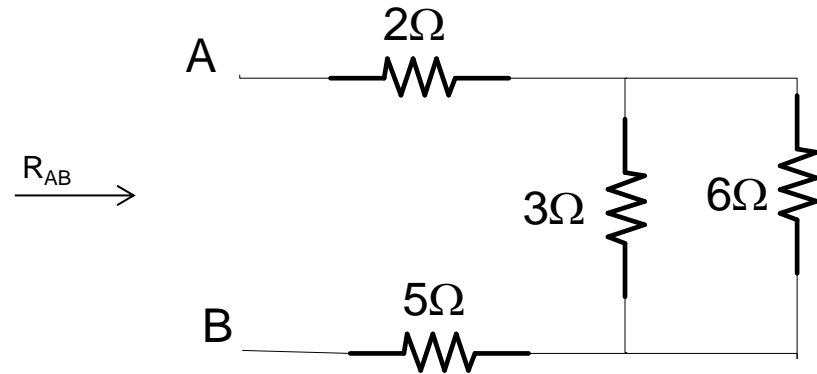EXAMPLE


Find the equivalent resistor between A and B?



3. SERIES AND PARALLEL RESISTORS

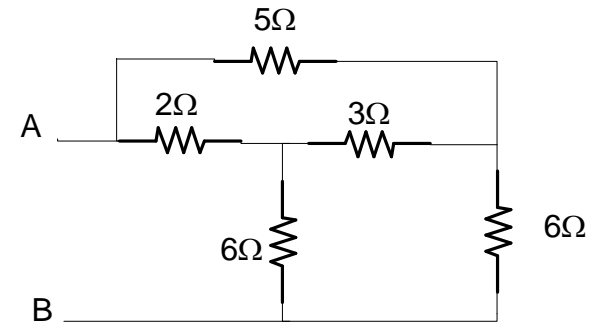EXAMPLE

Find the equivalent resistor between A and B?




Note: Resistors can be connected neither in series nor in parallel

4. VOLTAGE DIVISION

The same current, I , flows through both resistors.

The voltage drop across each resistor is the same (because both resistors have the same resistance).

$$\Rightarrow V_{AB} = V_{BC} = IR$$

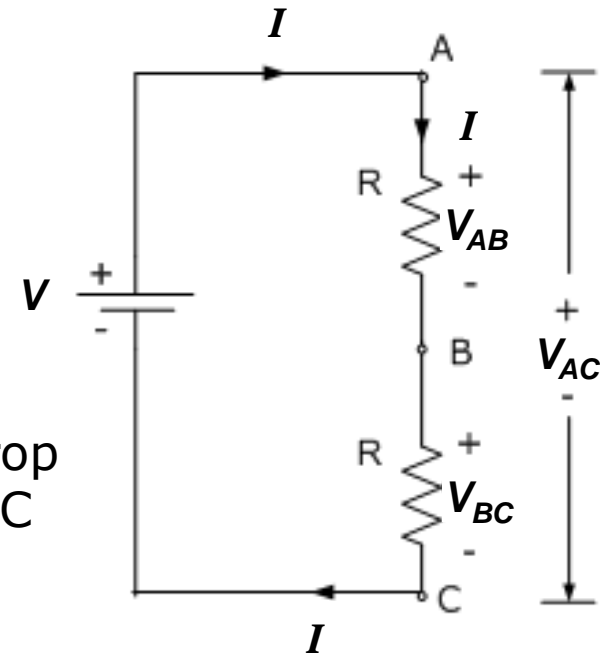

Voltage drop from A to C = Voltage drop from A to B + Voltage drop from B to C

$$V_{AC} = V_{AB} + V_{BC}$$

$$V_{AC} = IR + IR = I(2R)$$

But

$$V_{AC} = V$$

$$\therefore I = \frac{V}{2R}$$

$$\therefore V_{AB} = IR = \frac{V}{2R} \times R = 0.5V$$

Similarly $V_{BC} = 0.5V$

4. VOLTAGE DIVISION

What if $R_1 \neq R_2$?

Again, $V = V_1 + V_2$


$$= IR_1 + IR_2 = I(R_1 + R_2)$$

So, $I = \frac{V}{R_1 + R_2}$

and $V_1 = IR_1 = \frac{V}{R_1 + R_2} R_1 = \left(\frac{R_1}{R_1 + R_2} \right) V$

similarly $V_2 = \left(\frac{R_2}{R_1 + R_2} \right) V$
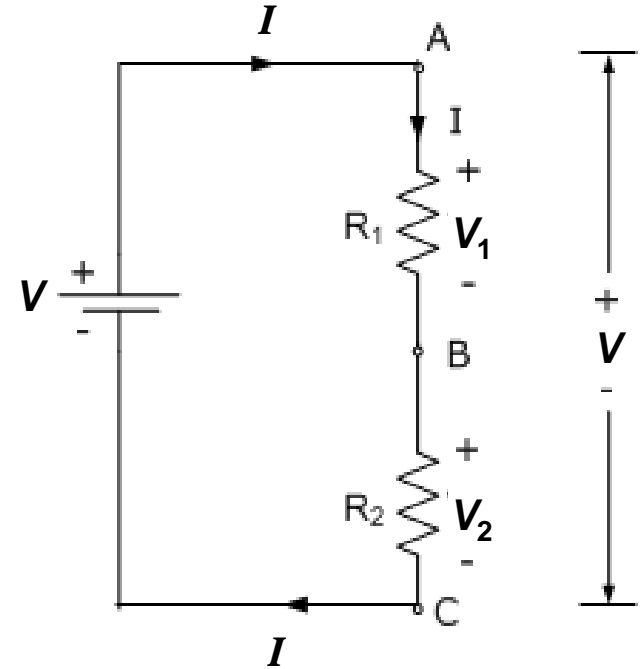
$$\text{E.g. } R_1 = 1\Omega, R_2 = 4\Omega \quad \Rightarrow V_1 = 1/5 = 0.2V, \quad V_2 = 4/5 = 0.8V$$




(Equivalent resistance in circuit is $R_1 + R_2$ i.e. in series)

4. VOLTAGE DIVISION

POLARITY CONVENTION REMINDER

Polarity on voltage
label V_2 reversed

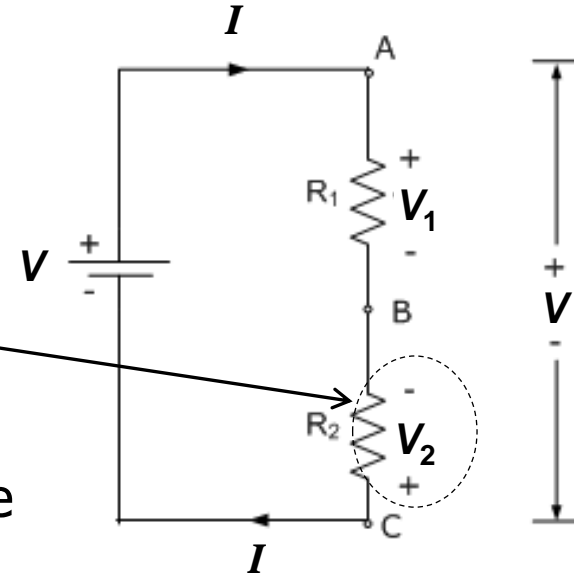

V = Voltage difference across R_1 from A to B + Voltage difference across R_2 from B to C

= V_1 + $(-V_2)$ ← An increase of V_2 = a drop of $(-V_2)$
 a drop of V_1

$$V_1 = IR_1 \quad \text{and} \quad V_2 = -IR_2$$

So $V = IR_1 - (-IR_2) = I(R_1 + R_2)$


$$V_1 = \left(\frac{R_1}{R_1 + R_2} \right) V$$

$$V_2 = - \left(\frac{R_2}{R_1 + R_2} \right) V$$

4. VOLTAGE DIVISION

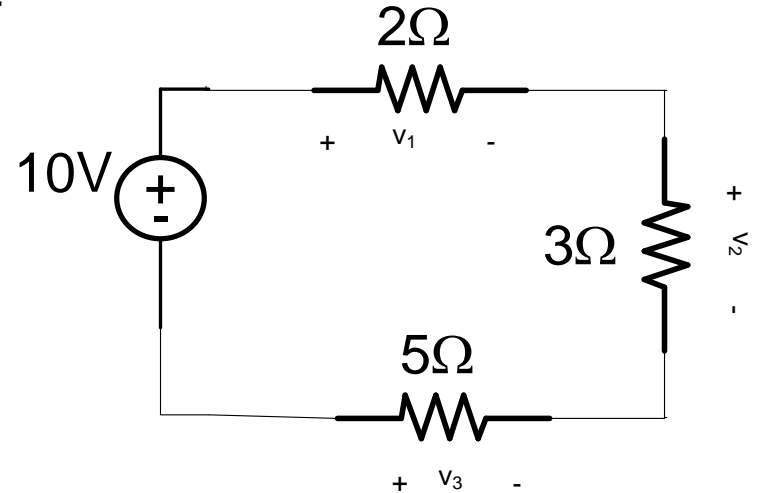Example

Find the value of the voltage V_1 , V_2 and V_3




5. CURRENT DIVISION

The same voltage, V , exists across both resistors.

Current through each resistor is the same (because both resistors have the same resistance)

$$\Rightarrow I_1 = I_2 = V/R$$

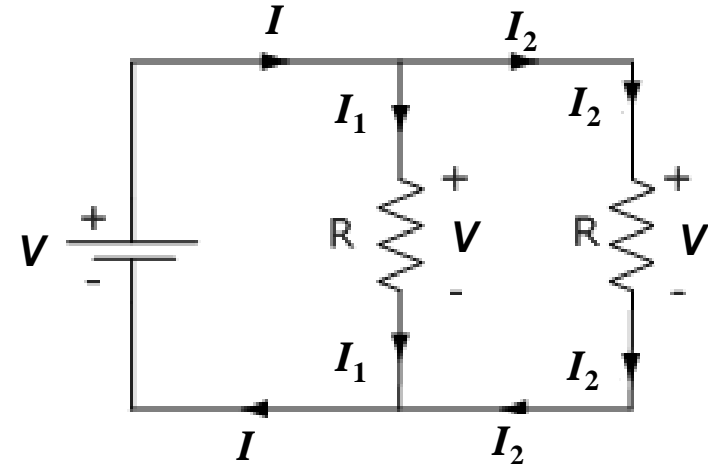

Total current, I = Current through first resistor, I_1 + Current through second resistor, I_2



i.e.
$$I = I_1 + I_2$$
$$= \frac{V}{R} + \frac{V}{R} = V\left(\frac{1}{R} + \frac{1}{R}\right)$$

(Equivalent resistance in circuit is $R/2$, i.e. in parallel)

So
$$I = \frac{V}{R/2} \text{ or } \frac{V}{R} = \frac{I}{2} \quad \text{and} \quad I_1 = I_2 = \frac{V}{R} = \frac{I}{2}$$

5. CURRENT DIVISION

What if $R_1 \neq R_2$?

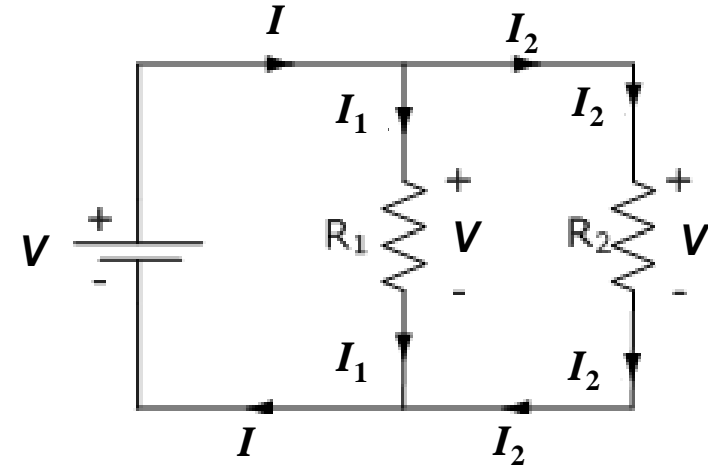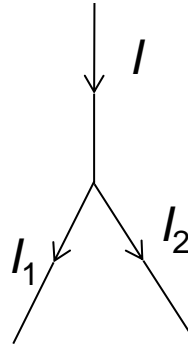

Again,

$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$= \frac{V}{\left(\frac{R_1 R_2}{R_1 + R_2} \right)}$$

R_T →

(Equivalent resistance in circuit is $\frac{R_1 R_2}{R_1 + R_2} \Omega$, i.e. in parallel)

5. CURRENT DIVISION


$$V = I \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\text{So } I_1 = \frac{V}{R_1} = \left(\frac{R_2}{R_1 + R_2} \right) I$$

$$I_2 = \frac{V}{R_2} = \left(\frac{R_1}{R_1 + R_2} \right) I$$

E.g. $R_1 = 1 \Omega$, $R_2 = 4 \Omega$

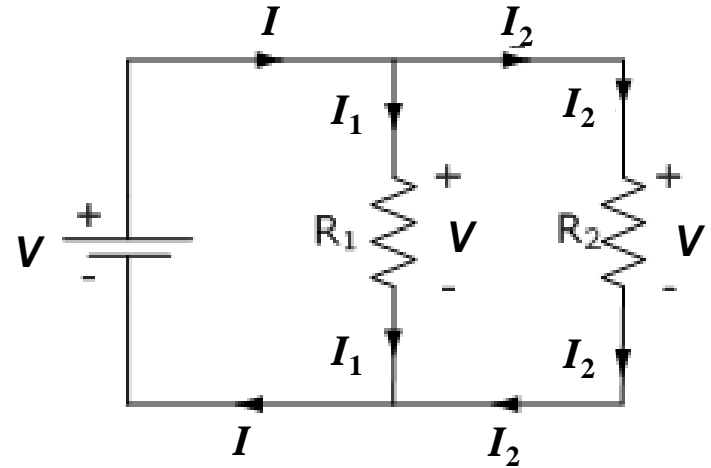
$$I_1 = V, \quad I_2 = \frac{V}{4}, \quad I = 1.25 \times V$$



Equivalent resistance in circuit = $1\ \Omega // 4\ \Omega = 0.8\ \Omega$

5. CURRENT DIVISION

POLARITY CONVENTION AGAIN

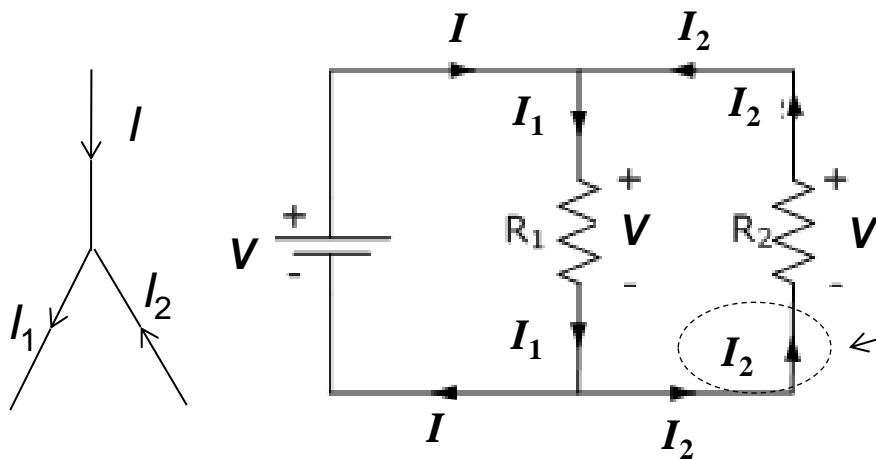

Direction of current **label** is reversed

Total current, I = Current "down" through R_1 + Current "down" through R_2 = $I_1 + (-I_2)$

$$V = I_1 R_1 = (-I_2 R_2) \Rightarrow I_1 = \frac{V}{R_1}, I_2 = -\frac{V}{R_2}$$


$$\text{So, } I = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I, \quad I_2 = -\left(\frac{R_1}{R_1 + R_2} \right) I$$

5. CURRENT DIVISION

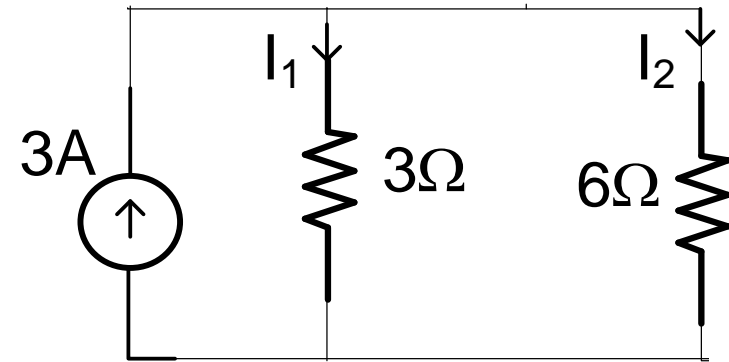Example


Find the value of the current I_1 and I_2



5. CURRENT DIVISION

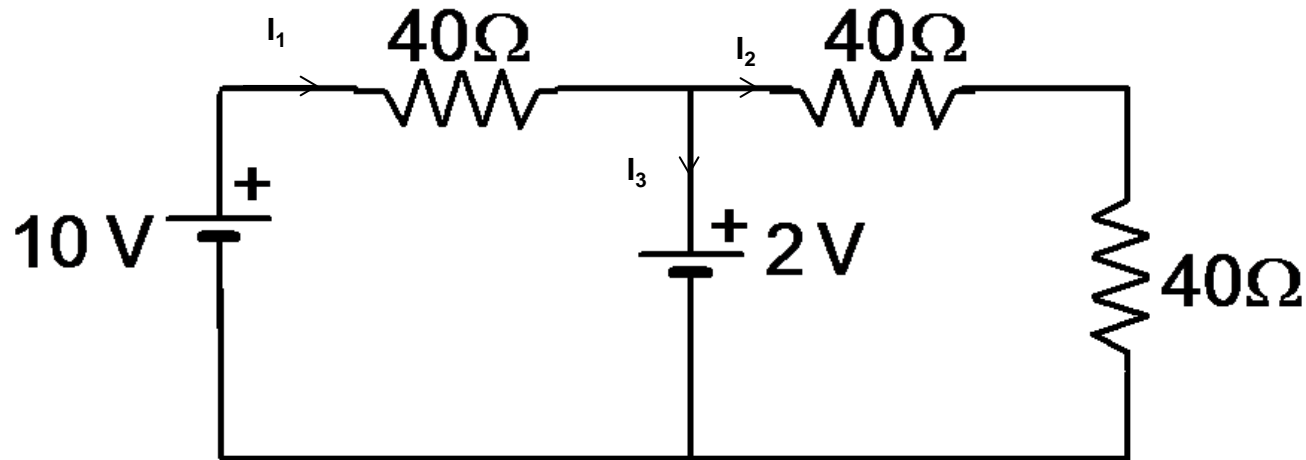Example

Analyze the below circuit to find the value of currents I_1 , I_2 , I_3



Need to apply more advanced circuit analysis methods