

WEEK 2-2018

Combinational circuit I



Binary logic and Gates

- Transistors interconnected each other to form **logic gates**
- Each gate has inputs and an output. It performs a **specific logical operation** on its binary inputs and provides a binary value at the output.
- Inputs and output of a logic gate are designated by alphabetical variables .
- These variables can assume only 1 or 0 values and are known as **Binary variables**.



Basic logical operations

- There are three basic logical operations : **AND**, **OR**, and **NOT**.

AND

- represented by a dot or an absence of operation
 $Z = X \cdot Y = XY = X \wedge Y$
- Z is 1 if and only if $X=1$ and $Y=1$; otherwise $Z = 0$

YES = 1

NO = 0

$X \cdot Y$
$0 \cdot 0 = 0$
$0 \cdot 1 = 0$
$1 \cdot 0 = 0$
$1 \cdot 1 = 1$

X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

Truth Table
for AND gate

4 = 2

AND logical operation can be extended to more than two input binary variables.

Basic logical operations

OR

- represented by a plus symbol or “ \vee ”

$$Z = X + Y = X \vee Y$$

- Z is 1 if X=1 or Y=1; Z is 0 if X = 0 and Y= 0

$X + Y$
$0+0 = 0$
$0+1 = 1$
$1+0 = 1$
$1+1 = 1$

X	Y	$X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

Truth Table
for OR gate

OR logical operation can be extended to more than two input binary variables.

Basic logical operations

NOT

- represented by a bar over the variable
 $Z = \bar{X}$
- Z is 1 if X=0 and Z is 0 if X = 1

X
$\bar{0} = 1$
$\bar{1} = 0$



X	Z = \bar{X}
0	1
1	0

Truth Table
for NOT gate

COMPLEMENT

Logic gates


- **Logical Gates** - Electrical circuits that implement logical operations.
- The input terminals accept voltage signals within allowable range (as a binary signals) and gives out at the output terminal a binary signals that also falls with in the allowable range.
- Intermediate values are crossed only during transitions from 0 to 1 or otherwise.
- Graphical (symbolical) representations of the three types of gates: **AND, OR, NOT**

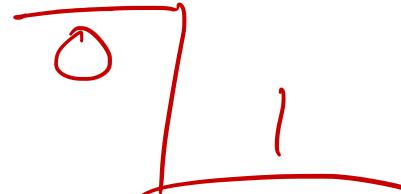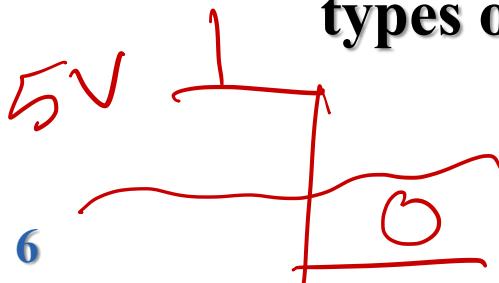


Logic gates



AND gate

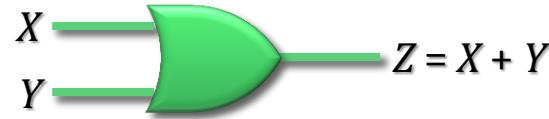


OR gate

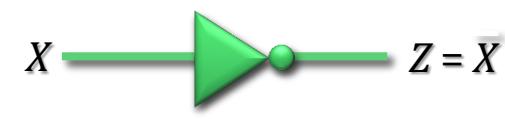


NOT gate (inverter)


- Time diagram (waveform behavior)

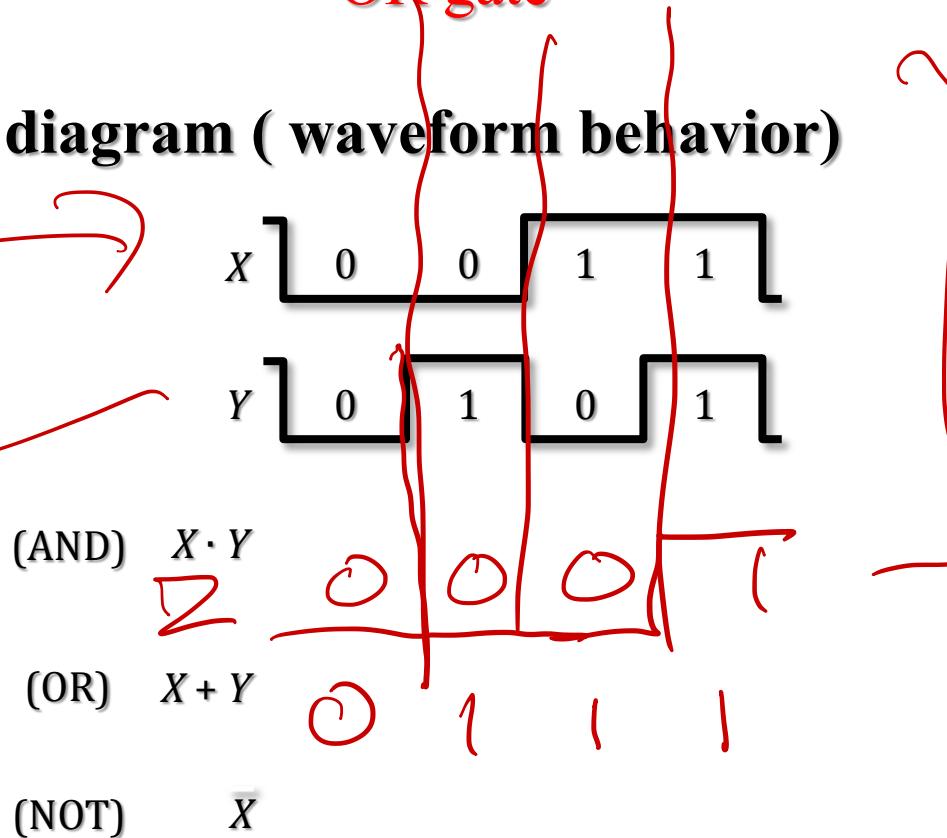

Gate delay

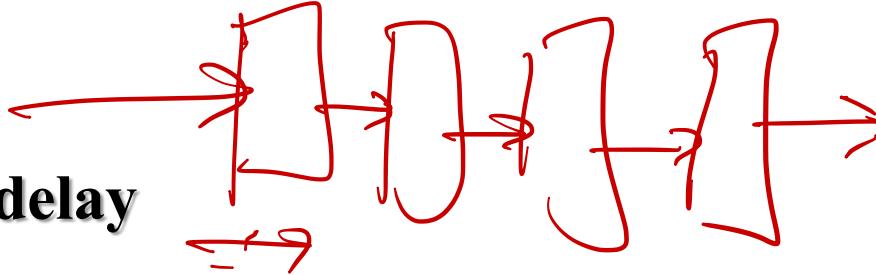

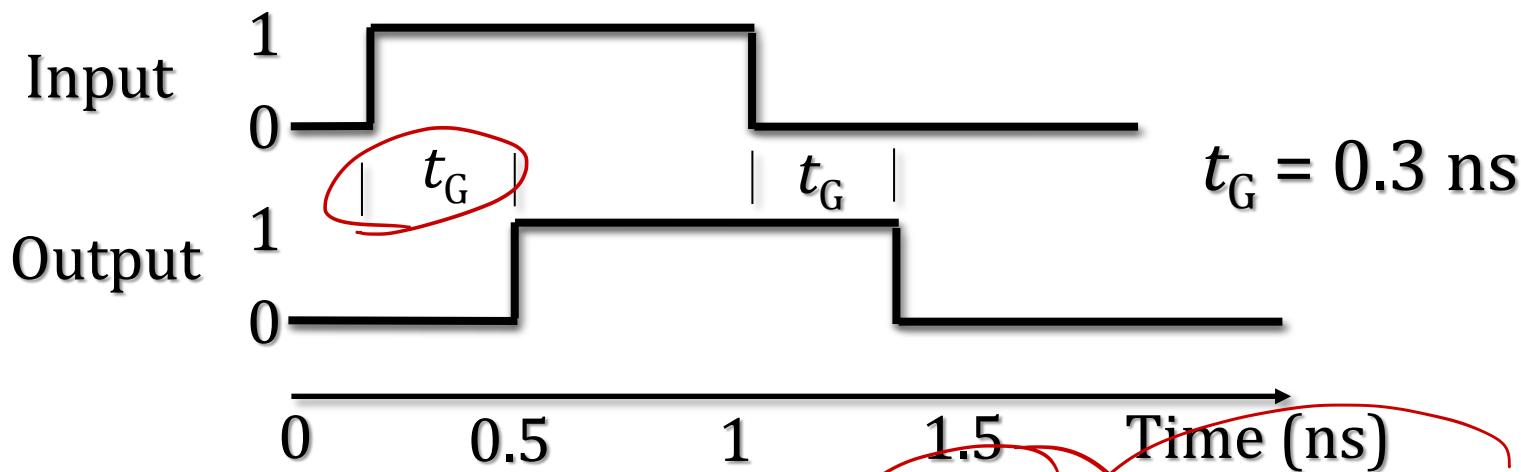- In reality, there is a gate delay
- Gate delay – the length of time it takes for an input changes to result in the corresponding output change.



- Gate delay is a function of **gate type**, **number of inputs**, **underlying technology**, and **circuit design of the gate**.

Boolean Algebra

- A *Boolean Algebra* is an algebra dealing with binary variables and logic operations.
- A *Boolean expression* is an algebraic expression formed by using binary variables, the constants 0 and 1, the logic operation symbols, and parentheses
- The order of evaluation in a Boolean expression:


(), NOT, AND, OR

$$Z = \overbrace{AB} + \overbrace{CD}$$

$$Z = AB + \overline{C}(D+E)$$

Boolean function

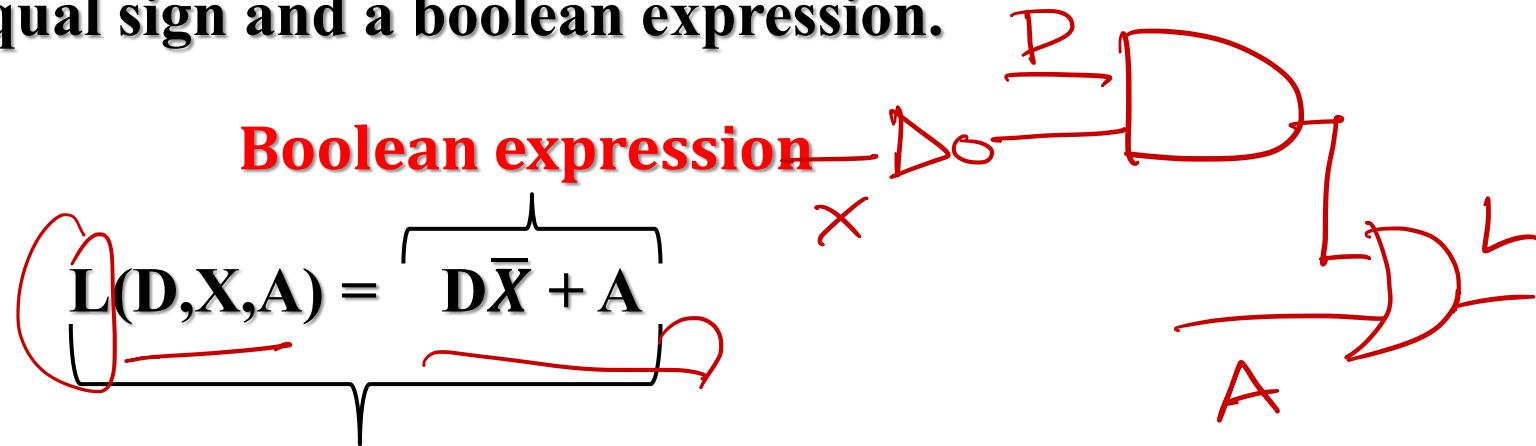- A *Boolean function* is a boolean equation consisting of a binary variable identifying the function followed by an equal sign and a boolean expression.




Boolean function or Boolean equation

- A boolean function can be transformed into a circuit diagram (logic diagram) composed of logic gates and interconnected by wires.

Boolean function

Logic Diagram

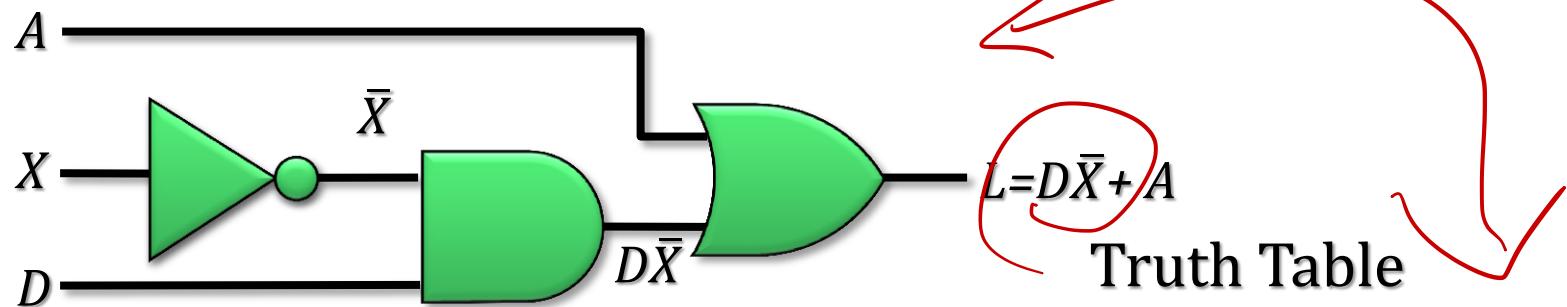

- A boolean function can be represented by a truth table

$$2^5 - 1$$

$$2^n \quad 2^3 - 1$$

D	X	A	L = D\bar{X} + A
0	0	0	0
0	0	1	
0	1	0	
0	1	1	1
1	0	0	
1	0	1	
1	1	0	
1	1	1	1


4

Boolean function

- There is **only one way** that a boolean function can be represented by a truth table
- The Boolean function, however, can be expressed by various boolean equations, which are not the same but equivalent. Eg. L and F have the same function.

$$L(D, X, A) = \underbrace{D\bar{X} + A}_{3 \times 3 = 9}$$
$$F(D, X, A) = D\bar{X} + AD + A\bar{D} \quad \underbrace{\qquad\qquad\qquad}_{6 \times 3 = 18}$$

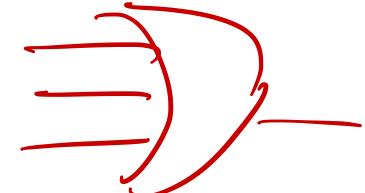- The boolean equation dictates the interconnection of gates in the logic circuit diagram.



- Simpler expression reduces the number of gates and the number of inputs into the gates

Basic identities of boolean algebra

$$1. X + 0 = X$$

$$2. X \cdot 1 = X$$

Identity

✓

$$3. X + 1 = 1$$

$$4. X \cdot 0 = 0$$

Null

$$5. X + X = X$$

$$6. X \cdot X = X$$

Idempotence

$$7. X + \bar{X} = 1$$

$$8. X \cdot \bar{X} = 0$$

Complementarity

$$9. \bar{\bar{X}} = X$$

Involution

Basic identities of boolean algebra

$$10. Y+X = X+Y$$

$$11. Y \cdot X = X \cdot Y$$

Commutative

$$12. X + (Y + Z) = (X + Y) + Z$$

$$13. (XY)Z = X(YZ)$$

Associative

$$14. X(Y + Z) = XY + XZ$$

$$15. X + YZ = (X + Y)(X + Z)$$

Distributive

$$16. \overline{X + Y} = \overline{X}\overline{Y}$$

$$17. \overline{XY} = \overline{X} + \overline{Y}$$

De morgan's law

$$\overline{XY} = \overline{X} + \overline{Y}$$

$$\overline{X+Y} = \overline{X} \overline{Y}$$

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{X+Y+Z} = \overline{X} \overline{Y} \overline{Z}$$

$$\overline{XY+Z} = \overline{W+Z}$$

$$W = XY = \overline{X} \overline{Y}$$

$$= (\overline{XY}) \overline{Z}$$

$$\overline{W} = \overline{XY} = \overline{X} + \overline{Y}$$

$$= (\overline{X} + \overline{Y}) \overline{Z}$$

Basic identities of boolean algebra

- Any expression can replace the variable X in all boolean identity.

Eg. $X + 1 = 1$

with $X = AB + C$

$$AB + C + 1 = 1$$

- Identity 10 -14 are similar to ordinary algebra.
However, Identity 15 does not hold in ordinary algebra.
- Identity 16 and 17 are De' morgan's rule and they are very important rules

X	Y	$\bar{X} + \bar{Y}$	\bar{XY}	$\overline{X + Y}$	$\bar{X}\bar{Y}$
1	0	1	1	1	
1	0	1	1	0	
0	1	1	1	0	
1	1	0	0	0	

Basic identities of boolean algebra

- De'morgan's law can be extended to three or more variables. The general De'morgan's theorem can be expressed as

$$\overline{X_1 + X_2 + \dots + X_n} = \overline{X_1} \overline{X_2} \dots \overline{X_n}$$

$$\overline{X_1 X_2 \dots X_n} = \overline{X_1} + \overline{X_2} + \dots + \overline{X_n}$$

Duality

- The *dual* of an algebraic expression is obtained by interchanging + and · and interchanging 0's and 1's
- Any Boolean theorem that can be proven is thus also proven for its dual!
- Note that previous identities appear in dual pairs
- Example:

$$\begin{array}{l} XY + \overline{X}Z + YZ = XY + \overline{X}Z \\ \hline \text{Dual } (X+Y)(\overline{X} + Z)(Y+Z) = (X+Y)(\overline{X} + Z) \end{array}$$

↑ ↑ ↗ ↑ ↑ ↗ ↓

Red annotations: A red circle highlights the first term XY . A red bracket underlines the terms $\overline{X}Z$ and YZ . A red circle highlights the second term XY . A red bracket underlines the terms $\overline{X}Z$ and YZ . Red arrows point from the terms X , Y , and Z in the original equation to the corresponding terms $(X+Y)$, $(\overline{X} + Z)$, and $(Y+Z)$ in the dual equation. Red arrows also point from the terms \overline{X} and Z in the original equation to the corresponding terms $(\overline{X} + Z)$ and $(Y+Z)$ in the dual equation.

Useful theorems of Boolean algebra

$$X + XY = X$$

$$X(X + Y) = X$$

Absorption

$$XY + X\bar{Y} = X$$

$$(X + Y)(\bar{X} + Y) = X$$

Minimization

$$X(Y + \bar{Y}) = X$$

$$X(\bar{X} + Y) = XY$$

Simplification

$$XY + X\bar{Z} + YZ = XY + YZ$$

$$(X + Y)(\bar{X} + Z)(Y + Z) = (X + Y)(\bar{X} + Z)$$

Consensus



Proof of consensus theorem

- Example: Prove the Consensus Theorem

$$\begin{aligned} XY + \bar{X}Z + YZ &= XY + \bar{X}Z + YZ \cdot 1 && (2) \\ &= XY + \bar{X}Z + YZ(X + \bar{X}) && (7) \\ &= XY + \bar{X}Z + \underline{XYZ + \bar{X}YZ} && (14) \\ &= XY + XYZ + \underline{\bar{X}Z + \bar{X}YZ} && (10) \\ &= XY(1 + Z) + \bar{X}Z(1 + Y) && (14) \\ &= XY + \bar{X}Z && (3) \end{aligned}$$

$\text{W} = \cancel{XYZ}$

$$\begin{aligned} W + WZ &= \frac{XY + (XY)Z}{XY} + \frac{\bar{X}Z + \bar{X}YZ}{\bar{X}Z} \\ &= W \end{aligned}$$

Expression simplification

$$x + \bar{x} = \cancel{x}$$

- A **literal** is a complemented or uncomplemented variable in a term
- Simplify the following expression to contain the smallest number of literals:

$$\begin{aligned} & AB + ACD + \cancel{\bar{A}BD} + \cancel{\bar{ACD}} + \cancel{\bar{ABCD}} \\ &= AB + \cancel{\bar{ABCD}} + ACD + AC\bar{D} + \cancel{\bar{ABD}} \\ &= AB + \cancel{\bar{ABCD}} + AC(D + \bar{D}) + \cancel{\bar{ABD}} \\ &\cancel{= \bar{ABD}} \quad (1+C) = AB + AC + \cancel{\bar{ABD}} = B(A + \cancel{\bar{AD}}) + AC \\ &= B(A + D) + AC \end{aligned}$$

$\cancel{A + \bar{AB}}$
 $\cancel{C + D}$

- Only 5 literals!

$$\boxed{\cancel{\bar{ABD}}} + \cancel{\bar{ABD}} = \cancel{\bar{ABD}}$$

$$\cancel{ACD + \bar{ACD}} = \cancel{AC(D + \bar{D})} = AC$$

Complement of a function

$$\overline{X+Y} = \overline{X}\overline{Y}$$

$$\overline{XY} = \overline{X} + \overline{Y}$$

- The complement of a function F , \overline{F} , can be obtained in two ways:

- By applying DeMorgan's theorem
- By taking the dual of the function and complementing each literal

Example: $F = \overline{XYZ} + \overline{XY}\overline{Z}$

$$\begin{aligned} & \overline{(X+Y+Z)} \\ & (X+Y+\overline{Z}) \end{aligned}$$

$$\overline{\overline{XYZ} + \overline{XY}\overline{Z}} = (\overline{X}\overline{Y}\overline{Z})(\overline{X}\overline{Y}\overline{Z})$$

$$\overline{\overline{XYZ}} = \overline{\overline{X} + \overline{Y} + \overline{Z}} = X + Y + Z$$

$$\overline{\overline{XY}\overline{Z}} = X + Y + \overline{Z}$$

$$F = (X + Y + Z)(X + Y + \overline{Z})$$

$$F = \overline{x(\bar{y}\bar{z} + yz)} \quad \swarrow$$

$$\bar{F} = \overline{x(\bar{y}\bar{z} + yz)}$$

$$W = \bar{y}\bar{z} \quad U = yz$$

$$\bar{F} = \overline{x(W+U)}$$

$$= \bar{x} + \overline{(W+U)}$$

$$= \bar{x} + \bar{W}\bar{U}$$

$$\bar{W} = \overline{\bar{y}\bar{z}} = \bar{\bar{y}} + \bar{\bar{z}} = y+z$$

$$\bar{U} = \overline{yz} = \bar{y} + \bar{z}$$

$$F = \bar{x} + (y+z)(\bar{y}+\bar{z})$$

$$\bar{F} = \bar{x} + (y+z)(\bar{y}+\bar{z})$$

↑


$$\left| \begin{array}{l} \bar{xy} = \bar{x} + \bar{y} \\ \bar{x+y} = \bar{x}\bar{y} \end{array} \right.$$

Demorgan's

Standard Forms

- *Standard forms* are standard ways to express Boolean functions *SOP*
- Contain product terms (**Minterms**) and sum terms (**Maxterms**) *POS*
- Result in more desirable expression for circuit implementation

Minterms:

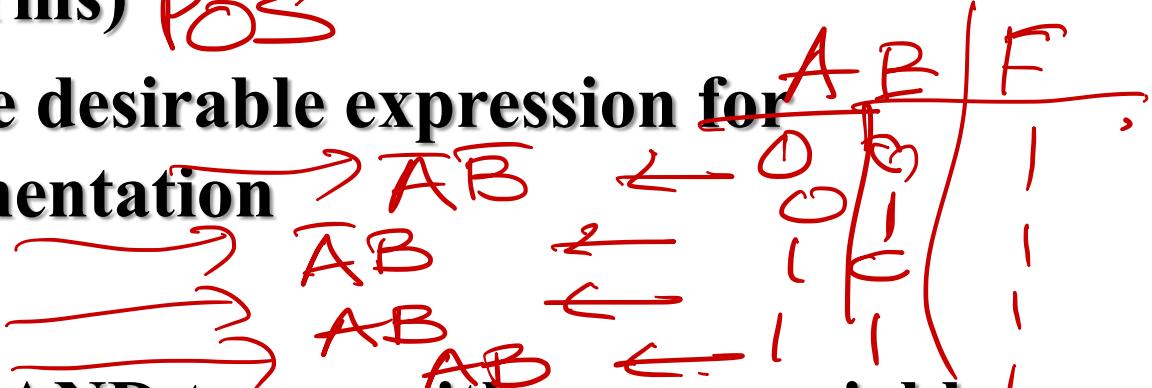

- Minterms are AND terms with every variable present in either true or complement form
- Every variable combination in a truth table has a corresponding minterm

$$F = \bar{A}\bar{B} + \bar{A}B + A\bar{B} + AB$$

$$F = AB + \bar{B}D + \bar{C}\bar{D}$$

$$Q = (\bar{A} + B)(\bar{C} + D + E)$$

$$H = A + (BC + DE)$$

$$W = \sum(m_0, m_3, m_7) \text{ SOP} = \underline{\underline{B}}(m_0 - m_1)$$

- For a function with n variables, there will be 2^n minterms
- The literals are listed in the same order for all minterms (usually alphabetically)

W ↗

X	Y	Z	Product Term	symbols	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7
0	0	0	$\bar{X}\bar{Y}\bar{Z}$	m_0	1	0	0	0	0	0	0	0
0	0	1	$\bar{X}\bar{Y}Z$	m_1	0	1	0	0	0	0	0	0
0	1	0	$\bar{X}YZ$	m_2	0	0	1	0	0	0	0	0
0	1	1	$\bar{X}YZ$	m_3	0	0	0	1	0	0	0	0
1	0	0	$X\bar{Y}\bar{Z}$	m_4	0	0	0	0	1	0	0	0
1	0	1	$X\bar{Y}Z$	m_5	0	0	0	0	0	1	0	0
1	1	0	$XY\bar{Z}$	m_6	0	0	0	0	0	0	1	0
1	1	1	XYZ	m_7	0	0	0	0	0	0	0	1

↙ K ↗ O ↗ O ↗ O ↗ O ↗ O ↗ K ↗

↑

Minterms

$$F = \sum(m_1, m_4) = \sum m(1, 4)$$

$$= \bar{X}\bar{Y}Z + \bar{X}YZ$$

X	Y	Z	Product Term	symbols	m_0	m_1	m_2	m_3	m_4	m_5	m_6	m_7	F
0	0	0	$\bar{X}\bar{Y}\bar{Z}$	m_0	1	0	0	0	0	0	0	0	0
0	0	1	$\bar{X}\bar{Y}Z$	m_1	0	1	0	0	0	0	0	0	1
0	1	0	$\bar{X}Y\bar{Z}$	m_2	0	0	1	0	0	0	0	0	0
0	1	1	$\bar{X}YZ$	m_3	0	0	0	1	0	0	0	0	1
1	0	0	$X\bar{Y}\bar{Z}$	m_4	0	0	0	0	1	0	0	0	0
1	0	1	$X\bar{Y}Z$	m_5	0	0	0	0	0	1	0	0	0
1	1	0	$XY\bar{Z}$	m_6	0	0	0	0	0	0	1	0	0
1	1	1	XYZ	m_7	0	0	0	0	0	0	0	1	0

- A variable in a minterm is *complemented* for 0 and is *not complemented* for 1
- The symbol index corresponds to the binary combination of the variables

Sum-of-Minterms Canonical Form

- Express a function as a sum of minterms
- Logical sum (*OR*) of all minterms where the function value is 1

$$\bar{F} = \sum(m_1, m_3, m_4, m_6)$$

- Example:

$$\begin{aligned} F &= \sum(m_0, m_2, m_5, m_7) \\ &= \bar{x}\bar{y}\bar{z} + \bar{x}yz \\ &\quad + x\bar{y}z \\ &\quad + xy\bar{z} \end{aligned}$$

x	y	z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Maxterms

$$F = \overline{F(1,5)} \\ = (x+y+z)(\bar{x}+\bar{y}+\bar{z}) \text{ POS}$$

- Similarly, maxterms are OR terms with every variable present
- In maxterms, a variable *is complemented for a 1 and not complemented for a 0*

X	Y	Z	Sum Term	symbols	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇	F	
0	0	0	$X + Y + Z$	M ₀	0	1	1	1	1	1	1	1	1	1
0	0	1	$X + Y + \bar{Z}$	M ₁	1	0	1	1	1	1	1	1	1	0
0	1	0	$X + \bar{Y} + Z$	M ₂	1	1	0	1	1	1	1	1	1	1
0	1	1	$X + \bar{Y} + \bar{Z}$	M ₃	1	1	1	0	1	1	1	1	1	1
1	0	0	$\bar{X} + Y + Z$	M ₄	1	1	1	1	0	1	1	1	1	1
1	0	1	$\bar{X} + Y + \bar{Z}$	M ₅	1	1	1	1	1	0	1	1	1	0
1	1	0	$\bar{X} + \bar{Y} + Z$	M ₆	1	1	1	1	1	1	0	1	1	1
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	M ₇	1	1	1	1	1	1	1	0	1	1

$$\cancel{F(X,Y,Z)} = X + Y + Z$$

Maxterms

- The symbol index corresponds to the binary combination of the variables
- For a function with n variables, there will be 2^n maxterms

X	Y	Z	Sum Term	symbols	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X + Y + Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X + Y + \bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X + \bar{Y} + Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X + \bar{Y} + \bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X} + Y + Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X} + Y + \bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X} + \bar{Y} + Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Maxterms

- The literals are listed in the same order for all minterms (usually alphabetically)
- Every variables combination in a truth table has a corresponding minterm

X	Y	Z	Sum Term	symbols	M ₀	M ₁	M ₂	M ₃	M ₄	M ₅	M ₆	M ₇
0	0	0	$X + Y + Z$	M ₀	0	1	1	1	1	1	1	1
0	0	1	$X + Y + \bar{Z}$	M ₁	1	0	1	1	1	1	1	1
0	1	0	$X + \bar{Y} + Z$	M ₂	1	1	0	1	1	1	1	1
0	1	1	$X + \bar{Y} + \bar{Z}$	M ₃	1	1	1	0	1	1	1	1
1	0	0	$\bar{X} + Y + Z$	M ₄	1	1	1	1	0	1	1	1
1	0	1	$\bar{X} + Y + \bar{Z}$	M ₅	1	1	1	1	1	0	1	1
1	1	0	$\bar{X} + \bar{Y} + Z$	M ₆	1	1	1	1	1	1	0	1
1	1	1	$\bar{X} + \bar{Y} + \bar{Z}$	M ₇	1	1	1	1	1	1	1	0

Product-of-Maxterms Canonical

Form

P

POS

- Express a function as a product of maxterms
- Logical product (*AND*) of all maxterms where the function value is 0

- Example:

SOP

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(M₅, M₇)

Minterms and Maxterms Relationship

- Review: DeMorgan's Theorem

$$m_0 = \overline{X}\overline{Y} \quad M_0 = X+Y$$

$$\overline{m}_0 = \overline{(X\overline{Y})} = X+Y = M_0$$

$$\overline{m}_i = M_i$$

X	Y	m	M
0	0	m_0	M_0
0	1	m_1	M_1
1	0	m_2	M_2
1	1	m_3	M_3

$$M_i = \overline{m}_i$$

- Two-variable example:

$$F = \sum m(1, 5, 7)$$

$$\longleftrightarrow F = \prod M(0, 2, 3, 4, 6) \leftarrow$$

$$\bar{F} = \sum m(0, 2, 3, 4, 6) \leftarrow$$

$$\bar{F} = \prod M(1, 5, 7)$$

X	Y	Z	F
0	0	0	0
0	0	1	1 ←
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1 ←
7	1	1	1 ←

Function Complements

- The complement of a function expressed as a sum of minterms is constructed by selecting the minterms missing in the expression
- Alternatively, the complement of a function expressed as a sum of minterms is simply the product of maxterms with the same indices

Function Complement Example

- Find complement expressions for the function:

$$G(X, Y, Z) = \sum m(1, 3, 5, 7)$$

- As a sum of minterms:

$$\bar{G} = \sum m(0, 2, 4, 6)$$

- As a product of maxterms:


$$\bar{G} = \prod M(1, 3, 5, 7)$$

X	Y	Z	G
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


Sum-of-Products

- *Sum of Products* form: equations are written as an OR of AND terms
- Similar to sum of minterms but does not need to contain all variables in every term
- Can be directly implemented as a *two-level circuit*

$$F = AB + CD$$

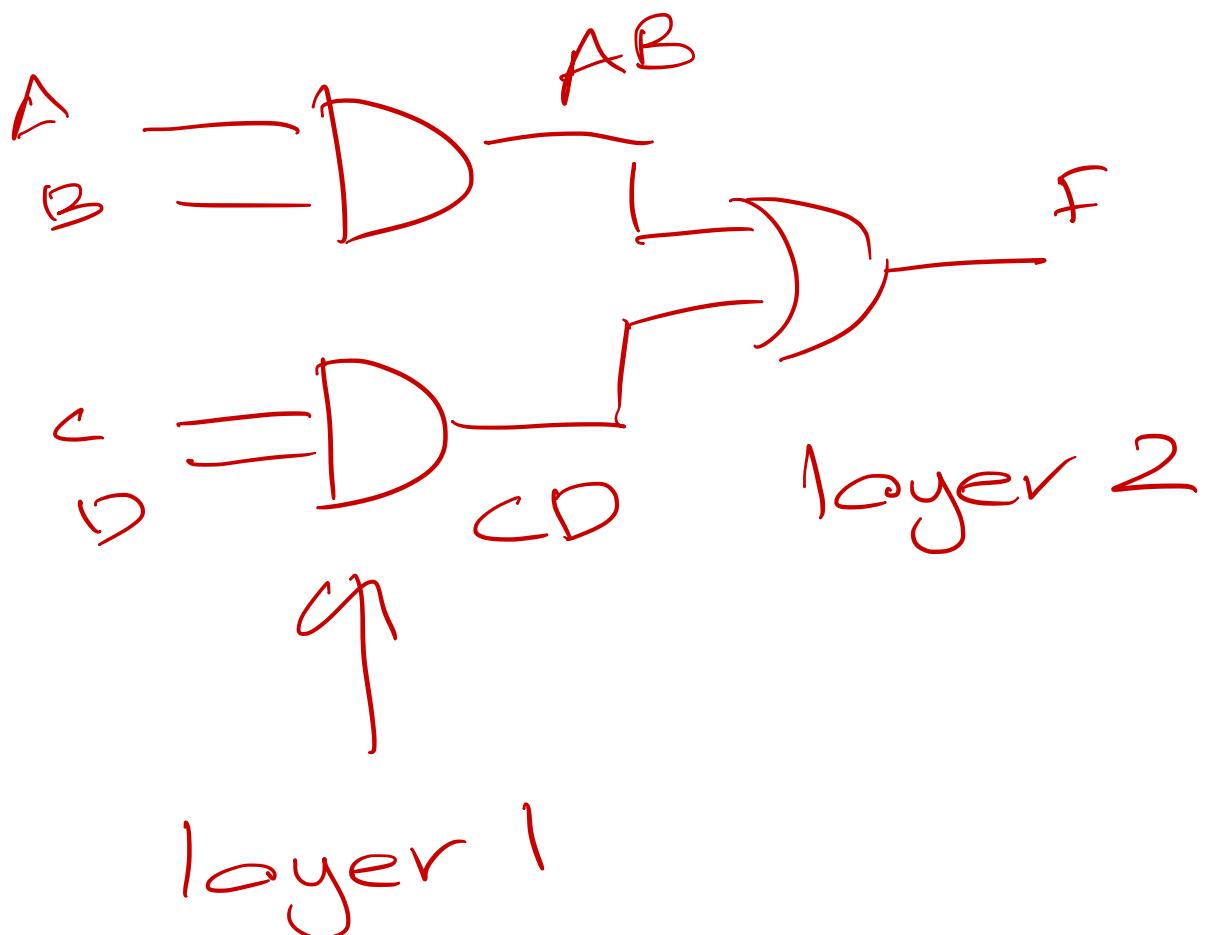


$$F = (A+B)(C+D)$$

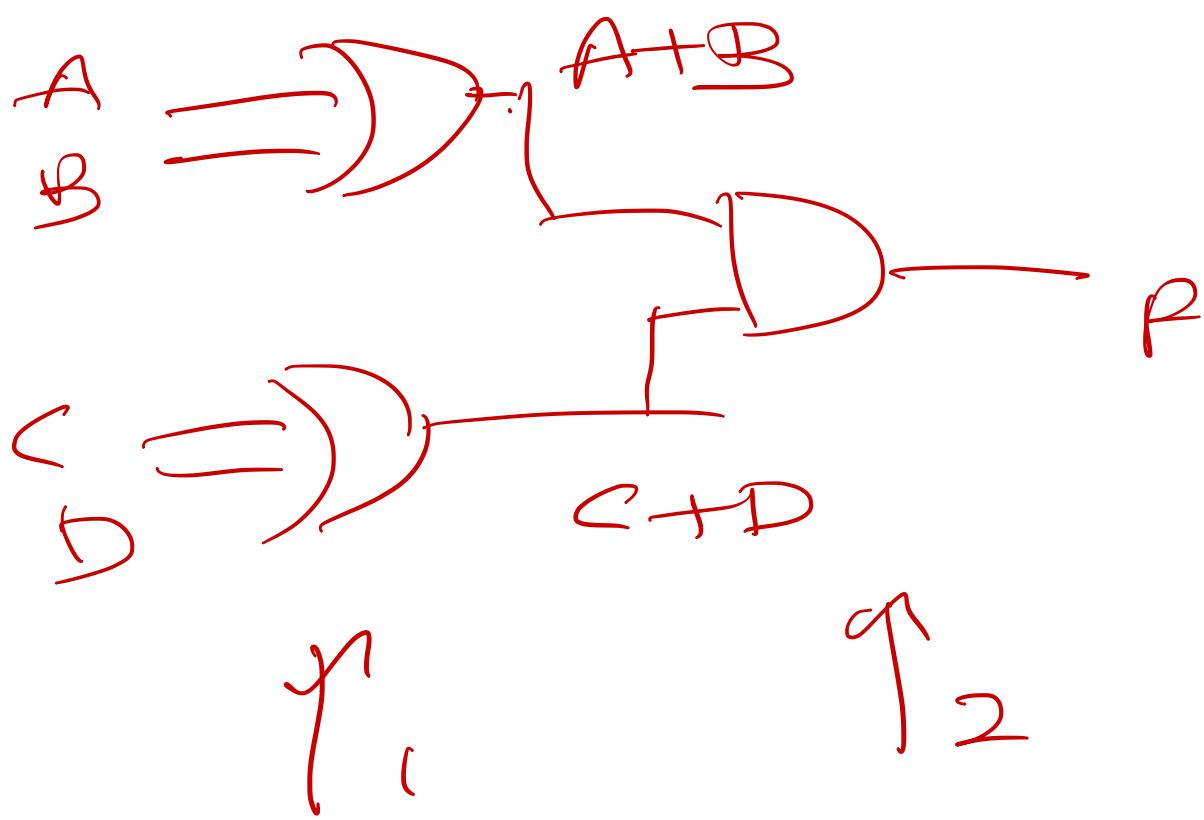

Sum-of-Products Implementation

$$F = \underline{1} + \underline{0} + \underline{0} = 1$$

- Example of the function:

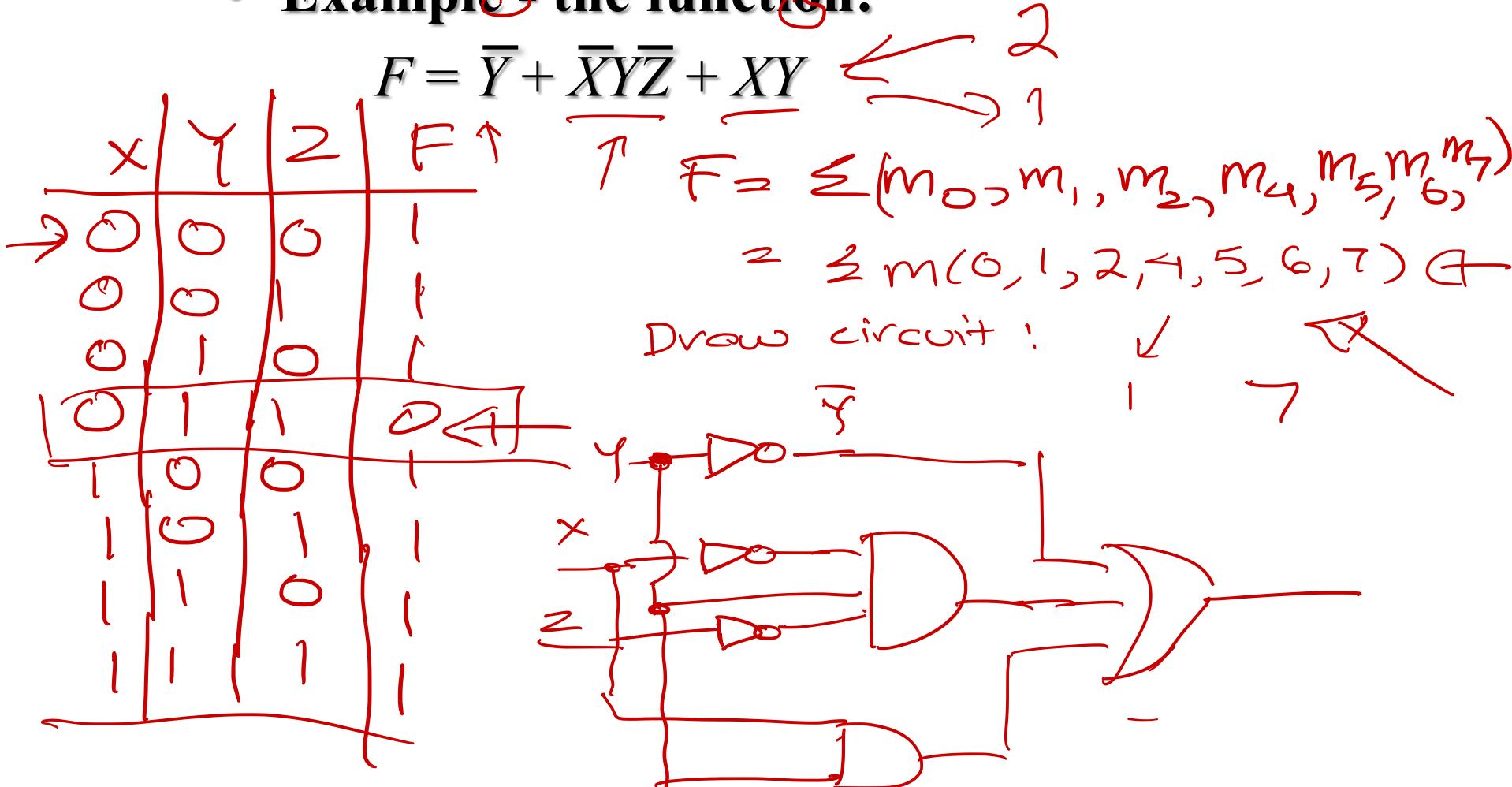


Product-of-Sums

- *Product of Sums form:* equations are written as an AND of OR terms
- Can also be implemented as a two-level circuit

- Example – the function:

$$F = X(\bar{Y} + Z)(X + Y + \bar{Z})$$

is expressed as a POS

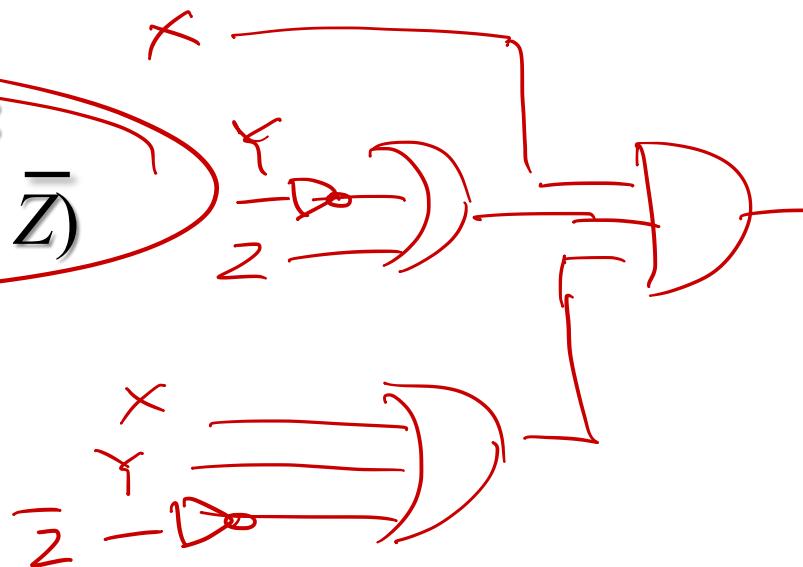

Cost Criteria

- Need a method to measure the complexity of a logic circuit

$$F = AB + \bar{B}\bar{C} + DE$$

6

$$3+1+2=6$$

- Define the *Gate-Input Cost* as the number of inputs to the gates in the implementation

- Can be calculated directly from the equation corresponding to the circuit
- Only count distinct terms and complemented literals

Gate input cost

= sum of

- 1) all literal appearances
- 2) number of terms
- 3) number of complemented literals

$$G = \overline{ABCD} + \overline{A}\overline{B}\overline{C}\overline{D}$$

$$H = (\overline{A}+B)(\overline{B}+C)(\overline{C}+D)(\overline{D}+A)$$


cost of $G = 8 + 2 + 4$
= 14

cost of $H = 8 + 4 + 4$

$$= 16$$

$$G = \overline{A} + (\overline{B}+C)(\overline{C}D)$$

$$\text{cost} = 5 + 3 + 0 = 8$$

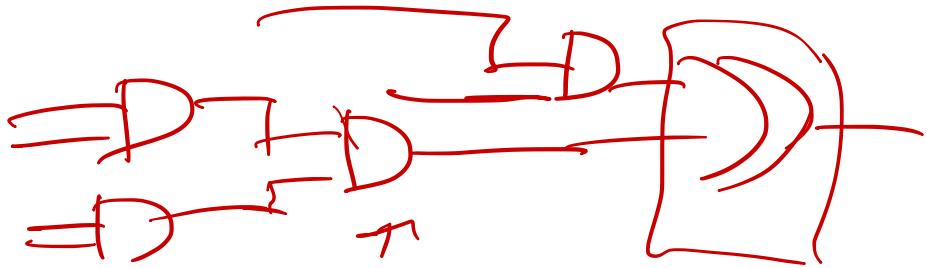

Gate-Input Cost


- Example:

$$F = AB + \bar{C}(D + E)$$

cost = 5 + 2 + 1 = 8

A
5 - 5
1 - 1

- The corresponding logic diagram:

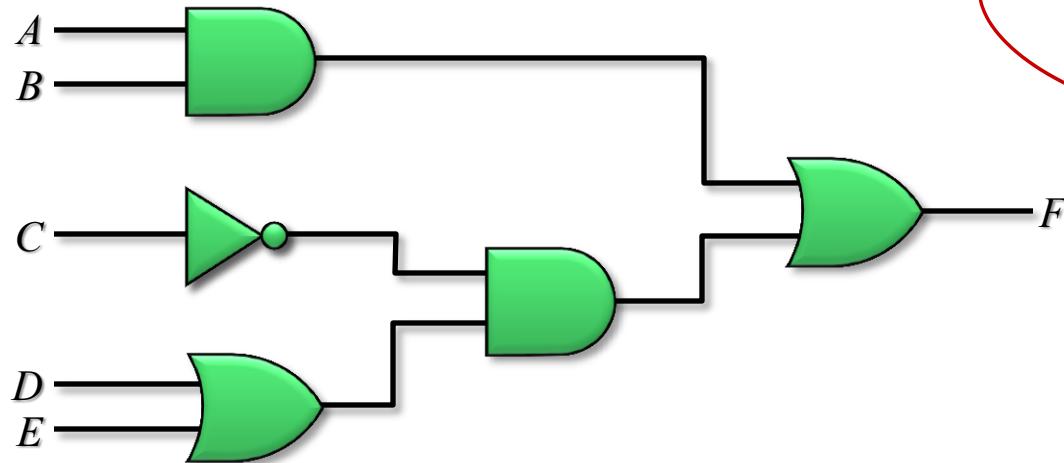

B
5 - 10